

# Wireless World

RADIO and ELECTRONICS



MAR. 1945

1/6

Vol. LI. No. 3

IN THIS  
ISSUE :


ORIGINS OF RADIOLOCATION

# PRIMER ON RUBBER BONDING

NUMBER

**9**

IN SERIES

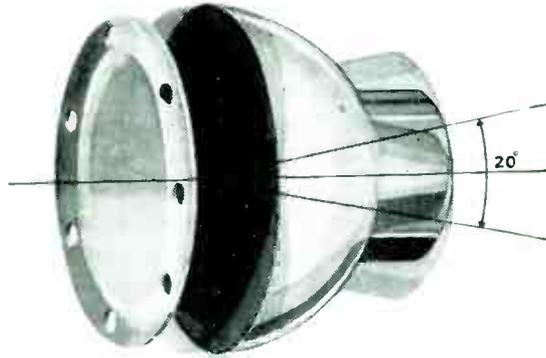

## THE "FLEXILANT" Q TYPE COUPLING

This relatively simple Coupling between a driven and a driving shaft can operate with a conical misalignment of 20° as shown. It can replace the Hook type of coupling with the added advantage and benefit of torsional flexibility. In other words it will absorb vibration originating from either end of the coupling.

Lastly, it can transmit power (dependent upon its size) from .05 H.P. to 45 H.P. at 100 R.P.M.

The Q Type Coupling is an example of how the Technique of Rubber Bonding can be applied to smooth away transmission irregularities on a passenger vehicle. Similarly, and as an improvement to passenger comfort, engine mountings and seat mountings can be planned to incorporate rubber in shear, and, going further into realms of refinement, rubber can also be used in vehicles of this character to eliminate vibration in electrical fittings and instrument panel mountings.

*You may wonder whether a bonded product would solve your problem. We shall know — when you ask us.*



### RUBBER BONDERS LTD.

ENGINEERS IN RUBBER BONDED TO METAL

FLEXILANT WORKS · DUNSTABLE · BEDS.

R 1126



# Over to you - OVER!

Today the output of Osram Valves is devoted to the war effort of the United Nations. Important contributions have been made in research, experiment and development by scientists and technical experts, in collaboration with the war services. But Osram Valves for maintenance of existing equipments are available. Consult your usual supplier.




*When priority of production is no longer essential Osram Valves, incorporating many striking developments in scientific research, will once more be freely available. Then it will be over to you — over!*
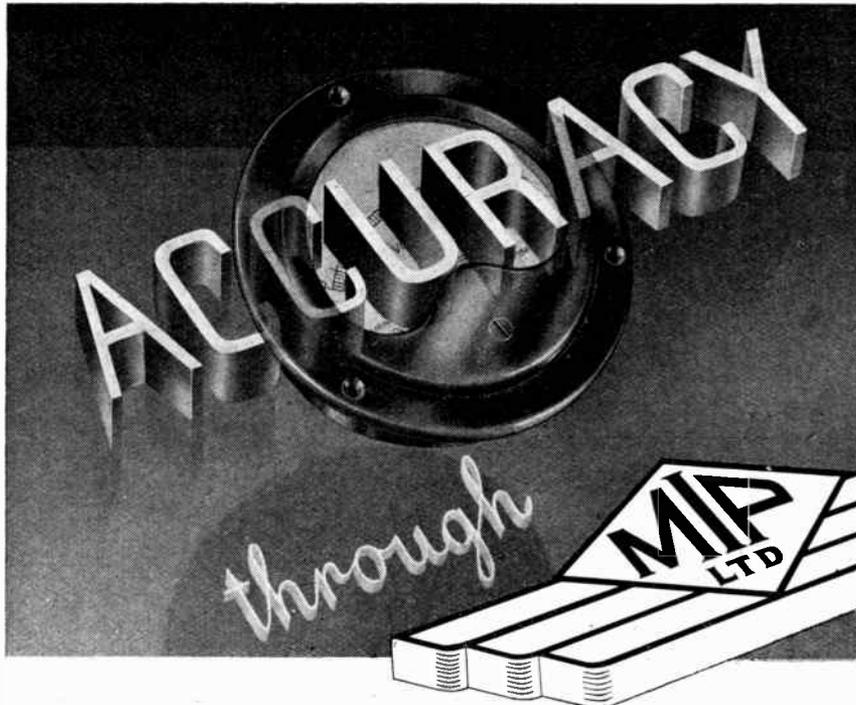
# Osram Valves


MADE IN ENGLAND

Advt. of The General Electric Co. Ltd., Magnet House, Kingsway, London, W.C. 2



Manufacturers  
of  
Switchboard and Port-  
able Pattern Microam-  
meters: Milliammeters:  
Ammeters: Voltmeters:  
Wattmeters and Testing  
Sets.

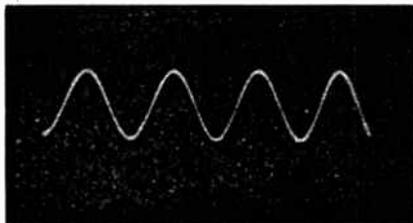**MEASURING INSTRUMENTS (PULLIN) LTD.**  
ELECTRIN WORKS, WINCHESTER STREET, ACTON, W.3.



**B.S.R. STANDARD SINE WAVE SOURCES**  
**TYPE LO.800A. OSCILLATOR**


—an actual oscillogram of output voltage is illustrated—gives good waveform even below 10 c.p.s. This necessitates a minimum "pull-in" between the two H.F. oscillators. Superlative design results in an almost perfect waveform from the lowest to highest frequencies. The output voltage is constant to within a few per cent. over the frequency range. This Model is chosen as a Standard by most Departments. Stable, reliable. Indispensable to all serious workers.

Output up to 5 watts. Three range output voltmeter incorporated—0-250, 0-50, 0-10. Four output impedances, 5000, 1000, 600 and 15 ohms. Frequency ranges (3 models), 0-15000, 0-25000 and 0-50000 c.p.s.



**BIRMINGHAM SOUND REPRODUCERS LTD.,**  
Claremont Works, Old Hill, Staffs.  
Cradley Heath 6212/3. Grams: Electronic, Old Hill

**Wharfedale**

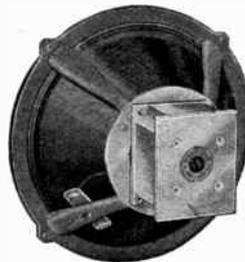

**PUBLIC ADDRESS LOUD SPEAKER**  
**W.12**

**ALCOMAX MAGNET**

ONE of the first large Speakers to be fitted with the new

ALCOMAX Magnet, giving enormous magnetic flux with moderate size (12" x 6 1/2") and weight (9-lbs.).

The entire unit is of robust construction to stand up to heavy input.

**LIST PRICE 135/-**


(Priority Orders Only)

**WHARFEDALE WIRELESS WORKS**

Hutchinson Lane, Brighouse, Yorks. Phone 2-Brighouse 60 Grams: WHARFDEL

Flux Density 11,500 lines/CM<sup>2</sup>  
Total Flux 130,000 lines  
Speech coil impedance 12/15 ohms

**RESPONSE CURVE**

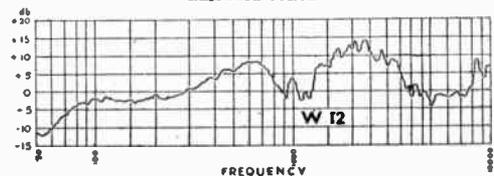



ADVERTISEMENT OF THE TELEGRAPH CONDENSER CO. LTD.

# Get it TAPED with LASSO

Regd. Trade Mark

Lasso Identification Tape will solve all your marking problems and save pounds in time and labour. Lasso provides neat filmic markers which can be applied quickly and easily at any point without disconnecting the leads. No tools are needed to attach it, and it is durable and legible, impervious to heat and fluids.

*Supplies of Lasso Tape are available only for high priority work owing to restrictions on raw materials.*



**CABLE ASSEMBLIES LTD.**

(Subsidiary of Herts Pharmaceuticals Ltd.) **BESSEMER ROAD, WELWYN GARDEN CITY**

**FLOATING ROTOR**

**DOUBLE CONTACT**

*Only in the famous*

# DANK SWITCH

Available in a wide range of circuit combinations for Radio, Television and other applications.

Manufactured by  
**BRITISH N.S.F. CO. LTD.**  
KEIGHLEY, YORKSHIRE

Phone: Keighley 4221/4

Grams: Enesef, Keighley


*There'll come a time . . .*

# Stentorian

## SPEAKERS

**WHITELEY ELECTRICAL RADIO CO., LTD.**  
MANSFIELD, NOTTS.

**F.W.S.CO.**

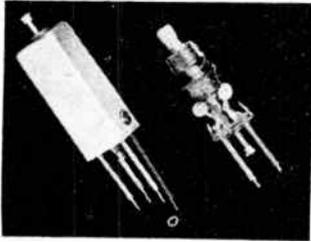

**WORLD'S LARGEST RADIO COIL MANUFACTURERS**

RADIO FREQUENCY INDUCTORS  
INTERMEDIATE FREQUENCY TRANSFORMERS

RADIO FREQUENCY COIL CHOKES

MICA COMPRESSION CONDENSERS

AIR DIELECTRIC CONDENSERS

MICA MOULDED CONDENSERS

SICKLES SILVER CAP CONDENSERS

GANGED PERMEABILITY TUNING COMMUNICATIONS EQUIPMENT

F.M. EQUIPMENT PARTS

U.H.F. RADIO EQUIPMENT

SPECIAL ELECTRONIC EQUIPMENT

**The F. W. SICKLES Co.**  
**CHICOPEE, MASS., U.S.A.**

*the Midget of Quality*

**RAYTHEON "FLAT" HEARING AID TUBES**

They fit inside a delicate ring, they are so small; but they are mighty in dependable performance for hearing aid apparatus. Long lived with low battery drain, RAYTHEON Flat hearing aid tubes give quality performance for electronic hearing aids.




**RAYTHEON CORPORATION**  
HEARING AID TUBE DIVISION  
Newton, Massachusetts.



ARMY-NAVY "E" WITH STARS  
Awarded all four Divisions of Raytheon  
for Continued Excellence in Production.

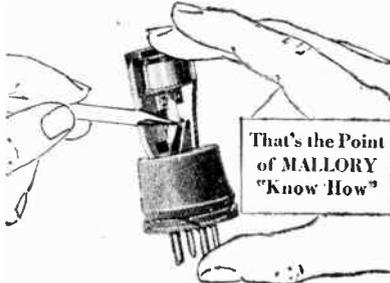P. R. MALLORY & CO. Inc.  
**MALLORY VIBRATORS**  
ARE ALWAYS DEPENDABLE



Contacts in a vibrator take a lot of punishment. They must operate under widely varying conditions of temperature and must "make and break" 115 times a second. Small wonder that alert engineers think of contacts first when selecting a vibrator!

For over 20 years, Mallory has been Industrial headquarters for every type of electrical contact. It has introduced new contact compositions . . . evolved better designs . . . formulated improved surface finishes.

As a result of this wide experience, Mallory equips its vibrators with special grade tungsten contacts which are cut in its own plant from material made to its own specifications. They give longer life, are subject to a minimum of erosion and transfer.

Mallory is ready to apply its special vibrator "know how" to your specific applications.

**P. R. MALLORY & CO. INC.**  
INDIANAPOLIS, INDIANA,  
U.S.A.

Radio and Electronics Division

ALSO  
**"MYKROY" CERAMIC INSULATING MATERIALS**  
**GENERAL ELECTRONIC VACUUM CONDENSERS**

**FOR THE FUTURE**

These Manufacturers will help solve your post-war problems.


Register your name now for full details which will be sent you when supply conditions again permit.

**FRANK HEAVER LIMITED**

**Kingsley Road, BIDEFORD, N. Devon**

**G.I.**

**VICTORY PRODUCTION**

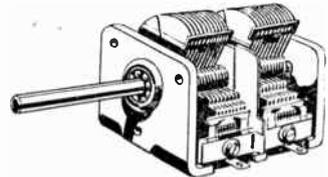

TYPE 2600 MIDGET VARIABLE CONDENSER

WHEN the mission of complete victory is accomplished, General Instrument will help "Win the Peace" by making the best use of still greater knowledge and experience in the manufacture of variable condensers and drives.

**THE GENERAL INSTRUMENT CORPORATION**

**ELIZABETH, N.J., U.S.A.**

**THE SHAPE OF THINGS TO COME..**

**TWO-WAY** radio communication systems, like the plastic-cased beauty illustrated,

are one of the new developments leading industrial designers are thinking of to speed the work of a busy post-war world. Applications of this compact, plastic-cased 'walkie-talkie' are almost unlimited. Naturally, this is only one of thousands of uses plastics will be put to after the war, but it will serve to remind you that post-war planning is being done . . . Kurz-Kasch designers, engineers, tool-makers and moulders . . . specialists for a generation in plastic planning and moulding will help you with your problems.



**KURZ-KASCH INC.**  
Planners and Moulders for the Age of Plastics  
**DAYTON · OHIO · U.S.A.**




**GOODMANS**  
*New* **T 2-12"**  
**LOUDSPEAKER**

for the **SERVICES**  
and all **PUBLIC ADDRESS PURPOSES**  
including **FACTORIES, WORKSHOPS,**  
**CANTEENS, ETC.**

*Goodmans*  
**LOUDSPEAKER & TELEPHONE ENGINEERS**

**INDUSTRIES, LTD.**  
**WEMBLEY, MDX.**

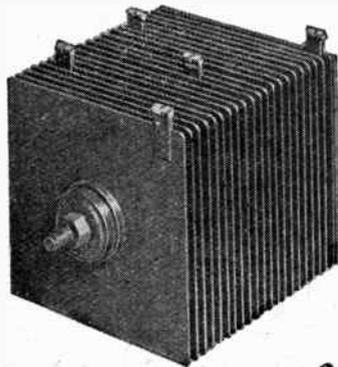

## The finest rectifier we know how to build

Thousands can—and will—testify that fifteen years ago we built rectifiers that are still giving efficient service . . . and yet to-day we are producing better rectifiers than we could have built even a year ago. The mass of accumulated experience enables us to continue pioneering new and advanced designs and the "Westalite" selenium compound unit is the direct result of years of steady progress towards even better rectifiers.



### METAL RECTIFIERS

**WESTINGHOUSE BRAKE & SIGNAL CO., LTD.,**  
**PEW HILL HOUSE, CHIPPENHAM, WILTS.**

## M.R. SUPPLIES

We continue to offer **RADIO AND ELECTRICAL MATERIAL** of the same high specification for which we have been renowned throughout the war years. All prices net cash and all items brand new. Immediate delivery.

**POWER PACKS.** Operation from 6 or 12 v. accumulator and suitable for mobile amplifier or radio. Made for the G.E.C. 2206 Mobile 8-watt Amplifier and delivering fully smoothed 300 v. 80 m.a. Sturdily built into steel-closed chassis 10in. by 9in. by 7in. overall, weight 23 lbs. Complete with plug-in vibrator and Osram U.52 Rectifying Valve, ready for use (except two small fuses). Wonderful opportunity, **£6.17.6.** (Note: We have only 65 of these and we advise an early call. We can pack and despatch for an extra 7/6.) Also a few G.E.C. 2332 **POWER PACKS** for 60-watt Amplifiers. Operation A.C. mains 190/250 v. H.T. delivery 500 v. 350 m.a. and 6.3 v. for 8 heaters. Large output transformer is incorporated with matching of four KT66 in parallel push-pull to 2.5, 5, 7.5, 15 and 600 ohm loading. In robust closed steel chassis, 15in. by 9in. by 7in., weight 48 lbs. Complete with two U.18 Osram Rectifiers, **£20** (last few—callers only).

**HEAVY DUTY OUTPUT TRANSFORMERS.** Limited supply again available. Handling 25-watt A.C. at high fidelity. Tapped prim. and sec. with p.p. and providing 11 ratios from 12/1 to 75/1, finished in brackets with terminal panels. Weight approx. 10 lbs. There is no better O.T. **59/6.** (Pkg./post 2/-)

**VITAVOX 12-inch P.M. SPEAKERS,** model K12/10, handling 10-watts, 15-ohms coil. Undoubtedly the speaker for the high-fidelity enthusiast. Small delivery at **£7** each. (Despatch 5/-)

**GRAMPIAN M/COIL MICROPHONES,** in square suspension frame with mounting boss, **£4.17.6.** Fully recommended. Also small supply of same make Senior model for highest quality work, **£7.15.0.** **G.E.C. CURRENT-FED MICROPHONES** for connecting direct to 15-ohm Speaker with 12-volt battery—require no amplifier. Ideal for instructions and short announcements, instantaneous in action and ample volume. Complete with matching transformer, **£9.15.0.**

**MICROPHONE STANDS,** all chromium. Table (extending), **29/6;** Floor, extending to 5ft. 6in. and collapsing to 2ft. for portability, **45/6.**

**GOODMAN M/COIL SPEAKER MICROPHONE UNITS.** Latest model with new high-efficiency magnet and protective front grille. Dia. 3 1/2in., imp. 15 ohms. A real marvel both as speaker and microphone, **30/-.** **METAL CABINETS** to suit (soiled). Octagonal 5 1/2in. with octagonal opening 3in. dia., **9/6.**

**STEP-DOWN MAINS TRANSFORMERS** for Chargers, L.V. Lighting, etc. Prim. tapped 200/250 v., Sec. 5, 12 and 17 v. at full 6-amps., **49/6.** (Despatch 2/-)

**SLIDING RESISTANCES** (100-watts). Full range again in stock. 4 ohms 5 amps., 10 ohms 3 amps., 50 ohms 1 1/2 amp., 100 ohms 1 amp., 200 ohms 0.7 amp. and 400 ohms 0.5 amp. Fully enclosed, excellent slide action, any one, **25/-.**

**"PYROBIT" ELECTRIC SOLDERING IRONS.** Easily the most popular and handy iron. We stock 220/250 v. only. "Instrument" model with pencil bit, **22/-.** Spare adjustable angle bit, **4/6.** Spare Elements, **3/6.**

**TRANSFORMER BOBBINS.** (Replacement for Eya, H.M.V., Marconi, etc.). Prim. tapped 200/240 v. Secs.: 350/350 75 m.a., 4 v. 4 a. and 4 v. 3 a. Core opening 1 1/2in. sq., by 1 1/2in. through 1/8". Also same but with 6.3v. 4a. and 5v. 3a., same price.


**VOLTAGE CHANGING TRANSFORMERS,** 200/250 v. to 100/110 v. (and vice versa). Fully shielded with countersunk terminal blocks, properly rated. 75 va., **29/6.** 120 va., **37/6.**

**G.E.C. PROJECTOR P.A. SPEAKERS** (as previously described) with 42in. all-metal horn, 10-watt, **£10.5.0.** 12-watt, **£12.** (Carr. either, 7/6). Units only, 10-watt, **£5.5.0.** 12-watt, **£7.10.0** (Standard thread).

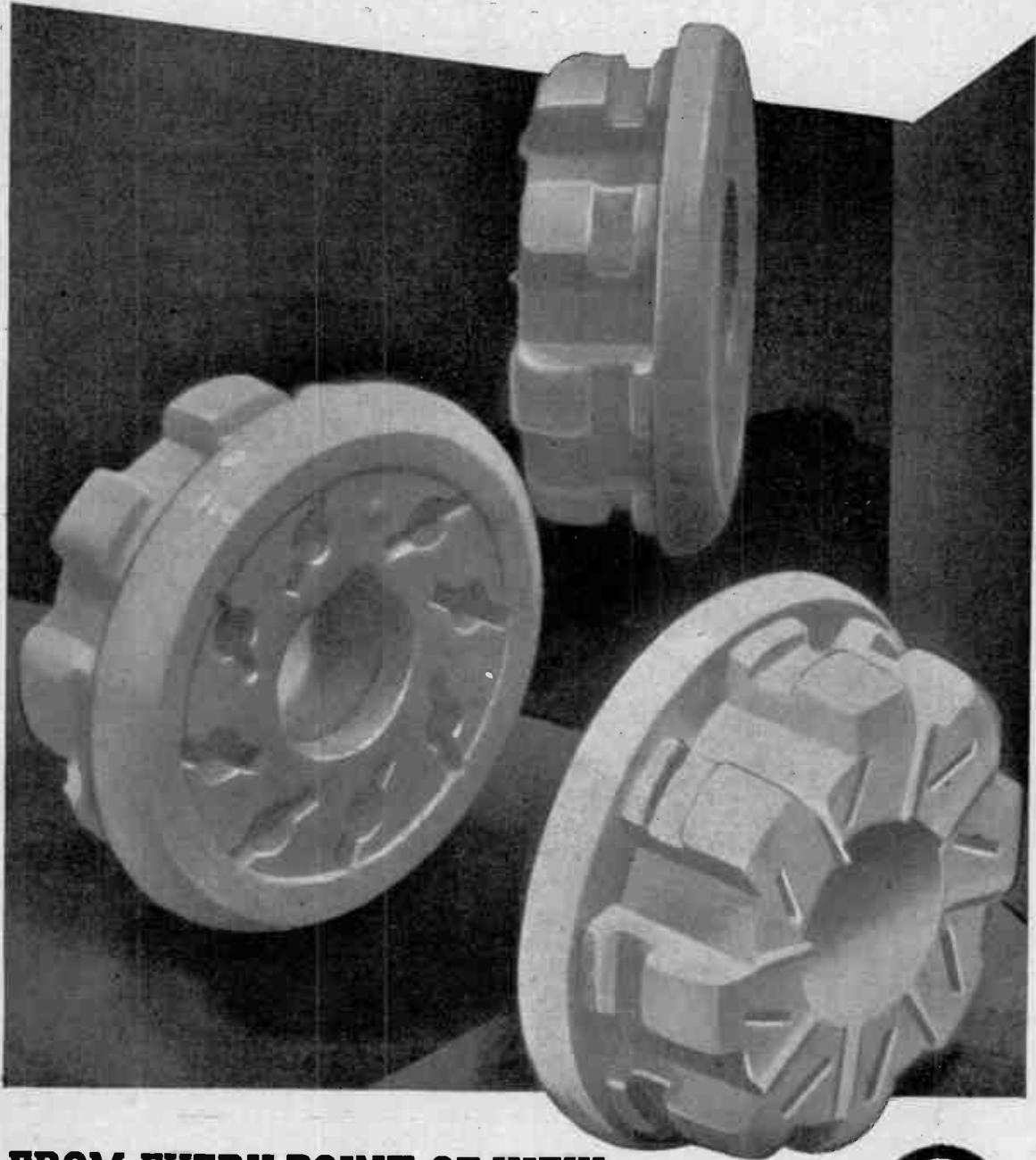**E.T.C. TOGGLE PRESSES** (as previously described), in stock, **£23.**

Please include sufficient for packing/post (where not stated).

**M.R. SUPPLIES, 68, New Oxford Street, London, W.C.1**  
(Telephone: MUSeum 2958)



## FROM EVERY POINT OF VIEW

Frequentite is the most suitable material for all high frequency applications. Ten years ago we introduced the first British-made low loss ceramic, and consultation with us before finalising the design of new components is a wise precaution.



# STEATITE & PORCELAIN PRODUCTS LTD.

Head Office: Stourport-on-Severn, Worcester.

Telephone: Stourport 111.

Telegrams: Steatain, Stourport.

SP20

# So much depends on them



"AVO" Electrical Testing Instruments are actively engaged on the fighting and factory fronts, sharing a great responsibility with a proud sense of duty and high confidence in the future

It will therefore be appreciated by our numerous trade friends that we can now only accept orders which bear a Government Contract Number and Priority Rating.



Sole Proprietors and Manufacturers :-

**THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.,** Winder House, Douglas Street, London, S.W.1.

'Phone: VICTORIA 3404-3

For *Reliability*

**TRIX**

Trust *TRIX*

Quality **SOUND** Equipment

THERE ARE TRIX AMPLIFIERS FROM 5 TO 500 WATTS FOR PRIORITY WORK

**THE TRIX ELECTRICAL CO. LTD.**  
1-5, MAPLE PLACE, TOTTENHAM CT. RD.  
LONDON, W.1.  
Tele: MUSEUM: 5817 Grams & Cables: TRIXADIO, WESDO, LONDON.

**CASE** by **IMHOF'S**  
ESTABLISHED 1845

THE HALLMARK OF A GOOD INSTRUMENT

If you are inclined to the view that your instruments deserve a case that is better built and of more attractive and functional design, or you build equipment that needs precision sheet metal work, you will be interested to have this catalogue. A penny stamp and the request on your business letterhead will bring it you.


ALFRED IMHOF LTD. 112-116 NEW OXFORD STREET, LONDON, W.C.1. MUSEUM 5944

BEACONS OF RELIABILITY

EDDYSTONE

Radio


PRODUCTS

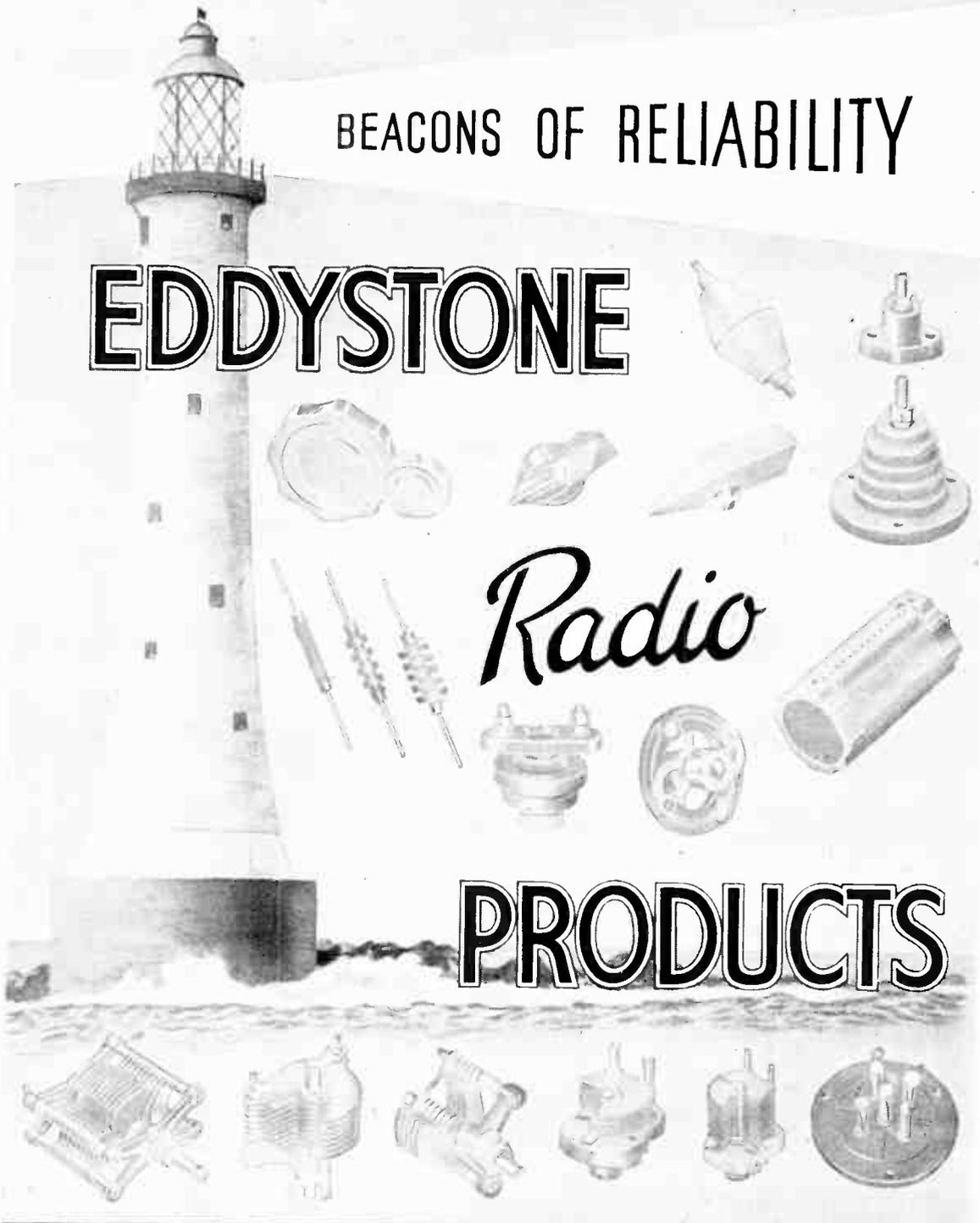

MANUFACTURED BY  
**STRATTON & CO., LTD.** EDDYSTONE WORKS **BIRMINGHAM.**  
 TELEPHONE: PRIORITY 2231 CABLES: 'STRATNOID' BIRMINGHAM.  
 LONDON AGENTS:-  
**WEBB'S RADIO.** 14, SOHO STREET, OXFORD STREET, LONDON. W. I.  
 TELEPHONE: GERRARD 2089



# REDIFFUSION WAVEMETER 605A

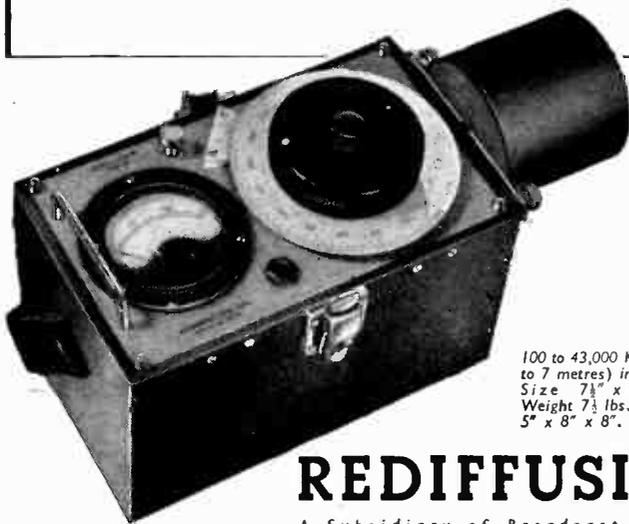

The compact, precise check on every ship and shore radio station. Used by very many senior inspectors and officers for setting and maintaining accurate frequency calibration. Immediate delivery.

100 to 43,000 K.C. (3,000 to 7 metres) in 8 ranges.  
Size 7½" x 9½" x 6½".  
Weight 7½ lbs. Coil box 5" x 8" x 8".


Write for details to Sales I.

## REDIFFUSION LTD *REDIFON*

A Subsidiary of Broadcast Relay Service Limited

Designers and manufacturers of Radio Communication and Industrial Electronic Equipment

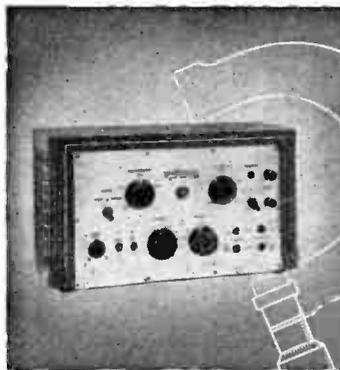VICTORIA STATION HOUSE • VICTORIA STREET • LONDON • S.W.1 (PHONE VICTORIA 8831)



AUDIO  
AMPLIFIERS &  
SUB-ASSEMBLIES  
TO *Critical* STANDARDS

In addition to Standard Amplifiers the activities of Acoustical include Special Amplifiers for Industrial Applications, Microphones, Transformers, Coil Winding, Sheet Metal Work, Stampings, Switch Assemblies, etc.



**ACOUSTICAL**  
MANUFACTURING Co. LTD.  
HUNTINGDON • TEL. 361

*The*  
**LOUDSPEAKER**  
YOU KNOW BY EAR  
*now making*  
**EVERY WAR EFFORT**

**BRITISH Rola LIMITED**  
DEVIZES • LONDON • BIDEFORD  
ENGLAND




From 100° in the shade to 40° below. Dubilier Type 4800 series metal-cased Tubular Paper Capacitors are made to stand up to the most stringent operative conditions of extremes in temperature. The elements are enclosed in seamless close grained metal tubes. These Dubilier Capacitors are what is meant by the catch-phrase "tough". Unaffected by extremes of temperature, excessive humidity or high altitudes—they are essential wherever such arduous conditions are anticipated.



*The name is . . . Dubilier*

C.R.C.13

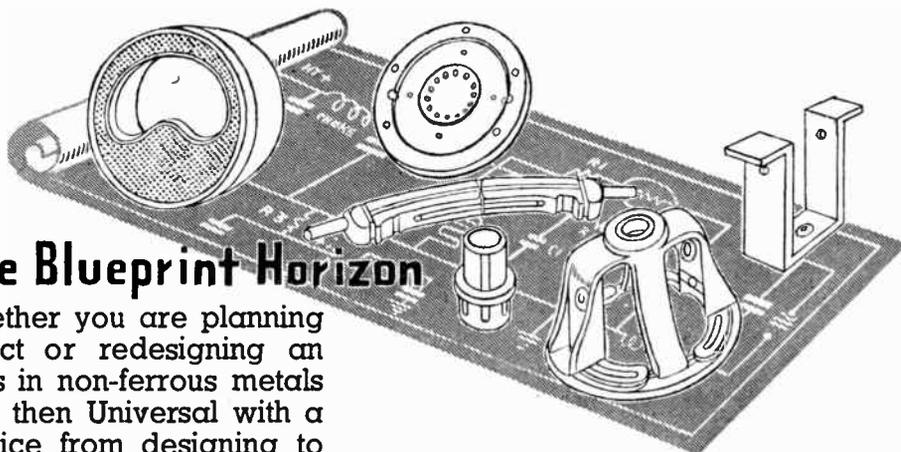

## Beyond the Blueprint Horizon

No matter whether you are planning a new product or redesigning an old—if castings in non-ferrous metals are called for then Universal with a complete service from designing to finishing can help you. On post-war products our Technical Staff will gladly work with your design and engineering departments so that your job is

ready for pattern or die making immediately restrictions are lifted. For immediate essential work the whole of our service is at your disposal... NOW

### UNIVERSAL ENGINEERING COMPANY

GRAVITY DIE CASTINGS, PRESSURE DIE CASTINGS, AND SAND CASTINGS IN NON-FERROUS METALS

### CASTLE BOULEVARD · NOTTINGHAM

and at CALLARD HOUSE, REGENT STREET, LONDON, W.1

# CELESTION

## LOUDSPEAKERS VALVEHOLDERS

Celestion Limited  
Kingston-upon-Thames  
Telephone : KINGston 5656-7-8

## MINIATURE or MIDGET

We specialise in their manufacture

**HIVAC**  
THE SCIENTIFIC VALVE

BRITISH MADE

*Originators, designers & manufacturers of Midget Valves*

HIVAC LIMITED, Greenhill Crescent, Harrow on the Hill, Middx. Phone: HARROW 08 95



APPROVED BY  
A.I.D. to D.T.D. 599, G.P.O. and  
all other Government  
Departments.

- Contains 3 cores of extra active non-corrosive flux. No extra flux required.
- Speedily makes sound joints on oxidised surfaces.
- Most economical solder to use to ensure speed in production and freedom from "dry" or "H.R." joints.

★ **ERSIN**

# MULTICORE SOLDER

The only Solder Wire with 3 cores of flux

Firms are invited to write for comprehensive technical information, including useful tables of melting points, etc. Sent free with testing samples.

Single reel rate nominal 1 lb. reels.		
13 SWG	- -	4/10
16 SWG	- -	5/3
Above prices subject to usual trade discount.		
‡ cwt.—ton lots at bulk rate. 6d. cartons for home use, available at most good radio and electrical dealers, ironmongers, etc.		

**MULTICORE SOLDERS LIMITED**

Commonwealth House, New Oxford Street, London, W.C.1. Tel.: CHAncery 5171-2

★ IN THE DEVELOPMENT AND MANUFACTURE OF

# Radio Frequency **CABLES** **B.I.** HAVE PLAYED A LEADING PART

★ . . . and though supplies are directed to the Services, the experience gained over a considerable manufacturing period is available for the benefit of approved users.

Note.—From fundamental principles, B.I. have made outstanding contributions to design and construction of cables for radio frequency transmission and have perfected production technique.



© BRITISH INSULATED CABLES LTD. PRESCOT, LANCs.


## SENSITIVE INSTRUMENTS



MODEL 200  
2" SCALE



MODEL 350  
3½" SCALE

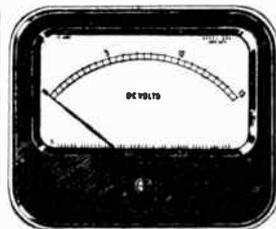

MODEL 500 5" SCALE

Specialising in the manufacturing of robustly constructed sensitive Moving Coil and Rectifier Instruments, we are regularly supplying these with sensitivities as low as 20  $\mu$ A full scale in both Moving Coil and Rectifier types.

These Instruments are also available as Thermocouple types as low as 1.25 mA full scale. Spade type or Knife Edge pointers and Mirror scales are available on most instru-



MODEL 250  
2½" SCALE



MODEL 250  
2½" SCALE


ments and illuminated dials can be supplied on Model 400 and 500 instruments.

# Taylor

electrical instruments

DELIVERY FROM STOCK can be made for many ranges of instruments against urgent priority orders.

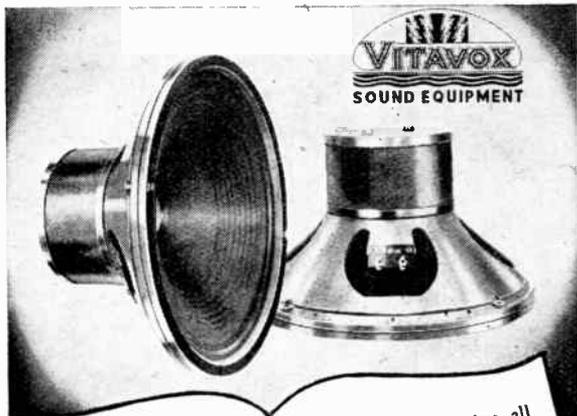TAYLOR ELECTRICAL INSTRUMENTS LTD.,  
419-424 MONTROSE AVENUE, SLOUGH, BUCKS. Phone: Slough 21381




IT is a fact that although VITAVOX K12/10 and K12/20 P.M. Speakers are not available in unlimited quantities, their quality is such that they are well worth waiting for.

It is a fact too that all specification figures are actual and not nominal.  
VITAVOX LIMITED,  
WESTMORELAND  
RD., LONDON, N.W. 9.  
Phone Colindale 8671/3
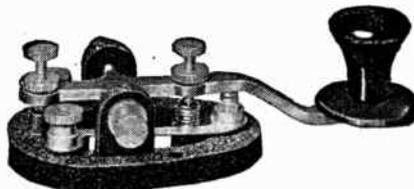
## JUST A REMINDER!

ALL who are interested in Morse Code and Short-Wave work are invited to refer to the details of the Raymart products advertised in the following issues of this journal.

- DECEMBER 1944. Page 12. RAYMART "SPEED KEY"
- JANUARY 1945. Page 6. RAYMART MICRO-VARIABLE CONDENSERS
- FEBRUARY 1945. Page 6. RAYMART COILS



Prompt attention is given to all orders and enquiries

# RAYMART

CRAFT A CREED

Telephone:  
Midland  
3254

48, HOLLOWAY HEAD, BIRMINGHAM, 1.

# For Peak Performance

*with High Voltages*



U.I.C. Fixed Ceramic Pot and Plate Condensers have been primarily developed for use in transmitter circuits. Made only from the highest grade raw materials and subjected to the most rigorous mechanical and electrical inspection, their performance especially with H.F. loads and high voltages is unsurpassed. TYPE APPROVED. Full details on request.

**UNITED INSULATOR CO. LTD.**  
 12-22 LAYSTALL STREET, LONDON, E.C.1  
 Tel: TERminus 7383 (5 lines) Grams: Calanel, Smith, London



**CERAMIC**  
*High-Voltage*  
**CONDENSERS**

**THE PIONEERS OF LOW-LOSS CERAMICS**



**5 mmf/ft**

NEW LOW LEVELS in capacity and attenuation of CO-AX Cables mean new possibilities in electronic equipment design both for the war effort and for the post-war electronic age.

Write for characteristics

**BASICALLY BETTER AIR-SPACED**

**CO-AX LOW LOSS CABLES**  
**TRANSRADIO LTD. 16 THE HIGHWAY BEACONSFIELD-4-BUCKS.**



Doing vital service amidst the battle smoke


**DAGENITE AND PERTRIX BATTERIES** DIIC144

Sole Concessionaires:  
**HOLSUN BATTERIES LIMITED, 137 Victoria St., London, S.W.1**

# BE PREPARED

The demands for P.A. Equipment, and especially of the more efficient Portable Types, is steadily growing, and the far-sighted will be prepared by determining that they will not be "caught short." But although the new "Universal Fifteen" AC-DC (190-260 v.) Portable Amplifier is coming off our production lines in a steady flow, supplies are not yet up to peace-time level, so we must of necessity deal with all orders in strict rotation. If you are amongst those who demand the effective welding together of experience, quality and economy in P.A., then you will do well to write now for fullest details of R.S. Equipment right away.

**R.S.**  
*Amplifiers*

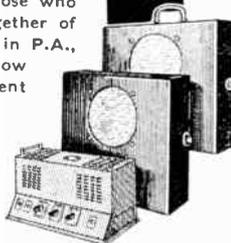

**R.S. AMPLIFIERS LTD.**  
 24, HIGHFIELD ROAD, SHEPPERTON, MIDDLESEX  
 Walton-on-Thames 1019

## FAN DISC LOCK WASHER VIBRATION PROOF

Overlapping teeth cannot be flattened. Teeth grip and cannot shake loose. In steel or phosphor bronze. Sizes from 10 B.A. For all types of bolts and screws.

SEND FOR SAMPLES, PRICES & LITERATURE



**FAN DISC LTD**

NORTHWOOD ST., ST. PAUL'S, BIRMINGHAM 3

*Superspeed*

**CORED SOLDER**

**A.I.D. APPROVED**

**H. J. ENTHOVEN & SONS LTD.**  
 230 THORNTON ROAD, WEST CROYDON, SURREY  
 THORNTON Heath 2462

# ◆ LINAGLOW LIMITED ◆

## offer

### SERVICE KITS

- 81. 1 8-mfd. 400/500 v. Electrolytic. 12 each assorted Tubular Paper Condensers, Carbon Wire End Resistors, Silver and Moulded Mica Condensers. New, ex-television, 10/6.
- 82. 1 8-mfd. 400/500 v., 1 32-mfd. 320 v. Electrolytics, 12 each Tubular Paper Condensers, Silver and Moulded Mica Condensers, Carbon Wire End Resistors, 1 Volume Control. New, ex-television, 21/6.
- 83. 1 8-mfd. 400/500 v., 1 32-mfd. 320 v., 1 16 x 8 mfd. 400/450 v. Electrolytics, 25 each Tubular Paper Condensers, Silver and Moulded Mica Condensers, Carbon Wire End Resistors, 37/6.
- 84. 3 8-mfd. 400/500 v., 3 32-mfd. 320 v., 1 8 x 8-mfd. 400/500 v., 1 16 x 8-mfd. 400/450 v., 1 10 x 10-mfd. 400/500 v. Electrolytics, 25 each Tubular Paper Condensers, Silver and Moulded Mica Condensers, Carbon Wire End Resistors, 6 yds. sleeving, 6 yds. P.V.C. Cable, 3 Tone Controls, 6 assorted Valveholders, 25.


- MAINS TRANSFORMERS.** 350-0-350, 4 v. 6 amp. C.T. 4 v. 2 amp. 100 m.a. Heavy Laminations, pre-war stock. Bargain, each 27/6; 350-0-350, 6.3 v. 3 amp. C.T., 5 v. 2 amp., 100 m.a., each 32/6.
- LOUDSPEAKER TRANSFORMER.** Pentode Output, 40:1, 60 m.a., 4/6. Midget Multi Ratio 60:1, 80:1, 40 m.a., 8/6. Multi Ratio 40:1, 60:1, 80:1, and push-pull, 80 m.a., 12/6. Pentode Output, 12/16 ohms, 100 m.a., 12/6. Heavy duty, multi ratio, 24:1, 41:1, 48:1, 1.5 x 1.82:1, 116:1, & P.P. 80 m.a., 15/6. 3:1 intervalve, 10/6.
- LOUDSPEAKERS.** 3 ohm Voice Coil. 6 1/2 in. Celebration, with transformer, 30/-, 8 in. Rola, 19/8; 8 in. Goodman, 22/6; 10 in. Mains Energized 250, 500 and 1,200 ohms, 35/-; B.T.H. model R.K., 10 in. Mains Energized Loudspeakers, 1,000 ohms field, 16 ohms speech, weight 28 lbs., reconditioned as new. Ideal for P.A. work, 26/6. Od. See Transformers above to suit.
- AERIAL AND OSCILLATOR COILS.** Best D.S.C. wire wound, colour coded on bakelite formers. Short, Medium and Long Wave, 16/50 m.; 200/550 m.; 1,000/2,000 m.; with circuit diagram, 15/- the set.
- I.F. TRANSFORMERS.** 465 Kcs., iron-cored Litz wound, aluminium can. Limited quantity, 17/6 matched pair, 9/6 each.
- WANDER PLUGS** in 2 colours, 3/- per doz.
- ELECTRIC SOLDERING IRONS,** 60 watt, 200/250 v., A/D/C, chrome plated, usually 13/9, 9/6.
- SCREENED INTERLACED FLEXIBLE MICROPHONE CABLE.** Twin, 6 yards for 8/9; Single, 1/- per yard.
- ELECTRIC POWER METERS,** as new, pre-war manufacture, 1/- in all 4 type, suitable for electric fires, cookers, etc. Ideal for boarding houses, hotels. Complete less locking key. Maker's price 70/-, each 35/-.
- WESTINGHOUSE METAL RECTIFIERS,** type H1, 2 1/2 v. D.C., 10 m.a. Bargain, each 3/6.
- M. & L. T.R.F. AERIAL COILS,** aluminium screened Phillips, 200/585, 725/2,000 metres, complete with circuit diagram, 2/9 each.

**VALVES,** American types, at B.O.T. controlled retail prices. For replacement purposes only. 6F5, 12F5, 12J5, 12SF5, 1H5, 9/2; 5Y3, 1C5, 1N5, 11/-; 6Q7, 12Q7, 11/7; 6F5, 6K6, 6K7, 6L7, 12J7, 12SJ7, 36, 1A7, 6V6G, 12/10; 6A8, 6BT, 6SA7, 14/-.

Also British Valves at manufacturers' List Prices. 6X5, 6U4, 6U6, 11/-; H141D1, T1D4, 11/7; AC/VP2, CL4, EF39, KTW61, Pen 45, SP41, SP42, T41, VP41, 12/10; D1 diode 1In. Peanut valve with valve-holder, 12/10; ECH3, ECH3, X63, 12Z3, 25Z5, 35Z4, 14/-; AC6 Pen, EL35, Pen 46, U21, 15/3; prices include Purchase Tax. Add 3d. per valve post.

\* Post Office permit necessary.
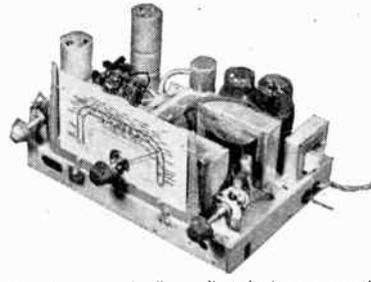
### T.R.F. 3-WAVEBAND 4-VALVE CONSTRUCTORS KIT, 17-2,000 m.




Aluminium screened coils, excellent short wave reception (the special coils used in this circuit give a performance equal to a superhet), 44 watts output, complete with loudspeaker, all parts, wiring and theoretical diagram—nothing extra to purchase. Chassis dim.: 12" x 8" x 6" to top of dial. 200/250 v. A.C.

- Including Tax **11 1/2 Gns.**  
Case and packing, 5/- extra.
- VALVEHOLDERS—AMPHENOL TYPE.** International or English (octal, chassis mounting, 1/- ea., 10/6 per doz. English Wafer type, 4-, 7-, 8-pin, 6 for 2/6).
- LOUDSPEAKER FRETTS.** Coppered brass, 14 1/2" x 9 1/2" x 9 1/2"; silk covered, 12" x 9 1/2" ply, 6 1/2" hole, 4/6.
- LINES CORDS,** 3-way heavy duty, 3 amp., 360 ohms, 9/6; 480 ohms, 13/6; 600 ohms, 15/6. 2-way, 360 ohms, 5/6; 480 ohms, 7/6; 600 ohms, 9/6.
- WIRE END CARBON RESISTORS,** 1/2, 1 and 2 watt Manufacturers' types. New, ex-television. Parcel of 100 assorted, 22/6.
- TUBULAR PAPER CONDENSERS,** 350/500 v. D.C. working. New, ex-television. .0001, 3/-; .0025, 4/-; .01, 6/-; .02, 7/-; .04, 8/-; .08, 9/-; .1, 10/-; .25, 12/- per doz. Parcel of 60 assorted, 22/6.
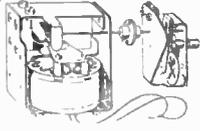
### SYNCHRONOUS MOTORS

200/250 v. A.C. 12 m.a., suitable for electric clocks, etc. Supplied complete with gears. Each **27/6**



### RELAYS

Complete with circuit breaking switch. 200/250 v. A.C. 60/80 v. D.C. 300 m.a. 15 amp. switch Each **7/6**

**RELAY AND METAL RECTIFIER AND MAINS TRANSFORMER** complete. Input 200/240 v. A.C. Output, 12 v. D.C. 150 ohm, 20 m.a. 35/-.

**VIBRATORS,** 4-in 6v., best quality American, 15/6.

**STRIPLIGHT METAL REFLECTORS** made from heavy gauge steel, 14" long, complete with two B.C. lamp-holders, less lamps, 10/6 each.

**RADIO MECHANICS' LONG-NOSE PLIERS,** ex-Government stock, reconditioned like new, exceptionally cheap, 4/- each. Extra long, 8/-, 10/6 each.

**RADIO MECHANICS' SIDE CUTTERS,** ex-Govt. stock, reconditioned like new, exceptionally cheap, 4/6 ea.

**HIGH VOLTAGE BRAIDED SLEEVING,** 1 and 1 1/2 mm., 1st class quality, 3/6 per dozen yards.

**P.V.C. CABLE,** 14/36, Red, Green and Blue, 2/- per dozen yards.

**ENAMELLED COPPER WIRE,** 30 s.w.g., 1 lb. spools, 5/- per spool.

**VOLUME CONTROLS,** 1, 5, 10, 20, 25, 50 and 100 thousand ohms, 1, .1 and 2 meg., without switch, 4/9 each. As above, with switch, 6/9; 100,000 ohms, 1 meg., Double Pole Switch, best American, 7/6; 2,000 ohm only, wire wound, 3/-; 1,000 ohm only, carbon, with screw adjustment, 1/6 each.

**D.C. RELAYS,** 50 ohm 4/8 v. 8 circuit, brand new, worth 15/- each 7/6.

**DIRECTIONAL BAFFLE** for R.K., 3ft. x 2ft. 6in. x 1ft. 6in., felt lined with suspension hooks, made from 1in. ply. As new, 23 15s. Od.

**MICRO VARIABLE CONDENSERS,** 30 mmfd. and 60 mmfd. Ceramic insulation, ideal for short wave work, 3/9 each.

**TUMBLER SWITCHES,** 2-way, ex-Government contract, 5 amp., exceptional value, 1/9 each.


**L.F. SMOOTHING CHOKES,** finest quality, 20 and 60 henrys, 150 m.a., 16/9 each.

**UNIVERSAL RAZOR RESISTORS.** Finished in bakelite case, 2-pin mains connectors, suitable for practically every type of electric razor. Drops voltage from 200/250 v. to 100/110 v. 10/6.

### ALL-WAVE SIGNAL GENERATOR

A.C. Mains 200/250 v. 50 cycle. Range covers from 20 M.C. to 100 K.C., all fundamentality in 5 bands without gears, 5/1M dial direct calibration in frequencies. Coarse and fine output attenuator. Internal modulation 400 C/S. Iron-cored coils. The generator is entirely screened in heavy metal cabinet with carrying handle. Dim., 10" x 10" x 12". Each **£13 10 0**

### REVOLUTION COUNTERS

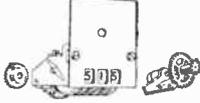

0-999 WITH GEAR DRIVE AND GEARS, **3/6**

**N.B.** Owing to depleted staff, we can only accept Cash with order. No C.O.D. Delivery 14 days.

◆ **CALLERS** to Show Rooms, **2 HIGHGATE HIGH ST., N.6.**

## LINAGLOW LIMITED

**HOURS OF BUSINESS:** Mon. to Fri. 9 a.m. to 5.30 p.m.  
Nearest Tube—Archway

◆ **POST ORDERS** to Dept. M.O.36 **61 HIGHGATE HIGH STREET, N.6.**

\*Phone: MOUNtview 9432

# Varley

## TRANSFORMERS and CHOKES For RELIABILITY

SEND US YOUR ENQUIRIES

### OLIVER PELL CONTROL LTD

CAMBRIDGE ROW, BURRAGE ROAD, WOOLWICH, LONDON S.E.


I am the c.g.s. unit of energy—you'll find me in every radio circuit.

**HULLO. -I'M AN ERG!**

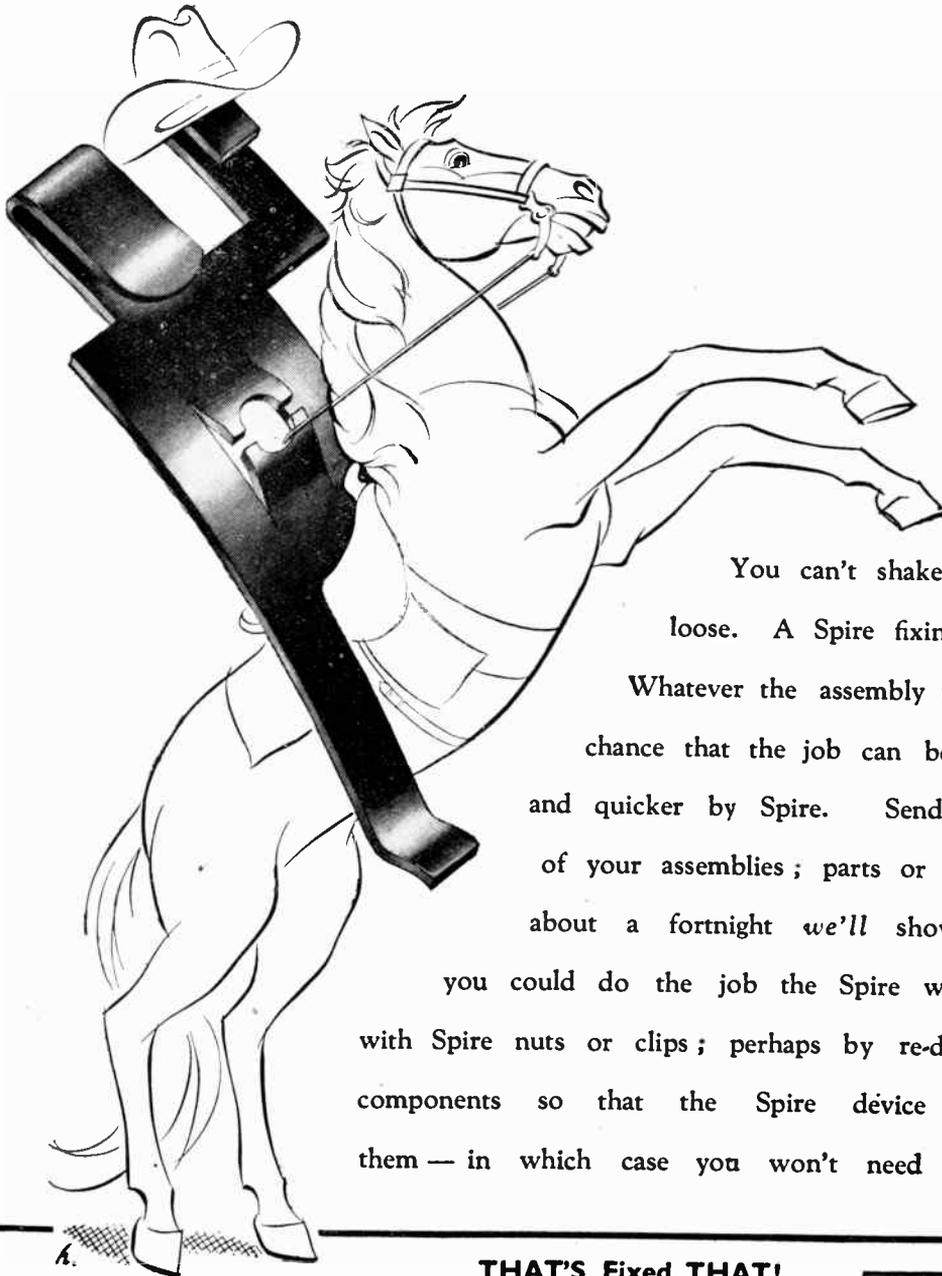**ERG**

ERG is the trade mark that will identify our products of quality—small parts for big jobs.

**ERG RESISTORS LTD.**  
1021a, FINCHLEY ROAD, LONDON, N.W.11. PHONE: SPEEDWELL 6867



You can't shake a Spire Nut loose. A Spire fixing locks itself. Whatever the assembly there's a good chance that the job can be done better and quicker by Spire. Send us examples of your assemblies; parts or drawings. In about a fortnight we'll show you how you could do the job the Spire way — perhaps with Spire nuts or clips; perhaps by re-designing your components so that the Spire device is part of them — in which case you won't need nuts at all.

### THAT'S Fixed THAT!

This is a typical case of intelligent use of Spire fixing. This was originally a spring clamp which was screwed to its base with screw, washer and nut. Now the clamp is redesigned to incorporate its own Spire fixing, and the nut and washer have disappeared. Apart from the saving in material it is a much quicker and simpler assembly job, the clamp is 'zipped' on to the screw and tightened firmly home. Designed as a fuse holder this fixing NS 1307 is suitable also for securing any cable, rod or circular equipment from  $\frac{1}{4}$ " to  $\frac{1}{2}$ " diameter.



# Spire

**\* A BETTER way of fixing**

Simmonds Aerocessories Limited · Great West Road · London · A Company of the Simmonds Group

# Wireless World

Proprietors :  
ILIFFE & SONS LTD.

Managing Editor :  
HUGH S. POCOCK,  
M.I.E.E.

Editor :  
H. F. SMITH

Editorial, Advertising  
and Publishing Offices :

DORSET HOUSE,  
STAMFORD STREET,  
LONDON, S.E.1.

Telephone :  
Waterloo 3333 (35 lines).

Telegrams :  
"Ethaworld, Sedist, London."



PUBLISHED  
MONTHLY

Price : 1/6

(Publication date 26th  
of preceding month)

Subscription Rate :  
Home and Abroad  
20/- per annum.

Radio and Electronics

34th YEAR OF PUBLICATION

MARCH 1945

MONTHLY COMMENTARY .. .. .	65
RADIOLOCATION.	
II.—History of its Development	
By Dr. R. L. Smith-Rose .. .. .	66
A NEW VERSATILE TONE CONTROL CIRCUIT	
By G. N. Patchett .. .. .	71
CATHODE BIAS IN PUSH-PULL STAGES	
By W. T. Cocking .. .. .	75
RAILWAY COMMUNICATIONS .. .. .	79
SUNSPOT MINIMUM YEAR	
By T. W. Bennington .. .. .	81
FREQUENCY CONTROL IN RADIO HEATING	
TEACHING MATHEMATICS	
By J. J. Durack .. .. .	83
RADIO DATA CHARTS—18	
Transmission and Phase Shift of RC Couplings	
By J. McG. Sowerby .. .. .	84
UNBIASED. By Free Grid .. .. .	86
WORLD OF WIRELESS .. .. .	88
LETTERS TO THE EDITOR .. .. .	91
RANDOM RADIATIONS	
By "Diallist" .. .. .	93
RECENT INVENTIONS .. .. .	96

Branch Offices :

COVENTRY :  
8-10, Corporation Street,  
Telephone : Coventry 5210.  
Telegrams :  
"Autocar, Coventry."

BIRMINGHAM :  
Guildhall Buildings,  
Navigation Street, 2.  
Telephone :  
Midland 2971 (5 lines).  
Telegrams :  
"Autopress, Birmingham."

MANCHESTER :  
260, Deansgate, 3.  
Telephone :  
Blackfriars 4412 (4 lines).  
Telegrams :  
"Iliffe, Manchester."

GLASGOW :  
26B, Renfield Street, C.2.  
Telephone : Central 4857.  
Telegrams : "Iliffe, Glasgow."



*As many of the circuits and apparatus described in these pages are covered by patents, readers are advised, before making use of them, to satisfy themselves that they would not be infringing patents.*


## "HYPERLOY"

### TRANSFORMERS AND CHOKES

A range of High-performance, space-saving Components designed to meet the most exacting requirements of modern Electronic and Communications equipments.


- Small in size
- Weighing only 2 oz.
- Meeting the most rigid Tropical Specification
- Easily mounted in any position
- Manufactured in a variety of windings to meet many diverse applications

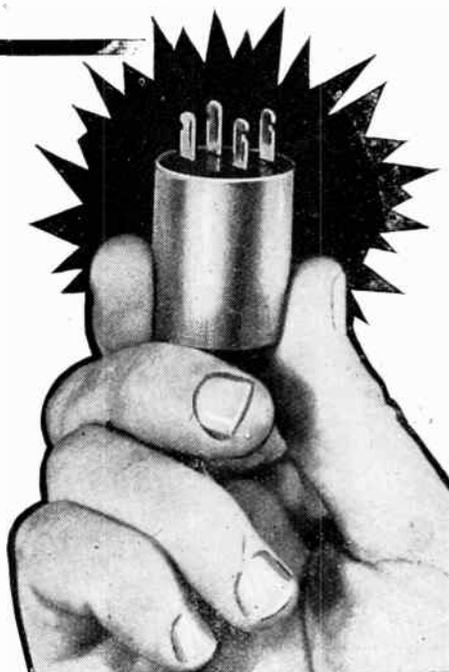★ Owing to wartime restrictions on supply of raw materials, it is not possible to supply Wearlite Components for purposes other than those connected directly with the war effort.




**WRIGHT & WEAIRE, LIMITED**  
HIGH ROAD, TOTTENHAM, LONDON, N.17 — Telephone: TOTTENHAM 3847-8-9

**MULLARD**

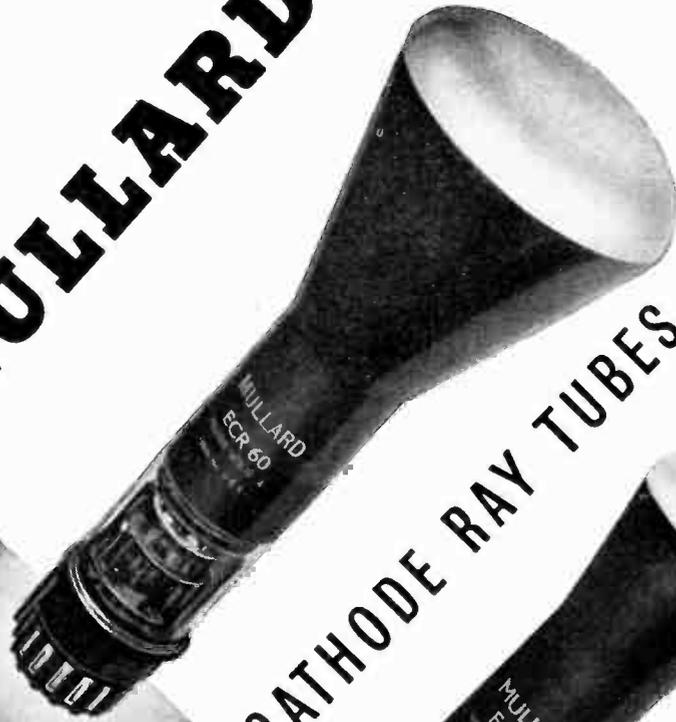

**CATHODE RAY TUBES**

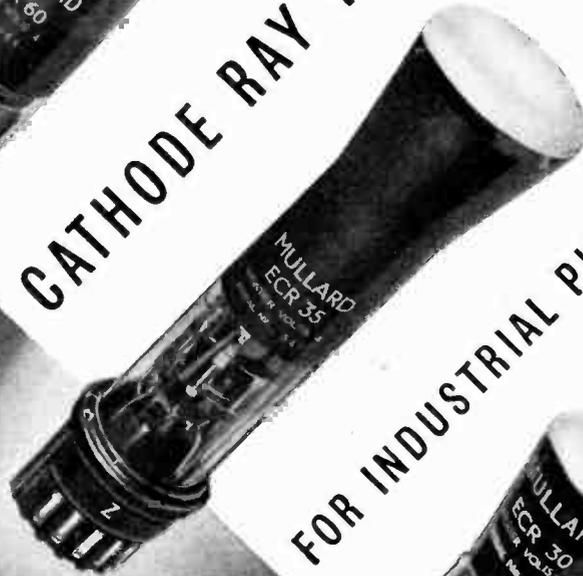

**FOR INDUSTRIAL PURPOSES**



TYPE	SCREEN DIAMETER	LIST PRICE
ECR. 60	6"	£7. 7. 0
ECR. 35	3½"	£6. 6. 0
ECR. 30	3"	£3. 3. 0

THE MULLARD WIRELESS SERVICE COMPANY LIMITED, CENTURY HOUSE, SHAFTESBURY AVENUE, W.C.2

(118)

# Wireless World

Radio and Electronics

Vol. LI. No. 3

MARCH 1945

Price 1s. 6d.

## Monthly Commentary

### Origins of Radiolocation

An article published elsewhere in this issue will, it is hoped, serve something more than its primary purpose of giving a simple account of the historical development of radiolocation. It should serve to emphasise the futility—or worse—of indulging in undignified wrangling over national priority in matters of scientific development and invention. Science tends ever to become more international, and developments are to an ever increasing extent built upon the foundations laid by workers of many lands. No longer does an important “invention” emerge fully fledged as an individual production.

Broadly speaking, that has been true throughout the whole half-century of radio. Readers may remember that, when its earliest history was debated in our columns a year or so ago, it was concluded that, building on the foundations laid by a German Jew working on the theoretical predictions of a Scotsman, the next significant steps in recognising and establishing electro-magnetic waves as a means of communication were taken by a German, a Russian, a Hungarian-American, an Englishman and an Irish-Italian. With a parent of such mixed descent, it is hardly likely that radiolocation, the offspring of radio, should be able to sustain claims for that racial purity so beloved of the *Herrenvolk*.

The initial ideas and also some of the technique of radiolocation were undoubtedly derived from methods of ionosphere research developed in England and the United States some twenty years ago. The principle of making use of reflections, thus established, was carried a stage further by employing it in U.S.A. for aircraft altitude indicators. The French “obstacle locator” was the first true “radiocator” to be described publicly, but at the same time work was proceeding in this country on aircraft locators working on the reflected wave principle. To stern necessity, in the shape of threatened war, must be ascribed the fact that we had a working system of radiolocation ready to meet the onslaughts of the *Luftwaffe*.

Just as radio development in general has been largely an international affair, so important single

developments tend increasingly to become a matter of properly co-ordinated team-work. As Dr. Smith-Rose points out in his article in this issue, practical radiolocation came into being as a result of a carefully planned programme of research devised by the Radio Research Board rather than as the invention of any one or more individuals. Here we have a good example of the importance of fundamental research, conducted for no obvious or immediate gain. From it came the scientific basis of radiolocation as an unexpected bonus.

◆ ◆ ◆

### The Radio Industry Council

It is a hopeful augury for the future that the Radio Industry Council, at its recent formal inauguration, celebrated the event by publicly drawing attention to the wartime achievements of the industry that it represents. Wireless is news to the British public, which is always ready to take an intelligent interest in the doings of the industry. Unfortunately, there has in the past been a lamentable failure to take advantage of this fact. Well-informed public opinion is worth cultivating, and this will doubtless become an important function of the R.I.C. By its constitution, the R.I.C. is essentially a federating council for co-ordinating the interests of the four independent associations that it represents. These bodies, which between them cover manufacturing activities in all wireless and electronic fields, are The British Radio Equipment Manufacturers' Association, The British Radio Valve Manufacturers' Association, The Radio Component Manufacturers' Federation and The Radio Communication and Electronic Engineering Association.

At the inaugural luncheon some of the more spectacular wartime achievements of radio, including the dramatic part played by radiolocation at the Battle of Matapan, were made public for the first time. These achievements are enumerated on another page.

In the difficult years that lie ahead the tasks of the R.I.C. are likely to be arduous and exacting. But it has made a good start, and we wish it well.

# RADIOLOCATION

## II.—History of its Development

**T**HE possibilities of devising some method of detecting solid objects with the view of avoiding collisions at sea was probably in the minds of many people immediately after the tragic disaster to the liner *Titanic*, which steamed at high speed into an iceberg while crossing the Atlantic on her maiden voyage in April, 1912. After this date there were doubtless many inventions of so-called "iceberg detectors," some of which depended upon the aural detection of an echo resulting from sounds emitted from a horn, siren or other source on board the ship. Echo-sounding devices based on this principle have been described during the past twenty-five years or more, and have been developed to a high degree for depth sounding at sea and submarine detection purposes. It is not proposed to divert our attention here to this sphere of development, but to restrict our consideration to the use of electro-magnetic waves, albeit to those of wavelength corresponding to a radio frequency rather than in the visual portion of the spectrum.

**Radio Waves for Exploring the Ionosphere.** — The first applications of radio waves for determining the distance of a reflecting surface were devoted to demonstrating the existence of the Heaviside layer as a portion of the upper atmosphere, now known as the ionosphere, which is responsible for the transmission of waves around the earth. After many years of speculation with a variety of indirect experimental evidence, the first direct demonstration of the existence of the ionosphere as a reflecting region was provided by Dr. (now Sir Edward) Appleton and M. A. F. Barnett towards the end of 1924 and during 1925.<sup>2</sup>

With the co-operation of the British Broadcasting Corporation the wavelength of the Bournemouth broadcasting station was varied over the range 385 to 395

By R. L. SMITH-ROSE,

D.Sc., Ph.D., M.I.E.E., F.I.R.E.

(National Physical Laboratory)


metres over a period of from 10 to 30 seconds, and the strength of the resulting signals at Oxford, about 100 miles distant, was measured. It was found that as the wavelength was varied, the received signal passed through a series of interference maxima and minima, indicating that the signal was the result of two sets of waves arriving by different paths; one set of waves was transmitted along the ground, while the other arrived by an indirect path after reflection from a layer. After verifying that the paths were in the same vertical plane, a measurement of the number of interference fringes caused by a known change in wavelength gave a measure of the height of the reflecting layer in the region, which later became known as the ionosphere.

This was the first classical

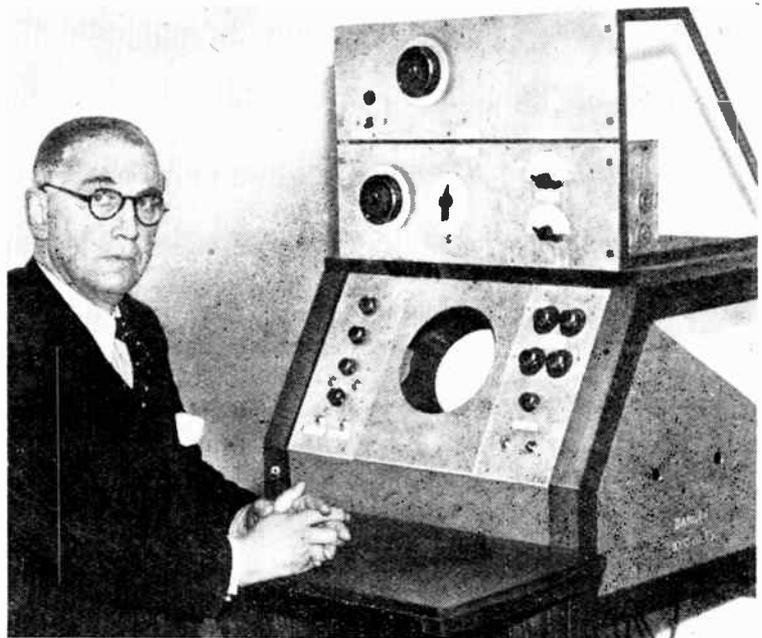example of the use of frequency-modulated radio waves for determining the existence and location of a reflecting layer which had hitherto remained undetected by any direct experiment. We may therefore say that the Heaviside layer was the first object to be detected by radiolocation experiments conducted by British scientists working under our own Radio Research Board, and assisted by the British Broadcasting Corporation.

Shortly after the first of the above measurements were made, G. Breit and M. A. Tuve<sup>3</sup> began some tests in the United States of America, using interrupted continuous waves which were the equivalent of pulses of continuous waves about 1 millisecond in duration and with a recurrence frequency of 500 per second. At the receiving station a high-speed oscillograph was used to record the incoming signals and permit the examination of their waveform. In July, 1925, experiments

<sup>3</sup> *Nature*, 1925, Vol. 116, p. 357.



Sir Edward Appleton, discoverer of the Appleton Layer and a pioneer of radiolocation.

<sup>2</sup> *Proc. Roy. Soc. A*, 1925, Vol. 109, p. 621.

were made over a distance of 7 miles using wavelengths of 71 and 42 metres, and it was observed that the received pulses, nominally of square wave-form, were distorted by the attachment of humps, sometimes in duplicate. These humps clearly indicated the arrival of a second wave-train, or echo, by an indirect path; and from a measurement of its time retardation in relation to the original hump due to the direct or ground wave, the path differ-

mentioned above, a considerable amount of research work was devoted to the development and use of methods of determining the height of the reflecting layers of the ionosphere, using both the frequency-change and pulse-modulation methods. A direct comparison of the two methods showed that they gave substantially the same result in height determination; and in a paper published in 1931, E. V. Appleton and G. Builder<sup>5</sup> described cer-

waves to the E region of the ionosphere and back again is of the order of 0.002 second, it is clear that using pulses of the type just described, first the ground-wave pulse will be all over before the arrival of the first echo, and secondly, that there is ample interval between successive ground-wave pulses to receive and record one or more echoes. For visually observing, and subsequently photographing, the nature of the received signals, a cathode-ray oscillograph was used, with a time-base provided from a similar basic circuit using a squegging oscillator, the stroke-frequency of the time-base being synchronised with the pulse recurrence frequency of the sender, so that a stationary image on the oscillograph screen was produced showing the ground wave and any echo waves received.

The type of result obtained is shown in Fig. 8 (a), (b) and (c) which are reproduced from the paper referred to above, and are specimens of the actual records obtained by Appleton and Builder in 1931. Fig. 8 (a) shows the ground-wave pulses received without echoes, while Fig. 8 (b) shows the presence of a single echo signal after reflection from the E<sub>1</sub> layer. In this case the time interval can be measured in terms of the trace of an alternating current

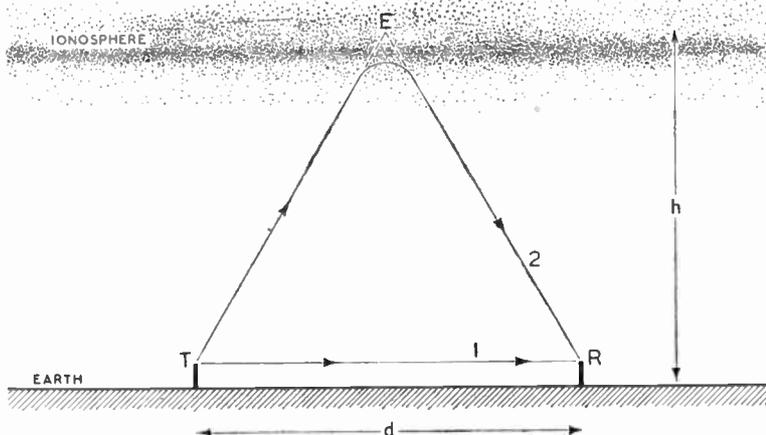


Fig. 7. Principle of technique used in determining height of reflecting regions in the ionosphere. Two sets of waves, 1 and 2, reach the receiver R from the transmitter T, along TR and TER respectively. From the difference in time of arrival, the path difference of these sets of waves, and so the height of the region E, can be determined.

ence of the two sets of waves could be determined. (See Fig. 7.)

In one of their publications, Breit and Tuve remark that their experiments on the above lines arose out of some work being carried out at the time on another method proposed by W. E. G. Swann and J. G. Frayne. It is also of interest to remark here that a United States patent was issued to H. Löwy<sup>4</sup> on an application filed in July, 1923, for a radio-frequency counterpart of Fizeau's method of determining the distance of a reflector, to which reference has already been made. In this patent Löwy describes an electronic switch used for alternately keying a transmitter and receiver, so that the latter is only in a sensitive condition after the pulse or train of waves has been emitted by the transmitter. It is not known whether this device was put to any practical use.

tain important improvements in sending and recording technique which demonstrated the advantages and illustrated the possibilities of the pulse method, in so far as the signals arriving at the receiver due to the ground wave and successive reflected echoes could be separately received and recorded. At the sending station a valve oscillator arrangement was used in the well-known "squegging" condition to produce trains of oscillations or pulses of a duration of about 100 microseconds, spaced in time 0.02 second apart; i.e., at a recurrence frequency of 50 per second. This type of oscillator had been used previously to give a linear time base for cathode-ray oscillographic delineation of wave-form by E. V. Appleton, R. A. Watson Watt, and J. F. Herd,<sup>6</sup> and its application to ionospheric recording had been suggested by Appleton in 1928.<sup>7</sup>

Since the time of transit of the



"This important and by no means easy step (application of the principle of using radio waves reflected from aircraft for detection and location) was accomplished by a small group of British scientists working under the direction of Mr. (now Sir Robert) Watson Watt."


**Later Ionosphere Researches.**—  
In the years following the dates  
U.S. Patent, 1,585,591—July, 1923.

<sup>4</sup> *Proc. Phys. Soc.*, 1932, Vol. 44, p. 76.  
<sup>5</sup> *Proc. Roy. Soc. A.*, 1926, Vol. 111, p. 672.  
<sup>7</sup> *Proc. Phys. Soc.*, 1928, Vol. 41, p. 49.

**Radiolocation—**

of frequency 1115 cycles per second shown below the signal record. Fig. 8 (c) is a snap photograph of the echo pattern on the cathode-ray tube, showing the ground wave G and the F region echo delineated on a time-base,

Fig. 8. (a) Record showing ground pulses only, and timing oscillation of frequency 1110 c/s. (b) Record showing ground pulses and echo received from F region about 3 milliseconds later. (c) Actual photograph of the ground wave and echo pattern as observed on the cathode-ray oscillograph screen. These records are reproduced from a paper by E. V. Appleton and G. Builder published in *Proc. Phys. Soc.*, 1932, Vol. 44, p. 82.

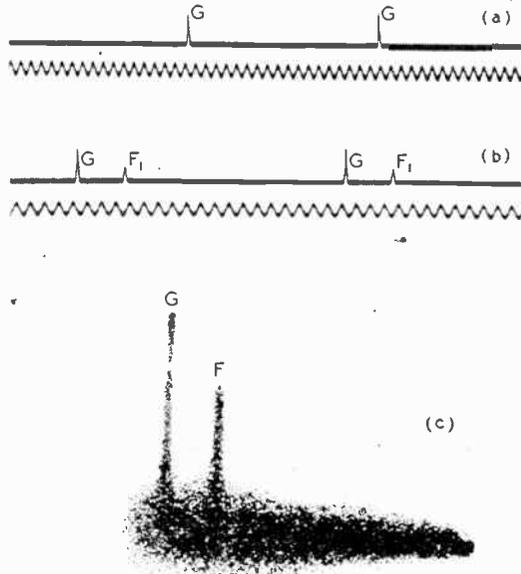

which in this case corresponds to a period of about 12 milliseconds. This was probably the first published picture of what is seen on the screen of the cathode-ray tube of a sending and receiving system used for determining range by measuring the time delay of the echo signal relative to that of the ground or direct path signal. The pulse-generating oscillator, and the cathode-ray tube and linear time-base combination so described by Appleton and Builder in 1931, formed the basis of the technique used some four years later in the first Radar experiments on aircraft detection conducted in this country.

**Aircraft Altitude Indicators.—**

While scientific research on methods of exploring the ionosphere was being conducted on the lines described above, a corresponding technique was being developed concurrently and on very similar lines for the purpose of producing an instrument for indicating the height of an aircraft in flight above the ground. For

example, in 1928 J. O. Bentley<sup>8</sup> described a method in which frequency-modulated waves are radiated towards the earth from a transmitter on the aircraft. A receiver, also on the aircraft, receives the waves after reflection from the ground and combines

them with those received direct from the transmitter, the latter waves differing slightly in frequency due to the time of travel of the waves to the ground and back again. The frequency of the beats in the receiver resulting from the two sets of waves is thus a measure of the height of the aircraft above the ground beneath, as distinct from its altitude above sea-level, which is what is indicated by the type of altimeter dependent upon barometric pressure. This instrumental technique was later improved by L. Espenschied<sup>9</sup> in 1930, and culminated in a commercial pattern of "terrain clearance indicator" produced by the Bell Telephone Laboratories in 1938. The apparent delay in the successful production of this instrument was due to the fact that the heights in question are much smaller than those involved in ionospheric research; and that therefore the echo-time intervals to be measured are correspondingly less; e.g., 10 microseconds for about

5,000ft. An illustrated description of this method of echo sounding for aircraft was given in *Wireless World* for February 2nd, 1939.

The pulse modulation method of altitude determination in aircraft is clearly applicable, provided that the pulse lengths are reduced sufficiently to discriminate the echoes arriving at a much shorter time delay than is the case of the ionospheric work. Such a system was, in fact, described by the Submarine Signal Company in June, 1933.<sup>10</sup> Here the scheme proposed for measuring distances used pulses of electric waves, in association with a means of receiving the reflected echoes, and determining the time interval between the emitted and received pulses with the aid of a cathode-ray tube and synchronised time-base.

**The Origin of True Radar.—**

The above section described the use of methods of measuring the time delay in transit of reflected radio waves for determining the distance of large surfaces, such as the ground or ionosphere. In contemplating the possibilities of determining the distance of smaller objects such as ships or aircraft, consideration must be given to the reflecting properties of bodies which are not large and may even be smaller than the length of the waves used. With light waves, this question does not arise except in the case of detecting objects of microscopic dimensions, the length of the waves being of the order of a few hundred-thousandths of a centimetre; but with radio waves the dimensions of the object from which reflection is desired may be comparable and even smaller than the wavelength used. Although the classical laws of reflection enunciated by Fresnel and verified experimentally in the case of optical phenomena, were equally applicable to the longer electric waves in the radio-frequency portion of the spectrum, there was still lacking at the beginning of the 1930 decade a satisfactory practical demonstration that the reflection or scattering of radio waves from an object such as a ship or aircraft was of a sufficiently high order to be detectable.

For this reason, it is interesting and important to record that in December, 1931, the British Post

<sup>8</sup> U.S. Patent 2,011,392—August, 1928.

<sup>9</sup> U.S. Patent 2,045,071—April, 1930.

<sup>10</sup> British Patent 406,903—June, 1933.

Office<sup>11</sup> observed the effects of reflection of waves from aircraft in the course of some radio communication tests being conducted on a wavelength of 5 metres over a path 12 miles long. Extracts from the station log show that on various occasions the received signal was subject to a beat type of variation, which was not only audible but was detectable on the volume indicator of the receiver. The amplitude of the beat varied from about  $\pm \frac{1}{2}$  db. up to 10 db. on some occasions, and at all times when this occurred an aircraft was found to be flying in the neighbourhood at various distances up to  $2\frac{1}{2}$  miles and at heights up to 500ft. The period of the beats varied from 5 to 15 per second; and this is to be compared with the calculated value of 11 per second for an aircraft flying directly towards the receiving aerial at a speed of 60 m.p.h.

This experience was confirmed by further observations made in America in 1932 by engineers of the Bell Telephone Laboratories in the course of an investigation of the mode of propagation of radio waves in the range of wavelengths between 4.7 and 5.7 metres. In a paper<sup>12</sup> describing this work by Messrs. C. R. Englund, A. B. Crawford and W. W. Mumford, and published in March, 1933, it is stated that an aircraft flying about 1,500ft. overhead and approximately along the line joining transmitter and receiver, a noticeable flutter of about four cycles per second was produced in the low-frequency detector meter of the receiver. When observations were carried out in the neighbourhood of an airport, it was noticed that near-by aircraft produced field strength variations up to 2 db. in amplitude. Similar re-radiation was noticed at various subsequent times, occasionally when the aircraft was invisible.

It was thus clearly established, over ten years ago, that radio waves reflected from aircraft in flight could be detected with suitable receiving equipment on the ground; and it now remained to be seen whether this principle could be applied to the development of a technique for the detection and location of aircraft at ranges and under conditions of

practical utility as an aid to navigation in peacetime and as a defensive weapon in war. This important, and by no means easy, step was accomplished by a small group of British scientists working under the direction of Mr. (now Sir Robert) Watson Watt, who was at the time Superintendent of the Radio Department of the National Physical Laboratory, incorporating the Radio Research Station at Slough where the initial experiments in the radio location of artificial objects in this country were conducted.

Under the auspices of the Radio Research Board, the Research Station had been responsible for a wide variety of investigation work on the propagation of waves, the study of atmospheric and of direction-finding, and Watson Watt and his colleagues brought all the resources of this work and the resulting technique to bear on the problem of making the radiolocation of artificial objects a practical and worthwhile proposition. In association with Appleton, he had been responsible for much of the application of the cathode-ray tube as a research tool for delineating the wave-form of atmospheric; Watson Watt, in association with the late J. F. Herd,<sup>13</sup> had also devised the original form of visual direction finder, using twin balanced amplifiers and a cathode-ray indicator.

The staff which had developed these techniques, supplemented by those who had converted Appleton's technique for ionospheric exploration into a routine recording equipment, were in a unique position to demonstrate the possibilities of aircraft detection and location by radio methods. Prominent among the members of the staff of the Radio Research Station who were responsible for the technical requirements of this early work were L. H. Bainbridge Bell who undertook a great deal of apparatus design and development at Slough and Drs. E. G. Bowen and A. F. Wilkins, who worked very successfully on the special problems associated with the transmitting and receiving equipment respectively.

After some preliminary experiments, these and other members of the staff under Watson Watt's

supervision established a new "ionospheric" exploring station on the East Coast of England, at which were installed the, for those days, high-power pulse transmitters made at Slough, together with suitable receivers and appropriate aerial systems and goniometers for determining the direction of arrival of the echo waves, both in azimuth and elevation, scattered back to the receiver from the aircraft which was illuminated, as it were, by the flood-lighting effect of the radiation from the transmitter.

Thus it was that in the early days of 1935-36, the technique of radiolocation of artificial objects was born in this country, and the members of that small band of scientists and technical assistants will well remember the thrill of seeing for the first time a clear image on the cathode-ray tube due to an aircraft which was so far away as to be invisible to the naked eye; the distance of the pip along the base line gave the range of the aircraft while its bearing and elevation were obtainable by turning the knobs of the goniometers.

Much hard work and not a little ingenuity were still required to convert the technique from an experiment in the hands of scientists to a working system which could be used and maintained by this miscellaneous type of personnel which was at that time provided by the Service departments for this new "side-line" of radio communication or signalling. It was not long, however, and well before war was declared, before more than one Service station was in operation, and the plotting of the tracks of various aircraft, some on their legitimate civil or military duties, and others whose business was perhaps less innocent, was a matter of daily routine.

**The Radio Research Board.**—The foregoing paragraphs have explained in a skeleton manner how radiolocation came about in this country, as a practical application of the combined techniques devised originally for the scientific exploration of the ionosphere and for direction-finding. All these investigations were in progress for nearly twenty years before the present war under the auspices of the Radio Research

<sup>11</sup> Radio Report No. 223, 3rd June, 1932, Part V.

<sup>12</sup> Proc. I.R.E., 1933, Vol. 21, p. 475.

<sup>13</sup> Journal I.E.E., 1926 (Proc. Wireless Section) vol. 1, p. 89).

**Radiolocation—**

Board, and the story here told provides an outstanding example of the manner in which a carefully planned programme of research on a broad national basis will in the long run yield results of immeasurable value. It will thus be appreciated that Radar came about in this country as a synthesis of knowledge and experience obtained in the course of scientific investigations and effectively applied to a practical issue, rather than as an invention by any one or more individuals to meet a specific demand.

This aspect of the whole subject was emphasised in the course of a speech made in July, 1943, on "Radio Research and Production Before, During and After the War." G. M. Garro-Jones, Parliamentary Secretary to the Ministry of Production, paid the following tribute to those responsible for this pioneer work in modern radio research.<sup>14</sup>

"In the decade 1925-35 the State contribution came through the Radio Research Board of the Department of Scientific and Industrial Research, in full activity on a programme of work which largely centred on the effects of atmospheric processes on radio. The Board and the National Physical Laboratory also did great things in an active programme of measurement and standards work. . . . Radiolocation, by far the most important national asset ever to emerge from the National Physical Laboratory, was a natural but not inevitable synthesis of techniques developed within the Radio Research Board's programme. It revived the laboratories of the defence services. . . . There is little need to emphasise the tremendous value of radio devices in the present war and the great part that the radio industry is playing in prosecuting the war to a successful conclusion. Radiolocation devices, radio navigational aids, and radio communication equipments have proved of unforgettable value when our very survival was in jeopardy, and are now proving of ever-growing value in offensive operations."

Having thus presented a review of the manner in which radar originated in this country, this article will conclude with a brief review of what appeared to be in

progress abroad during the same period.

**Work in Other Countries.**—An indication of the trend of thought and activities in other countries in the years before the outbreak of the present war can be gained from a perusal of one or two publications which are available. Reference has already been made to the patent taken out in U.S.A. by H. Löwy; but the main development in America seems to have taken place partly in the Service research institutions, and partly at the Bell Telephone Laboratories. The latter organisation, after developing the aircraft altimeter, demonstrated the use of this instrument in a modified form to the detection of ships over short distances.<sup>15</sup> With regard to the Continent, it is to be noted that the Telefunken Company filed a patent in 1935, disclosing an arrangement similar to the frequency-change method used by Appleton, with the modification also suggested by Appleton<sup>16</sup> that, while the carrier frequency remained unaltered, the frequency of the modulation was varied, while the number of interference fringes was counted at the receiver. The American journal *Electronics* published in September, 1935, a two-page set of illustrations descriptive of the aircraft detection arrangements alleged to be under development by the Telefunken Company. An interesting feature of this pictorial display was the reference to the use of wavelengths in the band 5 to 15 cm. and of magnetron valves with permanent magnets developed specially for wavelengths of about 10 cm. An alternative scheme was also described by the Telefunken Company in 1937,<sup>17</sup> which utilised two beams of transmitted waves to produce a stationary interference pattern, the disturbance of which by an object moving across it was detected at the receiver.

In Italy, E. Montu described a twin rotating aerial arrangement for locating aircraft in bearing and elevation, and the patent specification of this arrangement was published in this country in December, 1936.<sup>18</sup> About three years later U. Tiberio published the first part of a comprehensive paper,

discussing various aspects of the radiolocation of ships and aircraft, in the Italian periodical *Alta Frequenza*<sup>19</sup>: the later parts of the paper were apparently withheld from publication after the outbreak of war. An interesting development in France was the fitting of the steamship *Normandie* with an iceberg detector, which was described and illustrated in *Wireless World* for June 26, 1936. This equipment comprised a transmitter and receiver operating on a wavelength of 16 cm. and mounted in the fore part of the ship. The transmitting and receiving aeriels were of the dipole type and mounted in parabolic reflectors, 75 cm. in diameter and installed at a distance of 6 metres apart; this arrangement provided a beam having a width of  $\pm 10$  deg. at half amplitude, and the reflectors could be rotated automatically through an arc of 40 deg. When the receiver indicated the arrival of a signal from the transmitter after reflection from a distant object, the two parts of the equipment could be manually and accurately trained on this object, the distance of which could then be calculated from the directions of the transmitted and arriving waves. In this manner it was claimed that a coastline could be located at a distance of 20 km., and large ships at ranges up to about 7 km.

Such was the state of affairs abroad as judged by the sparse published information available. As to what was the actual state of affairs at the outbreak of the war in Europe must remain a matter of speculation at the present time; but many readers will look forward with interest to the time when more facts may be disclosed, and the progress of the Radar technique and operation conducted by the various belligerent nations may be described and compared.

<sup>19</sup> *Alta Frequenza*, 1939, Vol. 8, p. 305.

## OUR COVER

THIS month's illustration deals with one of the earliest practical devices for locating objects at a distance by means of reflected wireless waves. The photograph shows the transmitting and receiving reflectors of the "obstacle detector" installed by the Société Française Radio-Electrique aboard the liner *Normandie*.

<sup>14</sup> *Bell Laboratories Record*, June, 1943.

<sup>15</sup> *Proc. Phys. Soc.*, 1930, Vol. 42, p. 323.

<sup>16</sup> French Patent 809,612—August, 1936.

<sup>17</sup> British Patent 478,456—January, 1936.

<sup>14</sup> *Engineering*, Aug. 13, 1943, p. 135.

# A New Versatile TONE CONTROL CIRCUIT

## I.—Basic Principles of Tone Control

A LARGE number of tone control circuits have been published over the period of the last ten years (see references), all possessing some advantages and disadvantages. Many circuits are commonly used which, when turned to the maximum bass position just reduce the "top," their only redeeming feature being their simplicity and cheapness.

One requirement of any good tone control circuit is the ability to increase the treble or bass relative to the middle frequencies. In other words, if the bass tone control is turned in the "increase bass" direction, the amplitude of the lower frequencies will be increased relative to what they were originally, the middle and high frequencies remaining the same. A practical tone control circuit which achieves this object will be described in the second part of this article.

One point that is not always realised is that it is impossible to obtain an increase or boost of any frequency if the maximum gain of the amplifier is already being utilised. This means that in order to obtain an increase in the amplitude of the low or high frequencies it is necessary that the normal amplification should be less than the maximum by the amount of increase required.

By G. N. PATCHETT,

B.Sc., Grad.I.E.E., A.M.Inst.E.,  
Assoc. Brit.I.R.E.

This usually means that at least one extra valve is required for tone control.

Another point which is worth mentioning is that if bass or treble boost is used the output stage must be capable of handling

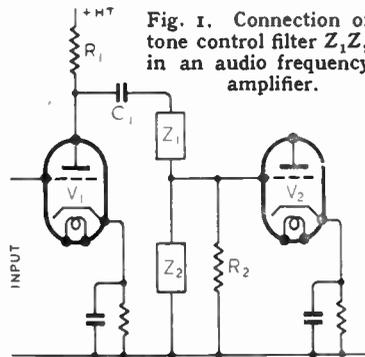


Fig. 1. Connection of tone control filter  $Z_1, Z_2$  in an audio frequency amplifier.

a much greater output than normal. For example, suppose that the normal output is one watt, then if the bass increase of only 3.2 times (10 db) is used the output stage will have to handle 10 watts at the low frequencies, since the power is proportional to the voltage squared.

We will begin by considering

the type of circuit consisting of a frequency discriminating filter or potential divider circuit, as this is by far the most versatile and successful so far employed. Fig. 1 shows the connection in an amplifier of a frequency discriminating filter, consisting of two impedances  $Z_1$  and  $Z_2$ , the impedance is at least one being dependent on frequency.  $R_1$  is the anode resistance of the valve  $V_1$ ,  $C_1$  is the DC blocking condenser and  $R_2$  the grid resistance of the valve  $V_2$ . The load on the valve  $V_1$  is not only the resistance  $R_1$ , but, neglecting the effect of the resistance  $R_2$  and the condenser  $C_1$ , the combined impedance of the resistance  $R_1$  and the impedance of the tone control filter  $Z_1 + Z_2$ , in parallel. In order to keep the distortion to a minimum the impedance of  $Z_1 + Z_2$  should be as high as possible. A limit to the impedance  $Z_2$  is fixed by the fact, that, in order to avoid alteration in the characteristic of the tone control filter, the value of the resistance  $R_2$  must be considerably greater than the impedance  $Z_2$ , a limit to the value of  $R_2$  being determined by the maximum grid-cathode resistance allowable for the valve  $V_2$ . Since the impedance of the tone control filter  $Z_1 + Z_2$  is usually smaller than the normal grid resistance used

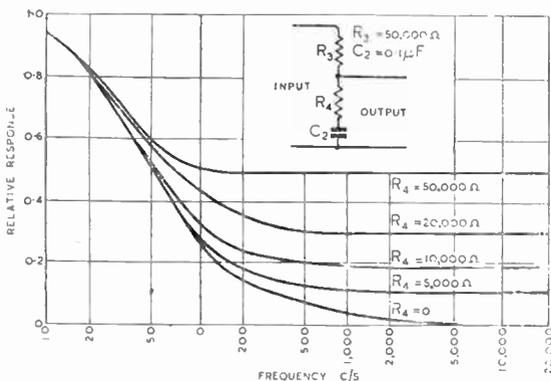


Fig. 2. Basic bass tone control filter showing the effect of varying the resistance  $R_4$ .

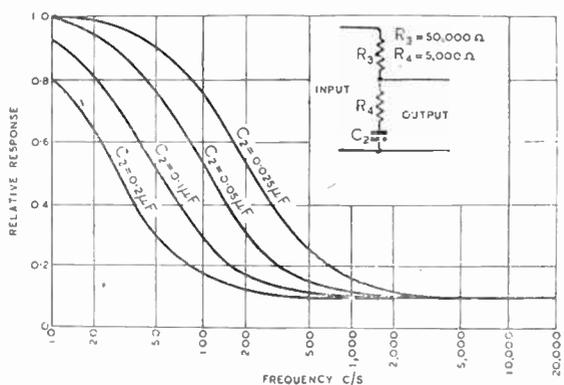


Fig. 3. Bass tone control filter showing the effect of varying the capacity of the condenser  $C_2$ .

**Tone Control Circuit—**

in resistance capacity coupling, the value of the condenser  $C_1$  must be increased so that its reactance at the lowest frequency is small compared with the impedance of  $Z_1 + Z_2$ , otherwise it will cause alteration in the frequency characteristic of the filter.

the lower portion of the tone control filter, which, in turn, increases the output/input ratio. Eventually a frequency is reached where the reactance of the condenser  $C_2$  is high compared with the resistance  $R_3$ , making the output equal to the input.

Considering the filter circuit alone, the maximum "gain" is unity (output = input). If therefore, a maximum increase of the

of increase at the low frequencies is now required. (Note, variation of  $R_4$  is not practical since this would cause a large change in volume.)

This may be achieved in one of three ways:—

(a) By variation of the capacity of the condenser  $C_2$ . The result of this is shown by the curves of Fig. 3. The arrangement has two disadvantages: first, the change can only be made in steps since the capacity of the condenser  $C_2$  cannot be reduced sufficiently to make it continuously variable, and, second, variation of the value of the condenser does not directly control the magnitude of the increase in the bass, but rather, the frequency at which the increase starts.

(b) By the use of a variable resistance  $R_5$  across the condenser  $C_2$ , as shown in the diagram of Fig. 4. The effect of the resistance across the condenser is to prevent the impedance of the lower portion of the network from increasing beyond that of the resistance  $R_5 + R_4$ . This method gives the continuous variation of the amount the low

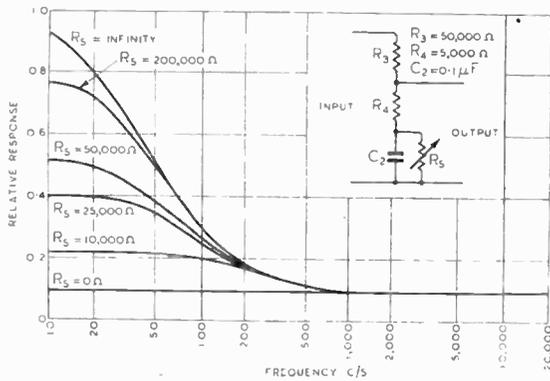


Fig. 4. Effect of varying the value of the resistance  $R_5$ .

**Bass Tone Control.**—A basic circuit for increasing the response in the base is shown in Fig. 2. At the middle frequencies where the reactance of the condenser  $C_2$  is small compared with the

bass of 10 times (20db) is required, the output at the middle frequencies must be reduced to 1/10 of the input, i.e.

$$\frac{R_4}{R_3 + R_4} = \frac{1}{10}$$

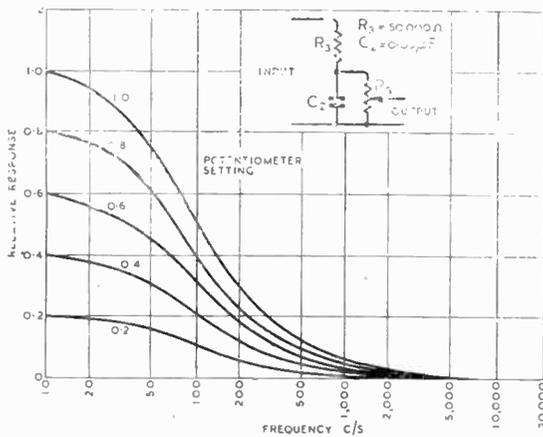


Fig. 5. Modified tone control filter, showing the effect of varying the setting of the potentiometer  $R_4$ .

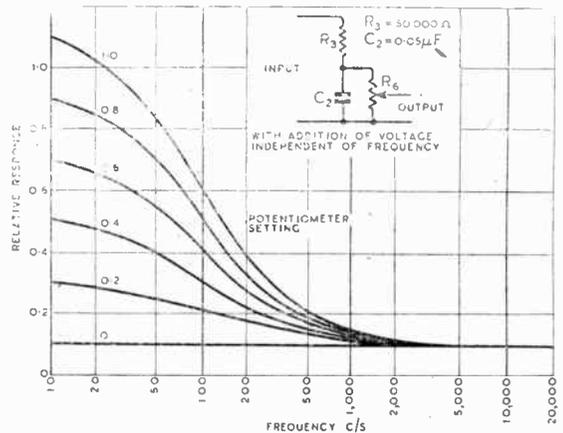


Fig. 6. Tone control filter as in Fig. 5 with the addition of a voltage independent of frequency and of amplitude equal to 1/10th of the maximum output of the filter.

resistance  $R_4$ , the ratio of the output voltage to the input voltage, is determined by the resistances  $R_3$  and  $R_4$  and given by the formula  $\frac{R_4}{R_3 + R_4}$ . As the frequency is decreased, the reactance of the condenser  $C_2$  increases, so increasing the impedance of

A suitable value for the resistance  $R_3$  is 50,000 ohms, making the resistance  $R_4 = 5,500$  ohms. Since great accuracy is not required, it is convenient to make the latter 5,000 ohms. The effect of varying the value of the resistance  $R_4$  is shown by the curves of Fig. 2. A method of varying the amount

frequencies are increased but has the disadvantage of altering the shape of the frequency-output characteristic of the filter, as seen by the curves of Fig. 4, calculated for various values of the resistance  $R_5$ , i.e. at the lower settings of the control, the magnitude of the increase is constant over a con-

siderable frequency range, rather than the more desirable increase in output as the frequency decreases.

method of obtaining the voltage independent of frequency and adding it to the output from  $R_6$  will be described later.

treble tone control by replacing the condenser  $C_2$  by an inductance. The effect of changing the inductance and the resistances

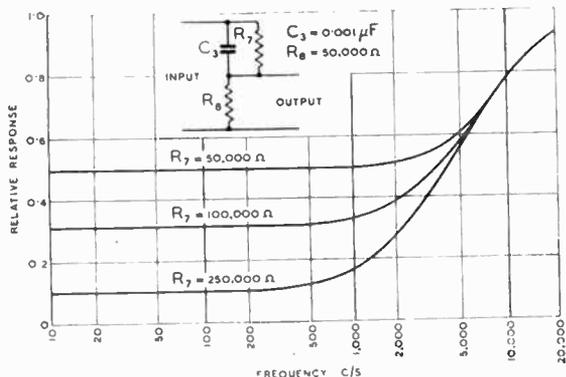


Fig. 7. Basic treble tone control filter showing the effect of varying the resistance  $R_7$ .

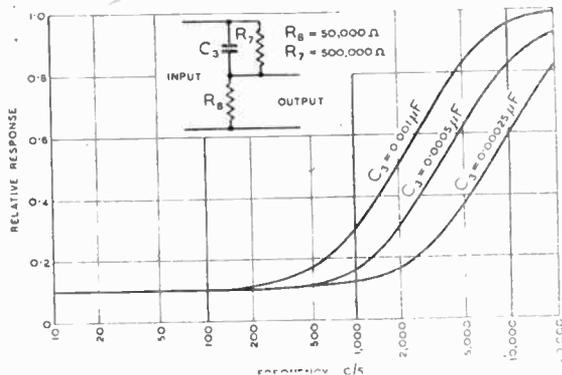


Fig. 8. Treble tone control filter showing the effect of varying the condenser  $C_3$ .

(c) A method devised by the author where the same shape of curve is produced at all settings of a continuously variable tone control. By omitting the resistance  $R_4$  and placing a high resistance "volume control"  $R_6$  across the condenser  $C_2$  as shown in the circuit of Fig. 5, the characteristics as shown in the same figure are obtained. If the output from the resistance  $R_6$  is added to a voltage independent of frequency, the characteristics as shown in Fig. 6 will be the result. The tone control  $R_6$  now gives a continuous variation in the magnitude of the increase at the low frequencies while having no effect on the shape of the curves. The

**Treble Tone Control.**—A similar circuit to that for the bass tone control may be used for

$R_3$  and  $R_4$  on the increase in the output at the high frequencies would be similar to the effect on the increase in the output of the low frequencies obtained by changing the condenser  $C_2$  and the resistances  $R_3$  and  $R_4$  of the

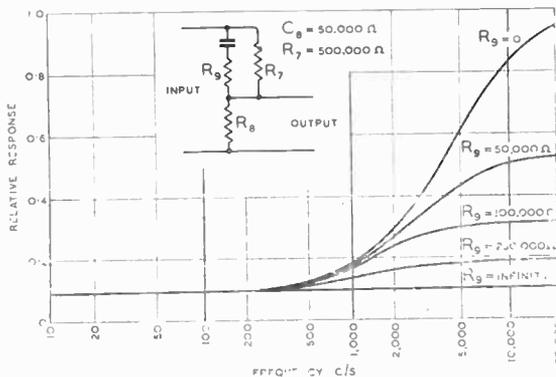


Fig. 9. Effect of varying the resistance  $R_9$  on the treble tone control filter.

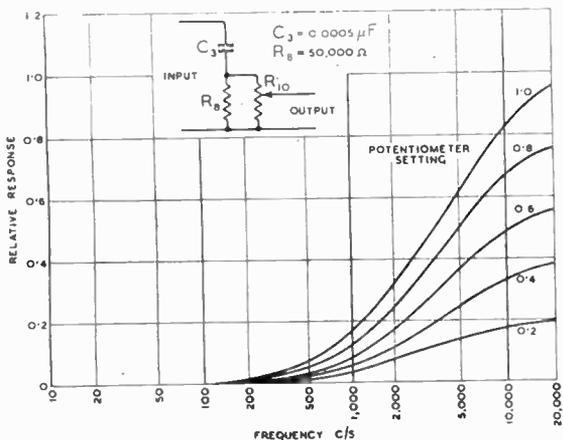


Fig. 10. Modified treble tone control filter showing the effect of varying the setting of the potentiometer  $R_{10}$ .

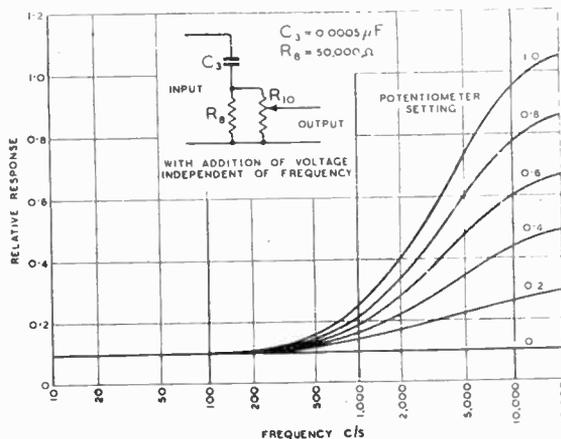


Fig. 11. Treble tone control filter of Fig. 10 with a constant voltage equal to 1/10th the maximum output of the filter.

**Tone Control Circuit—**

bass tone control just described. The use of an inductance has two disadvantages: an inductance of known value is not so easily obtained as a condenser or a resistance and there is always a tendency for the inductance to pick up hum. To avoid these difficulties a circuit using resistances and condensers only is used.

The basic circuit is shown in the diagram of Fig. 7. At middle frequencies, where the reactance of the condenser  $C_3$  is high compared with the resistance  $R_7$ , the two resistances  $R_7$  and  $R_8$  act as a potential divider, the ratio of output to input being  $\frac{R_8}{R_7 + R_8}$ .

Using a suitable value of 50,000 ohms for the resistance  $R_8$ , the effect of  $R_7$  is to determine the output at the middle frequencies and the result of varying  $R_7$  is shown by the curves of Fig. 7. The variation of  $R_7$  has a very similar, but opposite, effect to the variation of the resistance  $R_4$  of the bass tone control filter shown by the circuit of Fig. 2. Variation in the magnitude of the increase of the high frequencies may be obtained by one of three methods similar to those used in bass tone control.

(a) By the variation of the capacity of the condenser  $C_3$ . The effect of varying the capacity of the condenser  $C_3$  is shown by the curves of Fig. 8, where it will be noted that a direct control of the amount of treble increase is not obtained, but rather, the frequency at which the increase starts. A continuous variation can be obtained by using a  $0.0005\mu F$  two gang condenser for  $C_3$ , connecting the two sections in parallel to make a total of  $0.001\mu F$ , although this is rather clumsy.

(b) By the use of a variable resistance in series with the condenser  $C_3$ . If a variable resistance  $R_9$  is placed in series with the condenser  $C_3$  as shown by the diagram of Fig. 9. The impedance of the top portion of the network is prevented from becoming appreciably less than the value of the resistance  $R_9$ , i.e. the magnitude of the increase of the high frequencies is limited as seen by the curves of Fig. 9, calculated for different values of  $R_9$ . The effect of varying the

resistance  $R_9$  is similar, but opposite, to that of varying the resistance  $R_5$  of the bass tone control circuit shown in Fig. 4, and the method has the same disadvantage, i.e. alteration of the shape of the curves.

(c) A method similar to that described for the bass tone control circuit where a continuous control is obtained without altering the shape of the curves. By placing a "volume control"  $R_{10}$  across the resistance  $R_8$  (or making  $R_8$  the volume control) and removing  $R_7$ , as shown in the diagram of Fig. 10, the curves as shown in the same figure are obtained, for various settings of the control  $R_{10}$ . By adding the output from  $R_{10}$  to a voltage independent of frequency the results as shown in Fig. 11 are obtained.

**PARALLEL "R" AND SERIES "C" ON THE SLIDE RULE**

USERS of the ordinary 4-scale type of slide rule (i.e., without the reciprocal scale) will no doubt be interested in the following facts which are not generally known:—

To find the reciprocal of any number, all that is necessary is to reverse the slider and close up rule fully. Reciprocals of numbers appearing on scale "A" may now be read directly opposite on scale "B" (now upside down). By leaving slider in this position, it is now possible to calculate any combination of resistors in parallel—or condensers in series—without further movement of slider: the cursor only is required.

For, say, three resistors in parallel, proceed as follows: Set cursor to value of  $R_1$  on scale "A" and note corresponding number on scale "B." Repeat for  $R_2$  and  $R_3$  and add total of numbers on scale "B." Reset cursor to this total on scale "B" and the absolute resistance value appears opposite in scale "A."

After a little practice this will be found to be a much quicker method of calculation than the old formula and it reduces the operation to one of simple addition. This system may of course be used with equal ease for calculating the total capacity of any number of condensers in series, and the procedure is the same.

H. E. S.

**REORGANISING BROADCASTING**

VARIOUS schemes for the more or less drastic reorganisation of the B.B.C., whose Charter expires next year, have already been put forward. The latest proposals in this direction appear in a booklet\* published by the Arts Advisory Committee of the Communist Party. These proposals are summarised as:

(1) Constitution changes to turn the B.B.C. from a Royal monopoly into a public service under full Parliamentary control and to ensure that its administration is no longer carried on in secrecy.

(2) A decentralised organisation, made up of a number of autonomous regional broadcasting units, basing their work on the needs and interests of people in their area, and a national organisation designed to fulfil a new and more positive cultural rôle in various fields.

(3) The opening up of new channels of communication between broadcasting and the public, through new forms of advisory organisation which will draw in the audiences, the amateurs and the professional workers in various fields to co-operate in the making of programmes.

(4) A change in the status of broadcasting workers, which will give them full freedom to participate in the political and cultural life of the community, to discuss their work publicly, to mix with their audiences and with workers in other fields, and, if they wish, work outside broadcasting.

(5) More money.

Arguments for advertising broadcasting are examined and this system of financing programmes is emphatically condemned as "a political danger and a social evil."

\* "The B.B.C." pp. 24, 9d. net. The Communist Party, 16, King Street, London W.C. 2

**RE-STARTING TELEVISION**

SOME of the more spectacular contributions of radio to the war effort, revealed for the first time at the Radio Industry Council's recent formal inauguration, are enumerated on page 87. In addition, it was disclosed that the R.I.C. has submitted to the Hankey Committee a proposal for restarting British television on pre-war standards as soon as the German war ends. At the same time, work should start on a system for distributing television over the whole country by radio links. This was the method of distribution envisaged by the industry before the outbreak of war.

# CATHODE BIAS IN PUSH-PULL STAGES

## Is a By-pass Condenser Necessary?

By W. T. COCKING,  
A.M.I.E.E.

**D**OUBT is frequently expressed about the need for using a by-pass condenser across the cathode-bias resistance of a push-pull stage when this resistance is common to both valves. Text-books are usually silent on the subject and, in the rare cases when they do refer to it, are apt to conflict in their advice.


An exact analysis of the effect of omitting the condenser is quite easy to carry out if the valves are assumed to have completely linear characteristics. While such an analysis helps to an understanding of the action of the bias resistance, it is by no means sufficient. One of the chief characteristics of a push-pull amplifier is its ability to give an undistorted output when the valves are individually non-linear. It is, therefore, of the first importance not to restrict the investigation to the linear condition.

A complete analysis in the non-linear condition is impracticably complicated, however, but useful information can be obtained quite readily by investigating the circuit from two different points of view. An analysis based on the assumption of linear valves will reveal the effect of the cathode resistance on the balance of the stage when the two sides are somewhat dissimilar—as they usually are in practice. A further analysis, carried out for identity between the two sides, will show the effect of the cathode resistance on distortion when the valves are not linear.

From these two results a very good idea can be obtained of what happens when the valves are not only non-linear but the components on the two sides are not identical in value. It is true that this does not enable the exact performance to be calculated, but for the small degrees of distortion and the small amounts of unbalance that are normally permitted the approximation is sufficiently accurate for most purposes.

The effect of the cathode resistance on the balance of the stage will be considered first and it will be assumed that the two valves are each quite linear but not necessarily alike. A typical output stage is shown in Fig. 1, and the circuit is also identical with that of a transformer-coupled intermediate stage. In the latter case T would be an intervalve transformer and would have a centre-tapped secondary for feeding the next push-pull stage. The resistance  $R_L$  represents the output load circuit; in the case of an output stage it stands for the speaker impedance, whereas in an intermediate stage it represents the resistance shunting the secondary of the transformer.

Fig. 1. An equalising effect is obtained with  $R_c$  unshunted.

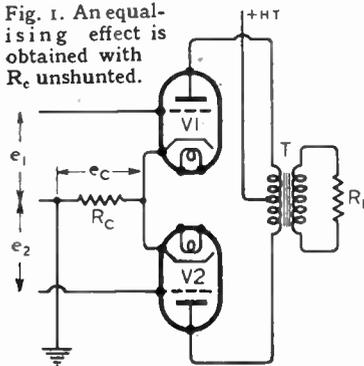

In a general way it is quite easy to see what happens. Suppose V1 and V2 are alike but that the input  $e_1$  to V1 is greater than the input  $e_2$  to V2. Clearly the alternating anode current of V1 will be greater than that of V2. The currents are in opposite phase through  $R_c$  and tend to cancel. As they are unequal, the effective current is their difference and this develops an alternating voltage across  $R_c$ . The anode current, however, depends on the grid-cathode voltage and this is equal

to the difference between the input and the cathode-earth voltages.

In the case quoted of  $e_1$  greater than  $e_2$  the cathode-earth voltage is in phase with  $e_1$  but in opposite phase to  $e_2$ . The grid-cathode voltage of V1 is, therefore,  $e_1$  minus  $e_c$ , while the grid-cathode voltage of V2 is  $e_2$  plus  $e_c$ . Thus the grid-cathode voltage of V1 is less than  $e_1$  and that of V2 is greater than  $e_2$ . The anode currents are proportional to the grid-cathode voltages, consequently the currents in V1 and V2 are less and greater respectively than they would be if no voltage were developed across  $R_c$ . In other words, when the input voltages are unbalanced the anode currents are not as much out of balance as they would be if  $R_c$  were shunted by a large-capacity condenser.

There is, in fact, feedback from the bias resistance, and it is negative on the side with the greater input and positive on the side with the smaller input. It thus tends to equalise the currents. By a similar process of reasoning it can be shown that the action is the same if the inputs are equal, but V1 and V2 are unlike either in their AC resistances or their amplification factors.

When  $e_1$  and  $e_2$  are equal and an ideal output transformer is used, unbalance can be caused only by the valves. In practice, this is the predominant cause of unbalance with good quality components. It is then easy to show that the ratio of the alternating anode currents is given by equation (1) in the Appendix.

The order of magnitude of the self-balancing action can be seen by a typical example. Suppose that the two valves are triodes having amplification factors of 6, but that one has an AC resistance of 1,000 ohms while the other is only 800 ohms. The bias resistance can be taken as 500 ohms. It is not necessary to specify

$n^2 R_L$  in this case, because the amplification factors are the same.

On inserting values in equation (1) it will be found that the alternating anode current of the lower resistance valve is 2.5 per cent. greater than that of the other. The use of a sufficiently large by-pass condenser across  $R_c$  is equivalent to making  $R_c$  equal to zero, and the higher current then becomes 25 per cent. greater than the other. Inasmuch as the omission of a by-pass condenser reduces the unbalance from 25 per cent. to 2.5 per cent., it is clear that the self-balancing action is of considerable magnitude.

With resistance, instead of transformer, coupling the results are similar, but they are not quite the same, for the anode circuits are not coupled together. The coupling in the transformer precludes any possibility of inequality between the two alternating anode voltages—only the currents can be different. With resistance coupling, however, there is no such coupling and both currents and voltages can be different.

### R-C Coupling


The basic circuit of a resistance-coupled stage is shown in Fig. 2. The symbol  $R_1$ , although shown against the coupling resistance of  $V_1$ , is actually used to denote the value of this resistance in parallel with the grid leak of the next stage.  $R_2$  similarly denotes the AC load impedance of  $V_2$ .

By exactly the same reasoning as before, it can be shown that any inequality of the anode currents caused by inequality of the inputs or valves is reduced by the feed-back action from  $R_c$ . As the output voltages are equal to the products of the respective anode currents and load resistances, the self-balancing action occurs on the voltages as much as on the currents.

This is, however, true only if  $R_1$  and  $R_2$  are identical. If they are not, the effect of  $R_c$  may be to do more harm than good.  $R_c$  always tends to equalise the currents, but if  $R_1$  and  $R_2$  are unequal, balanced currents will not give balanced output voltages.

That this is indeed the case can be seen by supposing that the input voltages and valves are identical, but that  $R_1$  is less than  $R_2$ . Then the current through

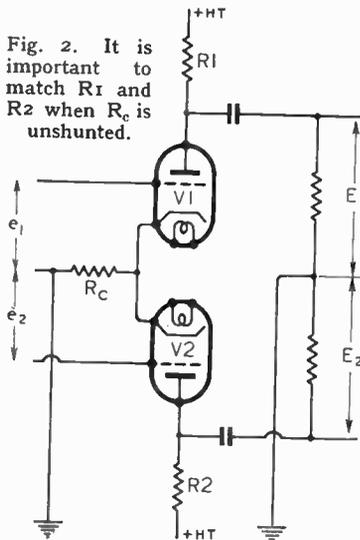$V_1$  will be greater than that through  $V_2$ , but in the absence of feed-back from  $R_c$  the output voltage developed by the higher current across the lower resistance  $R_1$  will be less than that developed by the lower current across the higher resistance  $R_2$ .



This is because the currents are dependent not only on  $R_1$  and  $R_2$ , but also on the valve resistances, so that the ratio of the currents is smaller than  $R_2/R_1$ .

When  $R_c$  plays its part, the feed-back reduces the current in  $V_1$  and increases it in  $V_2$ , so tending to equalise the currents. The decrease of current in  $V_1$ , however, still further reduces the voltage across  $R_1$ , and the increase of current in  $V_2$  further increases the voltage across  $R_2$ . The effect of  $R_c$  in this case, therefore, is to increase the voltage unbalance.

As compared with the condition when  $R_c$  is shunted by a large capacity, the feed-back effect reduces unbalance in the output voltages when they are caused by a lack of identity in either the input voltages or the valves. It increases the unbalance, however, when it is caused by inequality of the load resistances. When all elements are unbalanced the feed-back may either increase or decrease the unbalance—depending on the precise relations involved.

Equation (2) enables the performance to be readily calculated. As an example assume that the input voltages and amplification factors are equal. Let the amplification factors be 40,  $R_1 = R_2 =$

50,000 ohms,  $R_c = 1,000$  ohms,  $R_{a1} = 20,000$  ohms, and  $R_{a2} = 15,000$  ohms. Then when  $R_c$  is by-passed the unbalance becomes 7.5 per cent., but when there is no shunt condenser it is only 3 per cent. On the other hand, using the same values but making  $R_2 = 40,000$  ohms, with the valve resistances equal at 15,000 ohms, the unbalance is 17 per cent. with feed-back from  $R_c$  and 15 per cent. without feed-back.

It is clear, therefore, that from the point of view of balance it is definitely advantageous to omit the by-pass condenser from  $R_c$ , but that it then becomes somewhat more important to employ matched coupling resistances. When  $R_c$  is not by-passed, the equality of the coupling resistances is much more important than the matching of the valves or the balance of the input voltages. As ordinary resistors have a tolerance of  $\pm 20$  per cent., the possible unbalance between resistors nominally alike is as much as 40 per cent. For good balance nothing worse than 2 per cent. tolerance resistors should be used, but it is not necessary that they should be within 2 per cent. of their nominal value, merely that they should be alike within this tolerance.

It is now necessary to consider the effects of non-linearity in the valves. To simplify things as much as possible, it will be assumed that the input voltages are equal and that the valves and their individual loads are identical, so that the stage is perfectly balanced. It will also be assumed that the valves have square-law dynamic characteristics, for then only second harmonic distortion is introduced in the individual sides. The circuit is that of Fig. 2 and the output transformer referred to below is, of course, in a subsequent stage.

The first thing to notice is that the fundamental components of the anode currents, being in phase with the input voltages, are equal and opposite in the common HT lead and in the common cathode circuit. They cancel completely, therefore. The second harmonic components are in phase at these points, however, and consequently combine to produce an alternating voltage across any impedance in the cathode circuit. They cancel in the output transformer, where

the fundamental components add.

If the cathode resistance  $R_c$  is adequately by-passed the second harmonic distortion of the individual valves balances in the output transformer. The stage as a whole then introduces no distortion.

If  $R_c$  is not by-passed a voltage at twice the input frequency is developed across it and is applied in the same phase to the grids of both valves. In effect, therefore, the grid-cathode voltage of each valve consists of two voltages—one of frequency  $f$  and the other of frequency  $2f$ . As the valves are non-linear sum and difference frequencies are formed in the output, and they are  $f$  and  $3f$ . The one at the fundamental combines with the direct fundamental component and so changes its magnitude somewhat, but the other appears in the output as a third harmonic.

A second harmonic of the second harmonic component of the grid-cathode voltage is also formed—this is a fourth harmonic of the input. It flows through  $R_c$  and so produces a fourth harmonic component in the grid-cathode voltage. By sum and difference this produces 5th and 7th harmonics.

The net result of  $R_c$  is to produce in the anode currents of both valves an infinite series of harmonics of the input frequency. The even-order harmonics all cancel in the output transformer, but add in  $R_c$ , while the odd-order harmonics cancel in  $R_c$  and add in the output transformer.

### Output Distortion

In the ideal push-pull stage the effect of omitting a by-pass condenser to  $R_c$  is to produce in the output a series of odd-order harmonics where there were none before. Distortion is, therefore, increased. The important practical point, of course, is the amount of the increase. Unfortunately, it is only possible to calculate this easily in certain special cases. It is worth attempting it, however, for it gives a good indication of the order of magnitude of the effect, and so enables one to make a good guess at the results in a practical case in which exact calculation is too laborious to be worth while.

Equation (2) in the Appendix gives the third harmonic distortion ratio for the case when the

dynamic characteristic of the valve can be expressed by a quadratic equation. It is strictly applicable only to the case of a resistance-coupled stage, for no account has been taken of the coupling of the two valve circuits by a transformer. The subsequent combination of the outputs in a succeeding stage is considered, however.

The third harmonic distortion is expressed in terms of two symbols  $\alpha$  and  $\beta$ , and it may be as well to consider their meaning. The former is merely the ratio of second harmonic to fundamental in each valve acting independently. If the valve is completely linear  $\alpha$  is zero and there is no distortion in the stage at all. The other term,  $\beta$ , is a number, since  $A_1$  has the dimensions of a conductance and is really the effective value of the mutual conductance of the valve at the fundamental frequency. It forms a kind of coupling factor in the production of third harmonics from the second. It is zero when the cathode resistance is zero, or shunted by a large capacity, and there is then no third harmonic production.

Similar expressions to equation (3) can be determined for the higher order odd harmonics. Their percentage is always less than that of the third, however, so that if the design is carried out to make the third negligible, they also are negligible.

As one example of the magnitude of the effect, the case of the penultimate stage of the *Wireless World* Push-Pull Quality Amplifier has been examined. MHL4 valves are used with a cathode resistance of 500 ohms. Over a range somewhat greater than that covered by the maximum signal input it was found that the dynamic characteristic could be represented almost exactly by the necessary quadratic equation, the actual and calculated curves being indistinguishable on a normal scale of plotting. The values of  $A_1$  and  $A_2$  deduced from the curves are respectively 0.56 and 0.0086. The normal maximum input is 3.5 volts peak per valve, so that  $\alpha=0.0051$  and  $\beta=0.72$ . This gives the third harmonic ratio as  $4.66 \times 10^{-6}$ .

This is quite negligible, and is likely to be much smaller than the second harmonic in the out-

put when the stage is not perfectly balanced, as it will not be in practice. Such lack of balance will not affect the amount of third harmonic appreciably because it depends on the sum of the individual second harmonics of the two valves, whereas the second harmonic in the output depends on their difference. The sum is only changed by a small amount if the two sides of the amplifier are slightly different, but the difference changes a lot.

### Harmonic Relationship

The value of the term  $\beta$  must lie between 0 and 2. It is easy to show that even with the maximum value of  $\beta$  the simple equation (4) is sufficiently accurate for degrees of second harmonic distortion up to at least 20 per cent. ( $\alpha=0.2$ ). Thus, for 20 per cent. second harmonic per valve, equation (3) gives the third harmonic as 2.24 per cent. While equation (4) makes it 2 per cent. In practice,  $\beta$  is usually less than unity and it is not customary to allow the second harmonic per valve to be anything like 20 per cent. In nearly all practical cases, therefore, the simple equation (4) is sufficiently accurate.

In all ordinary cases of Class A push-pull the third harmonic ratio will not exceed  $\alpha^2/2$ , and will usually be less. 10 per cent. distortion per side is probably as much as is ever allowed in Class A; this makes  $\alpha=0.1$  and the third harmonic ratio cannot exceed 0.005, or 0.5 per cent. In actual fact, it will rarely be more than one-half of this, because  $\beta$  will be around unity.

In applying these results it must not be forgotten that no allowance has been made for valves having characteristics only expressible by a cubic equation. Such valves introduce third harmonic distortion directly and tetrodes and pentodes are the most obvious examples. When used in push-pull, however, the load impedance is always chosen so that the direct third harmonic distortion is a minimum, for the higher second harmonic distortion then obtained balances in the push-pull connection. Push-pull, in fact, offers little advantage unless the distortion per valve is predominantly second harmonic. It is reasonable to suppose, therefore, that the analysis given

above applies at least approximately to most normal cases.

It is safe to say that in any push-pull stage in which the second harmonic distortion per side is less than about 5 per cent., the odd-order harmonic distortion introduced by the omission of a cathode resistance by-pass condenser is negligible. As the omission of the condenser considerably improves the balance of the stage and is also economical, it is good practice not to use a condenser.

**When to Omit Condenser**

It is safe to say that a by-pass condenser need not be used in any normal Class A stage. In a Class AB stage which is driven fairly lightly, so that in reality it is only just Class AB, it is usually safe to omit the condenser. The total distortion may increase slightly, or what is really the same thing, the undistorted output may be slightly less. It will sometimes be better to make up for this by increasing the anode voltage and current slightly, provided that the valves are not already running at their limit, than to use a condenser.

With true Class AB the distortion per valve is fairly high, and a by-pass condenser on the cathode resistance is usually advisable. If Class AB is being utilised to the limit, however, in order to obtain the maximum possible output, then cathode bias itself is not permissible and the question of a by-pass condenser does not arise. This is always true of Class B; both Class B and "heavy" Class AB demand a fixed bias source because there is a large fluctuating anode current. Cathode bias is only allowable when the mean anode current is substantially independent of the signal input.

To sum up, in all push-pull stages but the output it is usually desirable to use a common cathode bias resistance without a by-pass condenser because of the self-balancing action then obtained. Distortion is increased by a negligible amount. In a Class A and "light" Class AB output stages the by-pass condenser can also normally be omitted with advantage. It should not be omitted, however, in a true Class AB stage. The omission of the condenser makes

it less important to use matched valves, and in the case of a resistance-coupled stage it becomes more important to match the coupling resistances than the valves.

**APPENDIX**

**The linear condition**

(Circuit of Fig. 1).

$$\frac{i_{a2}}{i_{a1}} = \frac{\mu_1 \{R_{a1} + R_c (2 + \mu_1)\} + n^2 R_L (\mu_2 - \mu_1) / 4}{\mu_1 \{R_{a2} + R_c (2 + \mu_2)\} + n^2 R_L (\mu_1 - \mu_2) / 4} \dots (1)$$

where

- $\mu_1$  and  $\mu_2$  = amplification factors of  $V_1$  and  $V_2$  respectively,
- $R_{a1}$  and  $R_{a2}$  = anode A.C. resistances of  $V_1$  and  $V_2$  respectively,
- $i_{a1}$  and  $i_{a2}$  = alternating anode currents of  $V_1$  and  $V_2$  respectively,
- $R_c$  = cathode bias resistance,
- $n$  = ratio of primary/secondary turns on transformer,
- $R_L$  = secondary load resistance.

(Circuit of Fig. 2).

$$\frac{E_2}{E_1} = \frac{R_2}{R_1} \frac{\mu_2 e_2 \{R_{a1} + R_1 + R_c (1 + \mu_1)\} + \mu_1 e_1 R_c (1 + \mu_1)}{\mu_1 e_1 \{R_{a2} + R_2 + R_c (1 + \mu_2)\} + \mu_2 e_2 R_c (1 + \mu_1)} \dots (2)$$

where

- $e_1$  and  $e_2$  = input voltages of  $V_1$  and  $V_2$  respectively
- $E_1$  and  $E_2$  = output voltages of  $V_1$  and  $V_2$  respectively,
- $R_1$  and  $R_2$  = anode circuit load resistances of  $V_1$  and  $V_2$  respectively (each equals the coupling resistance in parallel with the following grid leak).

Other symbols are the same as for equation (1).

**The non-linear condition**

The valve dynamic characteristic is assumed to be expressed by

$$I = a_0 + a_1 E_g + a_2 E_g^2$$

where  $I$  = direct anode current,  
 $E_g$  = grid bias.

Inserting  $I = I_{D0} + i$   
 $E_g = E_{D0} + e_g$

expanding by Taylor's theorem and extracting the alternating components gives,

$$i = (a_1 + 2a_2 E_{D0}) e_g + a_2 e_g^2$$

$$= A_1 e_g + A_2 e_g^2$$

where  $i$  = alternating anode current,  
 $E_{D0}$  = operating value of grid bias.

When  $R_c = 0$ , the ratio of second harmonic to fundamental components in each valve is  $\alpha = e_g A_2 / A_1$

When  $R_c$  is finite, the ratio of third harmonic to fundamental in the output of the push-pull stage is

$$\gamma = \frac{\alpha^2 \beta (0.25 + 0.078 \alpha^2 \beta^2 + 0.041 \alpha^4 \beta^4 \dots)}{1 - \alpha^2 \beta (0.75 + 0.156 \alpha^2 \beta^2 + 0.068 \alpha^4 \beta^4 \dots)} \dots (3)$$

where  $\beta = \frac{2}{1 + 1/2 A_1 R_c}$  provided that  $\alpha \beta < 1$

When  $\alpha \beta$  is small equation (3) reduces to

$$\gamma = \alpha^2 \beta / 4 \dots (4)$$

If  $I$  and  $i$  are expressed in mA,  $R_0$  must be in k $\Omega$ .

**Books issued in conjunction with "Wireless World"**

	Net Price	By Post
FOUNDATIONS OF WIRELESS. Fourth Edition, by M. G. Scroggle ... ..	7/6	7/10
TELEVISION RECEIVING EQUIPMENT, by W. T. Cocking ... ..	10/6	10/10
RADIO LABORATORY HANDBOOK, by M. G. Scroggle. Second Edition ... ..	12/6	12/11
WIRELESS SERVICING MANUAL, by W. T. Cocking. Sixth Edition ... ..	7/6	7/10
HANDBOOK OF TECHNICAL INSTRUCTION FOR WIRELESS TELEGRAPHISTS, by H. M. Dowsett and L. E. Q. Walker. Seventh Edition ... ..	30/-	30/7
RADIO DATA CHARTS. Third Edition, Revised by J. McG. Sowerby, B.A., Grad. I.E.E. ... ..	7/6	7/10
RADIO INTERFERENCE SUPPRESSION, by G. W. Ingram ... ..	5/-	5/4
LEARNING MORSE. 335th thousand ... ..	6d.	7½d
INTRODUCTION TO VALVES, by F. E. Henderson ... ..	5/-	5/4
RADIO WAVES AND THE IONOSPHERE, by T. W. Bennington ... ..	6/-	6/3

Obtainable from leading booksellers or by post from

ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1

# RAILWAY COMMUNICATIONS

## A Frequency-Modulated Carrier-Current System

From the point of view of communications, a moving train is unlike any other mobile station, in that "wired wireless" or carrier-current telephony may be considered as a possible alternative to true radio. In America, where the "inductive" system here described was developed, strong arguments have been adduced in favour of non-radiating methods of communication for use on railways.

THE application of telecommunications to moving trains, partly as an aid to operational efficiency and partly as a safety measure, has been closely studied by railway and communication engineers in America over a long period of years, and equipment for the purpose has now reached quite a high state of development.

It may be of some interest briefly to examine the minimum requirements for a train communication system, if it is to be a worth-while aid to the efficient operation of a railway. First, telephonic communication to and from a moving train over an adequate distance is essential, together with facilities for intercommunication between trains on the same, or adjacent, tracks, but only over a short distance. Secondly, the traffic controller should be able to break into any conversation in order to pass on an urgent and important operational message. Inter-communication between engine crew and guard on a train is also required.

### Inductive System

No doubt these requirements could be met in more than one way, but it must suffice, for the purpose of this article, to consider only the solution provided by the Union Switch and Signal Company, of Pennsylvania, with which is associated in this country the Westinghouse Brake and Signal Company, Ltd. Described as the Union Inductive Train Communication System, and based on the carrier-current or wired wireless principle, it is called an inductive system because the path of the signal from sending to receiving points includes two or more inductive links.

This is well illustrated in the accompanying schematic drawing showing the mechanism of transmitting a signal from a guard's


van to a locomotive, the location of the various inductive links being easily recognised. The guard's van may be part of the same train or it may be part of an entirely different train; the principle of operation is the same. Likewise a traffic office could take the place of either the locomotive or the guard's van.

Briefly stated, the carrier current output from the transmitter is induced into that portion of the railway track over which the vehicle is passing by means of a properly matched transmitting loop. The track rails, vehicle and adjacent ground form a load circuit for the loop, and maximum transference of energy results. The magnetic fields generated by the loop and the load circuit thread any adjacent telegraph or signalling wires paralleling the track and induce carrier-frequency currents in them.

Because the rails are poorly insulated and rail section joints very imperfectly bonded the signals induced in them suffer heavy attenuation, but those induced in the track-side wires may travel very considerable distances, since

will generally be of sufficient intensity to re-induce currents in the track rails, so enabling communication to be effected with trains in the vicinity. It is apparent that under some conditions very high receiver sensitivity may be required, and in order to ensure satisfactory reception in the most awkward locations a maximum sensitivity of 1 microvolt is available in all receivers.

As signal currents have to be injected into lines and conductors which are subject to wide variations in distributed impedance the best operation is obtained with carriers of fairly low frequency. When FM is used the Union system is operated on any frequency lying between 10 and 250 kc/s, a typical installation usually providing for two-channel working on perhaps 80 and 120 kc/s respectively. Most of the rolling stock and possibly all the traffic control stations would be equipped for transmission and reception on both channels, but as a rule the routine messages and inter-train communications are confined to one channel only, the other being reserved for emergency traffic and

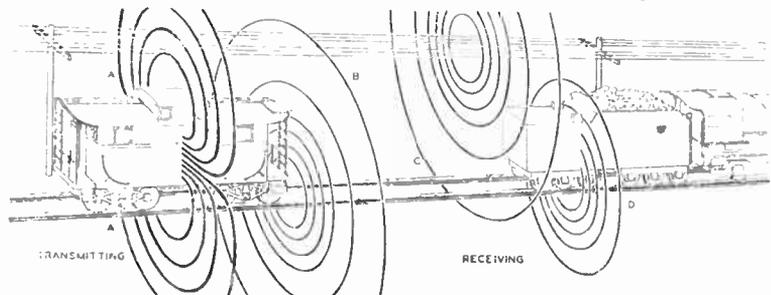

Schematic diagram showing the mechanism of transmission and reception by the Union Inductive Train Communication equipment. The two vehicles shown may be part of the same train or part of an entirely different train.

these are usually either telegraph or telephone lines and consequently are well insulated.

At distances of the order of 100 miles signal currents in the wires


to enable a fairly free channel to be available for the traffic controllers to break in on a conversation between trains.

Although a single receiver

**Railway Communications**— could, no doubt, be used for simultaneous reception on two different frequencies when one is for emergency use only, the Union system favours the more straightforward practice of providing a separate receiver for each channel. Thus the equipment for two-channel working has two independent receivers but only one transmitter, the latter being capable of rapid adjustment to whichever channel is required.

is inherently bad, and partly because this method of modulation has the least disturbing effect on varying amplitude signals such as telephone and telegraph services along the track. A speech frequency of 6,000 c/s is used; that is, a maximum of 3,000 c/s either side of the nominal carrier frequency. As this enables speech frequencies of from 200 to 2,750 c/s to be impressed on the carrier it provides good speech quality. Transmitters and receivers fol-

The normal working distances covered by the equipment illustrated here is approximately five miles between trains and up to 120 miles when communicating with a fixed traffic control. The longer distances in the latter case can be accounted for by the higher carrier power that can be injected into the line wires from a fixed station, where either a direct connection can be made, or, as is more usual, closer coupling effected by running some radiating wires parallel to the track-side wires for a hundred feet or so.

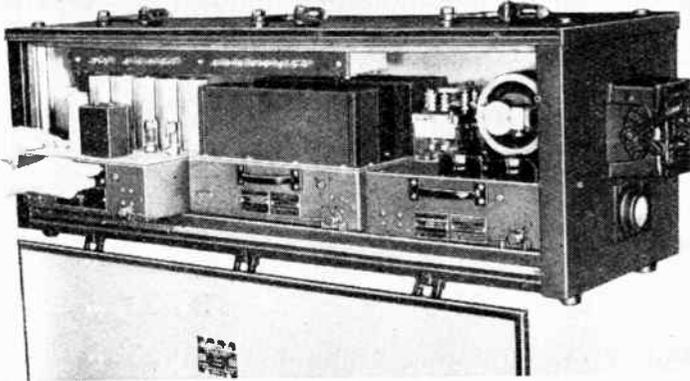

A single-channel train communication equipment comprising transmitter, receiver and power supply units. Interconnection is by means of plugs and sockets giving easy replacement of a faulty unit. The container has shock-absorbing mountings.

The equipment is relay operated by remote control, thus enabling the bulky part of the equipment, comprising receivers, transmitters and power supplies, to be accommodated in a convenient out-of-the-way part of the vehicle. Only the remote control unit with its telephone hand-set (which embodies a microphone and press-to-transmit switch) and a loudspeaker need be accessible to the users. The change-over switching is so arranged that the loudspeaker is always connected to the receiver tuned to the channel not being used for transmission at the time. If, for example, the channel selector switch were set for operation on 80 kc/s the telephone hand-set would be connected to the 80-kc/s receiver and the loudspeaker to the 120-kc/s set.

### Advantages of FM

Frequency modulation is now used in the Union equipment partly because it provides a better signal-to-noise ratio under conditions where electrical interference

low normal radio practice for FM equipment, but low-impedance transmitting loop and receiving coils take the place of the usual aerial systems. The four principal units; namely, transmitter, two receivers and power supply, are housed in a stout waterproof container hung on shock-absorbing mountings. Units are readily interchangeable with similar items in other equipments, the design permitting quick release and replacement of any faulty units. Plugs on the back of each chassis marry with corresponding sockets on the container so that when a unit is pushed into place interconnection between units is made automatically. The turn of a lever on the front of each chassis securely locks the units in the container.

Power is provided through a dynamotor from a bank of accumulators in the case of a guard's van installation and from the headlight electric supply in the case of a locomotive. This is a standard fitting on American locomotives which usually have a 32-volt DC supply for this purpose.

## POST-WAR FREQUENCY ALLOCATION

### Guiding Principles

AT a recent discussion meeting of the Radio Section, Institution of Electrical Engineers, fears were expressed that expediency might possibly prevent the allocation of frequencies on a purely rational and scientific basis. If that happened, it would be more than ever necessary to make the best possible engineering use of channels.

On the guiding principles of allocation, it was agreed that priority should be given to those services concerned with safety of life and with communications involving mobile stations, particularly ships and aircraft, for which no system other than radio is available. Further, the mobile station should have a first call on the best frequencies, as it is inherently more restricted in the equipment and power that it can use than is the fixed station. Transoceanic telephony should also rank high, as there is at present no satisfactory alternative to radio.

Narrower telegraphy channels, drastic reduction of bandwidths generally, closer frequency tolerances, better use of directional properties of transmitting aeri-als, and extended use of the principle of relaying over paths subject to favourable propagation conditions were all advocated as making for more effective use of radio channels. In connection with relaying, it was urged that provision of direct services between all the important centres of the world was inefficient or impracticable; the question of an international relay network was considered.

Dr. R. L. Smith-Rose, who opened the discussion, said, in summing up, that ultimately it might be necessary to accept the principle that radio should be restricted to those services for which a metallic connection was impracticable.

# *Angles on* **BRIMAR PRESTIGE**



*You can use Brimar Valves with the complete confidence that you will get peak performance from them. Valves are still in short supply, but you may be able to get the Brimar Valve you require.*

# BRIMAR

(BVA)

# VALVES

**STANDARD TELEPHONES AND CABLES LIMITED, FOOTSCRAY, SIDCUP, KENT.**

THREE SPOTS OF DIRT...



gang have just as Tojo and all his blight can shown how a little bit of in this world so can an imperfect transformer quite easily gum up the works of any electrical system. A mere few specks of dust nesting in the wrong place can make you wonder if you or the man who sold you the new spotwelder is daft . . . or both!! remember that every Parmeko transformer is "pressure impregnated". What does all that mean you ask? Well, to revert to the vernacular it means there's no muck in it now nor never. Makes a big difference - you'd be surprised!

The design of electronic equipment has grown into an exact science but even now there are many problems in Transformer design which, if not put in the hands of an experienced Transformer expert, can retard the performance of any equipment. The many years of experience during which Parmeko Ltd. have specialised in Transformers enables us to recognise and control any possible source of trouble.

PARMEKO LTD., LEICESTER.  
Makers of Transformers.



Clear as a Crystal

AND HERE IS THE REASON . . .

. . . the answer has been found in Bullers Low Loss Ceramics to the problem of Dielectric Loss in High Frequency circuits.

Years of Laboratory research and development have brought these materials to a high degree of efficiency. To-day they are in constant use for transmission and reception, and play a vital part in maintaining communications under all conditions.




Made in Three Principal Materials

FREQUELEX

An Insulating material of Low Dielectric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

PERMALEX

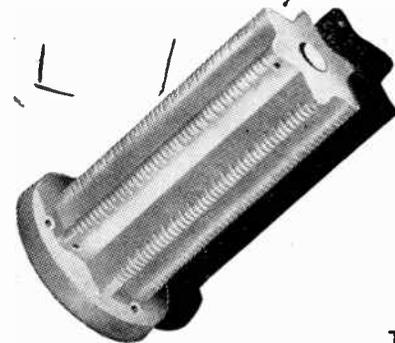A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.



TEMPLEX

A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.

BULLERS, LTD.  
THE HALL,  
OATLANDS DRIVE,  
WEYBRIDGE, SURREY  
Telephone :  
Walton-on-Thames 2451  
Manchester Office :  
196, Deansgate, Manchester.

Bullers

LOW LOSS CERAMICS



# SUNSPOT MINIMUM

## Has It Already Passed?

T. W. BENNINGTON

IN *Wireless World* for February, 1944, was an article entitled "1944: Sunspot Minimum Year," in which were discussed some of the solar phenomena which occur at the end of one solar cycle and the beginning of the next. It was pointed out that, though it was impossible to say with any certainty when the minimum of the current solar cycle would be reached there were definite indications that it was fast approaching, and that it might occur during 1944. In the July issue was a report of the indications put forward by Dr. A. H. Shapley, who, using formulae derived by Brunner, found that the minimum of the cycle might occur in 1944.9 (using the decimal date system). He was careful to add that this date should be regarded rather as an indication than as a definite prediction.

As 1944 is now well past it may be interesting to see what variations in solar activity did take place during that year. But it should first of all be stated that, because the solar activity fluctuates widely from day to day, it is impossible to know that the minimum has actually been reached until some time after that event. The solar activity—as evidenced by the size and frequency of appearance of the sunspots, and in other ways—may temporarily increase, only to decrease again to a new low level. Nevertheless the solar happenings of recent months do indicate that the minimum is possibly already past, and that the sun's activity has begun its rise towards the next solar maximum, which may occur in four or five years' time.

### Effects on Radio

Before going into any details about the solar activity it may—at the risk of being repetitive—be as well to reconsider the connection between it and the science of radio communication. Why should the radio man be at all interested in these solar phenomena?

Well, it is because of the fact that the short radio waves are dependent for their propagation over long distances upon the state of the ionosphere, and that the ionosphere is produced—at least largely if not entirely—by the ultra-violet light radiated by the sun. The degree of ionisation of the gases of the ionosphere therefore changes with the variation of solar activity, reaching high levels at the maximum of the solar cycle and low values at the minimum. When the ionisation is high then higher frequencies (shorter waves) must be used for a given distance for good propagation by the ionosphere, and when low ionisation prevails the lower frequencies (longer waves) must be used. Consequently, as the solar activity increases again we may expect to have to make more use of higher short-wave frequencies than for the past few years, perhaps to bring into use high frequencies not hitherto used and to discard some of the lower ones.

To return to the recent variations in solar activity. The sunspot activity is measured and recorded by means of a system of "relative sunspot numbers," which takes into account the number of sunspot groups and also the number of individual spots observed at different observatories. This "relative number" may thus be regarded as a measure of solar activity as evidenced by the sunspots. The Table gives the yearly means of this number for each year since 1937, the year of the last solar maximum. It is seen that the activity has decreased year by year from then,

Yearly Means of Relative Sunspot Numbers.		
Year	..	Sunspot Number
1937	..	114.4
1938	..	109.6
1939	..	88.8
1940	..	67.8
1941	..	47.5
1942	..	30.6
1943	..	16.3

so that the mean for 1943 was at the low value of 16.3. Although the yearly mean for 1944 is not yet available it was probably about 10.0. The yearly mean for 1933—when the previous minimum occurred—was 5.7.

### Lowest Level?

During the first few months of 1944—judging from the *monthly* means of the sunspot numbers so far available—the solar activity dropped to even lower levels than had occurred towards the end of 1943; indeed, during February and April there were practically no sunspots observable. But in August there was a considerable increase, and up to the end of December this increase had been fairly consistently maintained. So that as far as the period 1943-44 is concerned there was a minimum in the activity at about 1944.5. Was this the actual minimum of the sunspot cycle, or may the activity fall to a new low level? That is a question which only time can answer, but it may at least be said that there is a distinct probability that the minimum is indeed already past, and we are definitely on the way towards a new maximum.

During December there appeared a major group of sunspots—the first *large* group to be observed for many months—and this crossed the sun's central meridian on December 14.3. It was in solar latitude 22 deg. South, and this fact indicates that it might properly be considered as belonging to the new cycle. For towards the end of a cycle the spots belonging to the old cycle appear in low latitudes—around 8 deg.—but there also begin to appear sunspots in high latitudes (20 deg.-40 deg.), and these are considered to belong to the new cycle. These high-latitude spots have been appearing for the past eighteen months, and with increasing frequency during that period.

As was explained in the *Wireless World* article first referred to, the magnetic field of the sunspots undergoes a reversal of polarity at

**Sunspot Minimum—**

the end of a cycle, and the Mount Wilson Observatory has observed this reversal of polarity to be occurring in the case of the high-latitude spots for some time past. There are thus the three facts (a) the reversal in magnetic polarity of certain sunspots which has been observed for some time, (b) the observation with increasing frequency for the past eighteen months of high-latitude sunspots, (c) the increase in sunspot activity which commenced last August, which would seem to indicate that the solar activity has now started a general increase towards the maximum.

**Ionosphere Disturbances**

Incidentally readers of *Wireless World* will no doubt remember that the sunspots, besides producing a rise in the ionisation of the upper atmosphere such as gives rise to good propagation of short waves, sometimes also appear to be responsible for temporary ionosphere disturbances, radio fade-outs and magnetic storms. They will therefore be interested to know that, following the passage across the sun's central meridian of the large sunspot group on December 14.3, there was a considerable disturbance in the earth's magnetic field on December 16th-17th. A number of sudden radio fade-outs also occurred, and then ionosphere conditions were very "stormy" from December 16th-20th.

# FREQUENCY CONTROL IN RADIO HEATING

**A**LTHOUGH frequency control may be uneconomical in low-powered radio heating units it offers many advantages in larger installations. The hot and steamy atmosphere of a moulding shop is not the best environment for RF generators, and there is much to be said for the use of a separate RF "power house" with connection by transmission lines to operating heads adjacent to each press. Alterations in the layout of the press shop are more easily carried out with this arrangement, and the possibility of damage is limited to a comparatively small unit.

The successful utilisation of long transmission lines is dependent on correct termination, and this is facilitated if the "work circuit" is tuned to the generator frequency. An automatic device for compensating for capacity variation due to changes in dielectric constant of the material during heating has been described recently\* by R. W. Gilbert, and the circuit is shown in the figure. One of the parallel plates between which the preform is placed is movable, and the distance of separation is adjusted by a reversible electric motor


\* *Electronics*, December, 1944.

controlled by a relay in the output circuit of a phase-sensitive valve bridge. The input to the bridge is obtained through a separate transmission line to include phase shifts through the power transmission line caused by detuning of the work circuit. The phase deviation is in opposite directions on each side of resonance, and the polarity of the DC output—normally balanced to zero—also depends on whether the load is effectively inductive or capacitive. Not only does the plate separation adjust itself to allow for a rise in dielectric constant in the work during heating, but it also compensates for initial differences in the preforms.

In practice the movement of the top plate during the heating cycle is found to be about one-tenth of the preform thickness, and a plate speed of two to four inches per minute has been found satisfactory for thicknesses up to four inches. If the air space does not exceed one-fifth of the preform thickness, uneven heating due to fringing of the field is not excessive. Danger of flash-over in the generator due to mismatching while the initial adjustment of the work circuit is taking place must be guarded against by using tank circuit condensers with a factor of safety above normal. Risk of damage through starting up without a preform between the plates is lessened by limit switches on the plate traverse; the driving mechanism is also provided with a disengaging gear which operates if the plate makes contact with the preform.

To ensure that the generator is always fully loaded the presses are operated in rotation, and an interlocked contact system ensures that only one operating head at a time is connected to the generator.

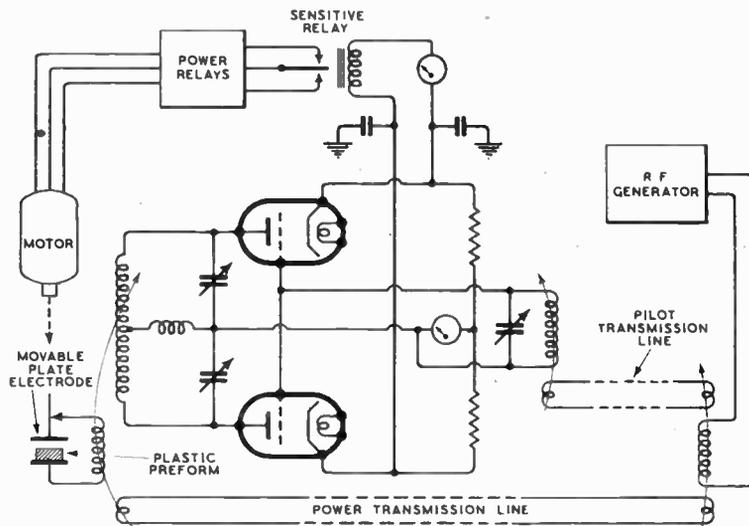If the proposed allocation of frequency bands for radio heating materialises, the ability to operate on a fixed frequency would in many cases save the cost of screening and its attendant working restrictions.



Essential circuit of frequency control mechanism for radio heating.

# TEACHING MATHEMATICS

## *Plea for Improved Methods*

By J. J. DURACK,  
M.A., F.Inst.P.

THE report on the above subject recently issued by a combined committee of members of the Institute of Physics and the Mathematical Association provides very interesting reading. Coming from such a body of experts, it deserves the serious attention of practical men.

There are, in the report, some statements with which many will immediately disagree. In the first line we read, "Some knowledge of mathematics is essential to every experimental physicist." And later, "A student whose mathematical ceiling is really unduly low would probably be well advised to transfer his interest to some other branch of science."

Now Faraday had no mathematical knowledge. We may read through the whole of his "Experimental Researches" without finding a single mathematical symbol. And how much would we miss to-day if Sir Humphrey Davy had advised him to transfer his interest from physics to some other science. We might still be without electricity for light, heat and power.

Let us not, however, rush to the other extreme and imagine mathematics a hindrance, as many may do after reading the report of Prof. Howe's I.E.E. speech in *Wireless World* for July, 1944. Prof. Howe told his audience that "the most outstanding achievements in the early days of wireless telegraphy were accomplished in spite of principles and theory."\*

The most outstanding achievement in wireless telegraphy was undoubtedly Hertz's discovery of electromagnetic waves which had been predicted some twenty years previously by Maxwell on purely mathematical grounds. Convinced of the soundness of Maxwell's theory Hertz deliberately set out to produce and detect these waves.

Discoveries in science are not made by haphazard experimentation but by looking for something.

\* It should perhaps be noted that this statement, without context or explanation of the circumstances in which it was made, may give a misleading impression of Prof. Howe's real views on the matter. [Ed.]

Theory provides the road along which the experimenter may travel and the greater his mathematical attainments the swifter his progress will be. Faraday's genius built up a geometric picture of lines of force which served him as a working theory. This picture, in mathematical dress, forms the basis of Maxwell's theory of electricity and magnetism.

The distrust of mathematics among practical men is fairly widespread. From time to time we are treated to tales of mathematical "errors" like the story of Tait and the golf drive. The errors, however, are not in the mathematics but in their misapplication. An erroneous assumption will, in the long run, lead to a false conclusion though the intermediate steps be perfectly correct.

In addition to mistrust we find amongst practitioners a fear, or hatred brought on by fear, of mathematics, however simple. I know, from personal experience, that this fear can sometimes be dispelled and interest stimulated by taking quite a complicated formula and explaining each term in simple language. A neat approach on these lines was taken by Martin Johnson with Maxwell's electromagnetic equations in *Wireless World*, Feb.-July, 1943.

In the Committee's report it is rightly stressed that theory and practice should go hand in hand, but little is said of the manner of conducting classes. The present system of the university lecturer is an hour's address to a large class, after which he collects his papers and departs. More than half the students gain little or nothing from such lectures. Classes should be limited to a dozen students, the last quarter-hour devoted to question and answer and the students given one or two problems to work out for themselves, the lecturer's solutions being given at the beginning

of the next lecture. In the words of the late Lord Rayleigh, problems, problems and still more problems, form the royal road for mathematical progress.

The minimum course set out in the report is:—

Algebra. Permutations and combinations, the binomial theorem.

Plane trigonometry. Solution of triangles.

Geometry. Cartesians in two dimensions, conic sections.

Calculus. Differentiation and integration of simple algebraic and trigonometric functions.

Mechanics. Statics, dynamics, hydrostatics, composition of vectors. Newton's laws, units and dimensions.

Formidable as this syllabus may appear to the practical man there are, I think, for the radio-electrician three important subjects missing. The limitation of geometry to two dimensions is decidedly harmful. We learn to think in two dimensions and most of our problems are three-dimensional. I once gave the following puzzle to a senior wrangler. "Make four equilateral triangles with six matches which must not be broken." At the end of half an hour he told me it could not be done. A working carpenter did it in five minutes. The wrangler's mind worked on the flat, the carpenter's in space.

Solid geometry should, I hold, go apace with plane geometry and the simplest and most natural method of treating solid geometry is with vector algebra, not cartesians. This course might possibly be replaced by one of practical carpentry or mechanics.

The second subject I would add is logarithms. There are occasions when our slide rule is not sufficiently accurate.

Logarithms also serve as an introduction to my third subject—imaginaries, invaluable in the treatment of alternating current. With a foundation of elementary logarithmic theory sufficient knowledge of imaginaries for practical purposes can be acquired in a few hours.

# RADIO DATA CHARTS—18

## Transmission and Phase Shift of RC Couplings

THE simple and familiar RC coupling is shown in Fig. 1. Let the output voltage of the first valve be  $E$ , and the voltage across the resistance  $R$  be  $e$ . Then:

$$\frac{e}{E} = \frac{R}{R - jX} = \frac{R^2 + jRX}{R^2 + X^2} \quad (1)$$

Where  $X = 1/2\pi fC =$  the reactance of the condenser at the frequency,  $f$ , in which we are interested. Taking the modulus of (1), we find

$$\left| \frac{e}{E} \right| = \frac{1}{\sqrt{1 + (1/2\pi fRC)^2}} \quad (2)$$

and this we may call the transmission factor. Thus if at any frequency the transmission factor is 0.9, then  $e = 0.9E$ . We may also be interested in the phase change through the coupling, and we can write this down at once from (1). It is

$$\phi = \tan^{-1} \frac{1}{2\pi fRC} \quad (3)$$

Thus we see that both the transmission factor and the phase shift depend only on  $2\pi fRC$ , so that an abac which multiplies  $f$ ,  $R$ , and  $C$  together can have scales graduated in terms of transmission factor and phase shift. This has been done, and the result is presented here. It has been left to the user to multiply  $R$  and  $C$  together. Given the value of  $RC$ , it is only necessary to join the corresponding point on the  $RC$  scale to the frequency required, and the transmission factor and phase shift are given simultaneously at the point where the ruler cuts the right-hand scales.

The uses of the chart will be obvious to anyone engaged in the design of audio amplifiers, but it may nevertheless be useful to remark a few of the more obvious uses. Besides the usual application to the design of audio amplifier couplings, the chart can be used for calculating bass cut in tone controls which are of this type. It is sometimes desirable—especially in high power public address systems—to limit the bass response of the amplifier to avoid overloading the speaker(s). If

By J. MCG. SOWERBY,  
B.A., Grad.I.E.E.

(By permission of the Ministry of Supply)

the required diminution in response at some frequency is fixed, the chart can be used to find the corresponding  $RC$  value. If this response is required to be variable, either  $R$  or  $C$  may be varied and the chart will perform the required calculations from which several response curves corresponding to different settings of the control can be laid off in a few minutes. The chart may also be of assistance in determining suitable constants for loudspeaker dividing networks of the simplest possible  $RC$  type, though the more complicated networks covered by Chart No. 10 in this series would give a better performance. In designing amplifiers for electro-medical and CRT recording work,

less than one when the fed-back signal is in phase with the input signal. This demand may not be met at some low, or some high frequency; and if it is not, then oscillation or other instability will result. At the low frequency end, most of the phase shift is usually contributed by the couplings, and it is hoped that the information given by the chart will save time in calculations concerning possible instability in such amplifiers. The chart may also be of use when frequency selective negative feedback lines are used.

**Example 1.**—A three-stage high-gain amplifier for oscillographic work (gain 100,000 times at 1,000 c/s) has two couplings whose  $RC$  value (or time constant) is 0.025, consisting of 0.1  $\mu\text{F}$  condensers and 0.25 megohm grid leaks. What is the gain and phase shift at 30 c/s?

Join 0.025 on the  $RC$  scale to 30 c/s. The ruler cuts the transmission factor scale at 0.979, and the phase shift scale at 11.95°. Hence the amplifier gain at 30 c/s will be  $0.979 \times 0.979 \times 100,000 = 95,800$  (4 per cent. low) and to all intents and purposes the phase shift will be 24°.

**Example 2.**—A feedback amplifier is required to have a phase shift not greater than 5° per stage at 50 c/s. What is the necessary  $RC$  value, assuming that all the phase shift takes place in the couplings?

Join 5° on the phase shift scale to 50 c/s and the ruler cuts the  $RC$  scale at 0.0364 which is the required minimum value. Condensers of 0.075  $\mu\text{F}$  and grid leaks of 0.5 megohm might well be suitable for the couplings.

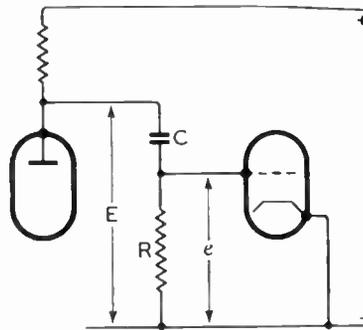


Fig. 1. Essential elements of a resistance-capacity coupling.


a very low frequency response (down to 1 or 2 c/s) is sometimes required, and the frequency scale of the chart is consequently extended to cover these requirements.

The phase-shift scale will, it is hoped, be useful to those concerned with negative feedback amplifiers. Nyquist's<sup>1</sup> criterion of stability in a feedback amplifier demands<sup>2</sup> that the loop gain of an amplifier (i.e. input, through amplifier, through feedback network, and back to input) shall be


<sup>1</sup>H. Nyquist. "Regeneration Theory." *B.S.T. Journ.* 11, p. 126. (1932.)

<sup>2</sup>Nyquist's criterion of stability is correctly stated: "Plot plus and minus the imaginary part of the fed-back vector against the real part for all frequencies from zero to infinity, with the feedback line open-circuited at the input, and for an input of  $(1 + j0)$ . If the resultant curve does not enclose the point  $(1 + j0)$  the amplifier is stable." The simplified version given in the text above is correct in most practical cases. It does not, however cover the case (for example) of the "nyquist" or "conditional" amplifier in which a reduction of gain leads to instability.

ABAC No. 18  
[Third Series]

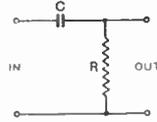

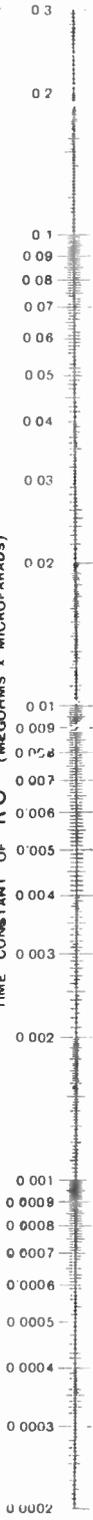
TIME CONSTANT OF RC (MEG OHMS x MICROFARADS)




FREQUENCY IN CYCLES PER SECOND



TRANSMISSION FACTOR

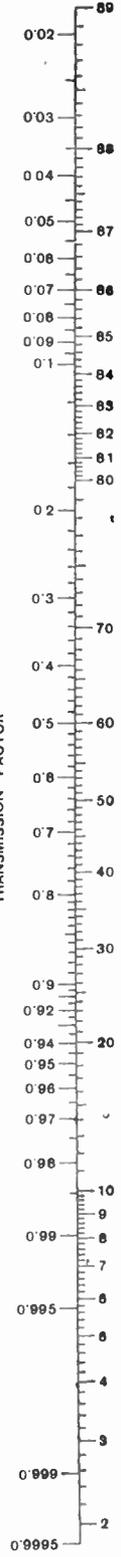

PHASE SHIFT IN DEGREES

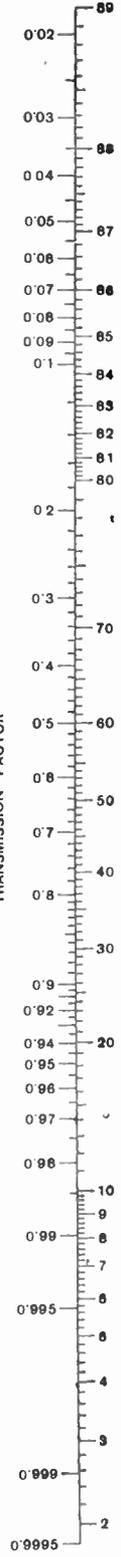

TRANSMISSION AND PHASE SHIFT OF RC COUPLINGS

Wireless World  
COPYRIGHT

# UNBIASED

## Horrors of Peace

THE British Interplanetary Society has always commanded my greatest respect because its work, like my own, lies so far above the heads of ordinary men. It is hardly to be expected, however, that the members of the Society would have available to them the same sources of under-the-counter information as myself and I do not think that they can be aware of the advanced stage which has been reached for the post-war commercial exploitation of the radio potentialities of V<sub>2</sub>, to certain aspects of which Arthur C. Clarke, a member of the Society, draws our attention in a letter published in the February issue of *Wireless World*.

Mr. Clarke tells us that by greatly increasing the speed of V<sub>2</sub>, we could have, circling round the earth for ever, an artificial satellite. After suggesting that this will be accomplished within a decade or so, he goes on to state that in perhaps half a century we shall be able to have in the sky three V<sub>2</sub> contraptions which would, relative to the Earth, be securely anchored in one position, and that these could be used as microwave relay stations to provide television and sound coverage for the whole of the Earth's surface.



"Under-the-counter information."

This information is, as far as it goes, thoroughly sound and reliable, but what Mr. Clarke does not tell us in his letter is that certain business interests which in pre-war days used to give, from well-known con-

By  
**FREE  
GRID**

●  
Cimex Radionis.


tinental stations, indelicate details of our internal anatomy in order to warn us of the awful fate awaiting us if we did not purchase their wretched pills and potions, are preparing to take the field on a far grander scale. They are, in fact, planning to launch into the firmament a veritable flock of these devilish devices, each completely equipped with transmitter and an almost endless supply of recorded programmes and advertising propaganda, the latter being made possible by the enormous strides made in microfilm technique.

The danger is a very real one, since once these things are in the air they would stay there for ever, the only limitations of their life being ordinary wear and tear of the moving mechanical parts of the reproducing apparatus; this, of course, can be reduced to a negligible amount by modern technique. All needed electrical power can, as Mr. Clarke rightly points out, be derived indirectly from solar energy.
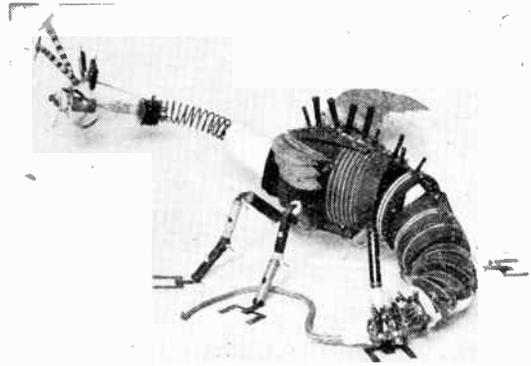
## Freud Had a Word For It

WE frequently hear it said that no matter how great and famous or how erudite and learned a man is, he will always be found to possess human weaknesses like ourselves. If the history books are to be believed, even Judge Jeffreys, who earned undying fame at what the B.B.C. would no doubt call the Sanguinary Assize, had a tender spot in his heart for cats; so much so that on one occasion when he had sentenced a man to be hanged, drawn and quartered, he mercifully changed the quartering part of the sentence to halving on hearing that the prisoner was a fellow felophile.

In spite of all this I cannot say that I had ever experienced any personal proof of this human trait in the lives of the great until fairly



recently when I went by invitation to the works of one of the few wireless companies (maybe the only company) which can claim to have been actively engaged in business during the reign of Queen Victoria. Actually, I believe, they fitted the Royal yacht with a wireless installation in 1898. Of course, in those far-off days wireless was merely a matter of telegraphy, and it was not, therefore, one of the B.B.C.'s programmes which drew the famous "We are not amused" from the lips of the Queen.

As I passed through the famous portals and tripped clumsily over a discarded "maggie" in the vestibule, nostalgic memories of the "naughty 'nineties" came back to my mind. When I was ushered into the presence of the great by an attendant fairy who took my card, I half expected to hear the irritating tapping of the decoherer and to see long-forgotten faces in the room into which I was shown. I had, at any rate, expected to be confronted by grave and reverend seigneurs bending with unhuman seriousness and cold and calculating scientific mien over the modern counterparts of the 10-inch coil and coherer.

As I entered the room my expectations were, with one exception realised. The grave and reverend seigneurs were certainly there, and they were, in truth, bending with all seriousness over an object on the table which I at once took to be the *dernier cri* in the world of wireless wizardry. I was astounded, therefore, when I saw the object to which one of them was just putting the finishing touches. I promptly asked and received permission to photograph it and reproduce the result here for your benefit. I can only suppose that it is one more piece of evidence of that peculiar trait in the character of the great and learned to which I have already referred. Freud would, no doubt, have a word for it; so have I, but the Editor won't let me use it.

# "IT CAN NOW BE REVEALED . . ."

## Some Achievements of the British Radio Industry

Thanks to a relaxation of censorship rules, it is now possible to write more freely on some of the outstanding contributions of wireless during the war. Although the full story cannot yet be told, we are, for example, able to publish articles on the principles and origins of radiolocation. Last month, at the inaugural luncheon of the Radio Industry Council, F. B. Duncan, the chairman, referred to a number of topics that have hitherto been banned. Relevant extracts from Mr. Duncan's speech are printed below.

IN actual use in the war, the story of the results we [the British radio industry] helped to make possible begins with the Battle of Britain. Radiolocation gear enabled men on the ground to detect and plot the course of enemy aircraft from miles away. The enemy suddenly realised that the British Nation was one scientific jump ahead of him.

From this first result our scientists, designers and technicians have strained every nerve to invent and perfect new gear. Every anti-aircraft gun-site and every searchlight in this country was equipped with special type radiolocation which reduced the human error in sighting. New findings enables British naval vessels to be the first in which dead-accurate gun-laying was assisted by radio beam. In 1941 an Italian fleet off Matapan was blasted from the sea by the guns of British cruisers and destroyers aided by radiolocation in pitch darkness. Last year the *Scharnhorst*, the proud boast of Germany, was sunk at an incredible range of many miles by battleship gun-fire dead on the target, with the help of still more advanced radiolocation gear.

By the second year of war night fighters were led by a ground control to enemy aircraft. The destruction of the night bomber was made possible largely due to this and the uncanny searchlight accuracy. As our attacks grew by further development bomber aircraft were directed unerringly to their targets.

D-Day saw the most pregnant development of all when new and special types of radiolocation enabled our airborne and parachute troops to be accurately concen-

trated by radio on minute landing areas in darkness. No other means could have kept in contact and prevented the dispersal of forces so large as those involved.

To-day, pin-point aerial bombardment is assured by the recently disclosed "black box" which gives the bomber pilot an ever-changing picture of the earthly scene below him, so that neither darkness, nor cloud, nor fog obscures the target from him.

Probably the best single contribution from British engineers will ultimately prove to be an item to which we cannot now give a name. It is a vacuum device, something infinitely more than a valve, of such delicacy and complexity that only the most skilful hands can make it. This is the heart of many of the most advanced types of radiolocation gear, permitting effective operation on very high frequencies.

After the war it will be directly applied to automatic and infallible anti-collision devices, which will ensure the safety of ships and aircraft all over the world's traffic routes.

I could continue to tell you of the many applications of radio gear to tanks, ships, aircraft, which amount to stupendous totals, some of which are clearly indicated in the recently published White Paper, but it would still be impossible for me to give you a proper picture of the complicated technical and engineering work that has been done in our valve, component and equipment factories, but when it is fully told it will stand as a lasting monument to the British radio industry . . . its technicians, and its workpeople. . .

# GALPINS

## ELECTRICAL STORES

"FAIRVIEW,"  
LONDON ROAD, WROTHAM,  
KENT.

TERMS: Cash with order. No C.O.D.  
All prices include carriage or postage.

**ELECTRIC LIGHT CHECK METERS**, first-class condition, electrically guaranteed, for A.C. mains, 200/250 volts 50 cy. 1 phase 5 amp. load, 11/- each.

**SOLID BRASS LAMPS** (wing type), one-hole mounting, fitted double contact, S.B.C. holder, and 12 volt 16 watt bulb. 4/-.

**TUNGSTEN CONTACTS**,  $\frac{1}{8}$  in. dia., a pair mounted on spring blades, also two high quality pure silver contacts,  $\frac{1}{8}$  in. dia., also on spring blades, fit for heavy duty, new and unused. There is enough base to remove for other work. Set of four contacts, 4/-.

**ROTARY CONVERTER**, input 40 volts D.C. output 75v., 75 m/A, A.C., also would make good 50v. motor or would generate. 22.

**AUTO TRANSFORMERS**. Step up or down tapped 0-110-200-220-240; 1,000 watts. 25.

**POWER TRANSFORMER**, 4kW, double wound, 400 volts and 220 volts to 110 volts, 50 cycle, single phase. Price 220.

**AUTO TRANSFORMER**, step up or step down 500 watts, tapped 0-110-200-220-240 volts. 23 10s.

**1/2 WATT WIRE END RESISTANCES**, new and unused, price per doz., 5/-, our assortment.

**MOVING COIL AMPMETER** by famous maker, 2in. dia., flush mounting, reading 0-10 amps., F.S.D., 20 M/A, price 27/6.

**AMPLIFIER COMPONENTS** from dismantled American 10 and 20 watt amplifiers, all metal cases and compound filled.

**INPUT TRANSFORMERS**, ratio 12 to 1, centre tapped, price 15/-.

**P.P. OUTPUT TRANSFORMER**, ratio 6.2 to 1, centre tapped, price 10/-.

**POWER TRANSFORMER**, pri. 95/100 v., sec. 200-0-200 at 80 M/A, also 5 v. at 3A, price 12/6.

**METAL RECTIFIERS**, size 14 x 3 $\frac{1}{2}$  x 3 $\frac{1}{2}$  in., output 50v., 1 amp., 35/-; another 5 $\frac{1}{2}$  x 2in., output 100v.-250 M/A, 17/6; another 200v.-50 M/A, 10/-.

**CABINET LOUDSPEAKER**, for extension only, 5 watt output, 8in. dia. cone, high quality, size of cabinet 10 x 14 x 8 $\frac{1}{2}$  in. x  $\frac{1}{2}$  thick, cabinet slightly marked at top, price 23.

**SMALL M.L. ROTARY CONVERTER**, in cast alli. cas., size 14 x 4 $\frac{1}{2}$  x 4 $\frac{1}{2}$  in., permanent magnet fields, converters need attention, not guaranteed, 30/-.

**POWER TRANSFORMER**, suitable for arc welding, input 230v., 50 cycle, 1 PH, output 50 volts at 200 amps., price 217; ditto, output 150 amps, 215; ditto, output 100 amps, 212.

**METAL RECTIFIER**, output 6v.-1 amp., 12/6; ditto, output 500v.-120 m/A, 30/-; ditto, output 200v.-100 M/A, 17/6.

**TRANSFORMER** for rewinding only, approx. 2kW, weight complete with clamps, 45 lbs., price 30/-.

**BLOCK CONDENSERS**, 4 MF, 300v., AC working, 6/-.

MOVING COIL AND M.I. METERS.

FOR FULL DETAILS OF ABOVE AND OTHER GOODS, SEND FOR LIST, 2jd.

# WORLD OF WIRELESS

## COMMONWEALTH BROADCASTING

**M**ANY problems on both the technical and the programme side of Commonwealth broadcasting can best be solved by round-table discussion, and when the European war ends the character of the broadcasting interchanges between countries of the British Commonwealth will entirely change. It is to discuss these common problems and to explore the field of post-war cooperation that representatives of the Dominion broadcasting organisations are now meeting in London. The delegates will also exchange information, experience and ideas on many professional matters such as technical developments, programme technique, controversial broadcasting and school broadcasting.

During the Conference, which began on February 15th and closes on March 9th, the delegates will visit many B.B.C. establishments throughout the country.

Among those attending the Conference are: Howard B. Chase, chairman, and E. L. Bushnell, Canadian Broadcasting Corporation; Col. C. J. A. Moses, general manager, Australian Broadcasting Commission; Prof. J. Shelley, director, and J. R. Smith, chief engineer, New Zealand National Broadcasting Service; Major R. S. Caprara, director, South African Broadcasting Corporation; N. Filmer, branch manager, and H. Collett, divisional engineer, Transvaal Division of S.A.B.C.; Prof. A. S. Bokhari, director general, C. W. Goyler, chief engineer, and S. Gopalan, development and planning officer, All-India Radio.

## "NO NATIONAL BOUNDARIES"

**T**HE chief of the Telecommunications Division of the U.S. Department of State, Francis Colt de Wolf, addressing the 33rd annual meeting of the American Institute of Radio Engineers, stated that for the past two years they had been working on plans for post-war telecommunications. He said that in formulating their plans they had in mind a modernisation of the existing international telecommunication bodies, bringing them more in line with the necessities of present-day radio, particularly in the field of radio interference and radio regulation.

He stressed the need for deciding whether they were "prepared to surrender a certain modicum of sovereignty to insure a more efficient control of radio, for radio knows no national boundaries."

Mr. de Wolf announced that the

third Inter-American Radio Conference would be held in Rio de Janeiro in June.

## APPOINTMENTS BUREAU

**A**S a result of meetings between representatives of the Institutions of Civil, Mechanical and Electrical Engineers, it has been decided to form a Professional Engineers' Appointments Bureau. The complementary objects of the Bureau are to provide employers with a source from which they can obtain the services of qualified civil, mechanical and electrical engineers and to afford members of the three institutions a means of introduction to prospective employers.

The Bureau will be administered by a Board consisting of the president, secretary and three members of each of the institutions. It will not be run for profit, and will be operated apart from the three institutions.

It is anticipated that the Bureau will ultimately become self-supporting, but an appeal has been made for donations to start a fund to carry it through the formative years.



**FARADAY MEDALLIST.** Dr. C. C. Paterson, O.B.E., F.R.S., has been awarded the Faraday Medal by the Institution of Electrical Engineers for conspicuous services rendered by him in the advancement of electrical science, particularly in the field of electrical research. Dr. Paterson, who has been director of the G.E.C. Research Laboratories since its inception, is a past president of the I.E.E., and was elected a Fellow of the Royal Society in 1942.

## RADIO OFFICERS

**F**OLLOWING the recent question in the House of Commons on the surplus of marine radio officers, enquiry was made of the Radio Officers' Union regarding the present situation. It was learned that there are enough men in the Merchant Navy Reserve Pool to meet present requirements, and, moreover, that the intake of radio officers without previous seafaring experience has practically ceased.

In reply to the question in the House, the Postmaster-General stated that the wireless telegraphy schools were advised last June that the present situation was foreseen. He also pointed out that the granting of the P.M.G.'s certificate carries no guarantee of employment.

## CANADIAN SHORT WAVES

**F**URTHER details are now available of the test transmissions from Canada's new short-wave station at Sackville, New Brunswick. Transmissions on 15.22 and 17.82 Mc/s are radiated on weekdays from 1045-1315 and on Sundays from 1130-1715 GMT.

Reception reports are still required and should be sent to A. E. Powley (not Porter as stated last month), Canadian Broadcasting Corporation, 32, Great Castle Street, London, W.1.

The official opening date of the station has been postponed until March 10th.

## ATHENS RADIO

**W**ITH the reopening of the Athens wireless telegraph station on January 29th for Press traffic, another chapter in the short history of this station opens.

Cable and Wireless established direct wireless communication between London and Athens in 1940. Short-wave listeners will remember that soon after the Athens station was opened it was adapted for telephony and used for a short period each evening to transmit news bulletins in foreign languages. From the occupation of Greece in April, 1941, until its liberation from the German Forces in October last year the station was closed.

During the internal strife in December the station, which is at P'allini, some eight miles from the capital, was cut off from Athens except for an underground cable. The power supply was cut, but the transmitter was operated from an emergency source, and supplies were dropped to the besieged staff and garrison by parachute.

On December 30th the E.L.A.S.

attacked the station and simultaneously cut the underground cable. Although under fire and with one of the engineers wounded, one transmitter was maintained so that a message could be sent to the Athens H.Q. via London giving news of the attack. The staff was later ordered to immobilise the station and prepare to leave. In an hour thousands of pounds' worth of valves was destroyed.

The station was occupied by E.L.A.S. for only eight days.

**SUBSCRIPTION TELEVISION**

THE possibilities of introducing a subscription television service is discussed by the president of the Scopphony Corporation of America.

The Scopphony programme would be confined to subscribers by a system of scrambling.

Subscribers would receive a celluloid or paper "pattern" which would be inserted in the unscrambling device. The "pattern" transmitted by Scopphony stations would be changed periodically.

**U.S. WAR SURPLUS**

THE recent correspondence appearing in *Wireless World* on the disposal of war surplus equipment raises interesting comparisons with American schemes.

Plans have been made whereby manufacturers act as "disposal agents" for surplus Government apparatus. This presumably applies to unused apparatus only as the plan provides for the manufacturer-agent to sell his own products for the Government-appointed Defence Supplies Corporation on a "commission basis."

**WHAT THEY SAY**

**RADAR: A WINNER.**—In 1940 it became clear that the country most advanced in radar would win the war. This country up to the laboratory stage, was the most advanced in the world. But it was not much good having a great laboratory unless you had the craftsmen.—*Mr. Bevin, Minister of Labour, recalling response of radio men to operate Radar.*

**COMPARISONS ARE ODIUS.**—In view of the larger number of pre-war sets purchased in England, that country may resume television on pre-war standards, but the British may emerge with a television system which might set the pace for the rest of the world, except for the single American advance of colour. . . . The British . . . have not produced a practical full-colour system. . . . Thus the United States seems to be in the enviable position of having world leadership in television at its finger-tips.—*Paul W. Kesten, C.B.S. Executive Vice-President, speaking on his recent visit to England.*

**LARGE-SCREEN TELEVISION.**—It will be our policy, as soon as circumstances permit, to develop a television unit displaying a screen about 3ft. by 2ft. and introducing colour, with the further aim of producing, as before the war, a large unit suitable for public entertainment, but with the addition of the use of colour. We do not for a moment suggest that such units can be brought to the point of satisfactory commercial exploitation without a considerable period of development.—*Sir Maurice Bonham Carter at the Annual General Meeting of Scopphony Ltd.*

**HIGH POTENTIAL.**—The threat to drive [U.S.] television off its present familiar channels into the UHF and to delay video by five years or more, is actually a threat to delay employment—to hold up jobs for 600,000 people, post-war, at a time when jobs will be so vitally needed. . . . Television, if continued on its present channels, has a potential employment-creating value at least equal, if not double, that of present radio-broadcasting.—*"Electronic Industries," New York.*

**TECHNICAL TACTICS.**— Formal science, by theory and experiment, opens a bridgehead on the industrial front; the bridgehead is enlarged by the oriented empiricism of good technical practice; and the gains are consolidated by further applications of formal science.—*Sir Robert Watson Watt, discussing the interplay of formal science and practical radio development, at the British Association Conference on the "Place of Science in Industry."*

**U.S. CIVILIAN SETS**

IT is announced by the Radio and Radar Division of the American War Production Board that "there is no possibility in the near future of making any new civilian sets, in view of military demands." Moreover, replacement components and valves are being manufactured in a limited quantity—sufficient to keep "an average of one set in operation in each radio-equipped home!"

**PERSONALITIES**

**Dr. William L. Everitt** has been elected president of the American Institution of Radio Engineers. He was recently appointed head of the department of electrical engineering at the University of Illinois, but at present is on war work as Chief of the Operational Research Branch, Office of the Chief Signal Officer, U.S. Army. His research work has been mainly concerned with high-power radio amplifiers and impedance-matching circuits. He is the author of "Fundamentals of Radio."

**Dr. Peter C. Goldmark** has been appointed Director of a new depart-


**CRONAME**  
RADIO COMPONENTS



**MILITARY** demands on the electronics industry require large quantities of material made to precision standards never before approached by quantity production methods. Crowe has had signal success in solving problems of rapid production of precise electronics control mechanisms. This experienced ability will be an important factor in the post-war programmes of many firms.

*Exclusively Represented in Great Britain by*  
**FRANK HEAVER LTD.**  
Kingsley Road, Bideford, N. Devon.

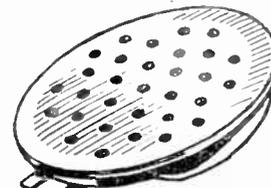**CRONAME INCORPORATED**  
(formerly Crowe Name Plate Mfg. Co.)  
CHICAGO, ILL. U.S.A.



H.A.5 DEAF-AID  
CRYSTAL MICROPHONE

**ASTATIC** will be ready to serve you again with high quality piezo-electric devices when the 'All-Clear' of Victory sounds. Astatic deaf-aid microphones can be supplied only if Import Permits are established. Model H.A.5 illustrated is used as standard by America's leading hearing-aid instrument makers.

**ASTATIC**

THE ASTATIC CORPORATION  
CONNEAUT, OHIO, U.S.A.  
and  
TORONTO, CANADA.

—Exclusively Represented by—  
**Frank Heaver Ltd.** Kingsley Road, Bideford, N. Devon

**World of Wireless—**

ment of the Columbia Broadcasting System, that of Engineering and Research.

L. A. Hooke, who has succeeded Sir Ernest Fisk as Managing Director of Amalgamated Wireless (Australasia), Sydney, has been General Manager since 1936 and associated with the company since its incorporation in 1913.

David Sarnoff, President of R.C.A., who was recently awarded the Legion of Merit, has been promoted from the rank of Colonel to Brigadier General.

Paul A. Porter has been appointed chairman of the U.S. Federal Communications Commission in succession to James L. Fly, who has retired.

N. K. Bunn (Works Manager) and J. L. Harvey (Production Manager) have been appointed Joint General Works Managers of British Insulated Cables. W. J. Clements is appointed Works Manager.

C. A. Edgell, whose appointment as Sales Manager of British Mechanical Productions (Clix radio components) is announced, has for nearly three years been Administrative Manager of the Company's factories concerned mainly with the production of radio components.

**OBITUARY**

It is with regret we record the following deaths.

K. L. Wood, who joined the Eastern Telegraph Co. (later taken over by Cable and Wireless) in 1899, retiring from the position of Engineer-in-Chief in 1939, died on Feb. 4th, aged 61.

F. R. S. Balfour, who died recently, aged 71, was director of many companies, including Cable and Wireless, Marconi International Marine Communication Co., and Marconi Sounding Device Co.

N. S. Holland died on January 22nd. He resigned from his position as director of A. C. Cossor last year owing to ill health.

Dr. Walter Weber, chief engineer of the technical department of the German Broadcasting Company, has died recently. He was responsible for many improvements in German transmitting apparatus and carried out important research on the interference method of measuring non-linear distortion, and the high-frequency magnetophone—an important advance in the technique of magnetic recording.

**IN BRIEF**

**FM Growth.**—When last we reported the number of applications for FM stations awaiting decision by the U.S. Federal Communications Commission, which was in July, the figure was 190. It has now increased to over 300.

**Anglo-U.S. Co-operation.**—The President of the Radio Executives' Club of New York recently presented on behalf of its members a scroll to the B.B.C. "in appreciation of its unstinting co-operation with American broadcasters, networks and independent stations to make complete the coverage of the war, and for inspiring radio throughout the world to become a powerful voice which will declare ever loudly for all

the people their desire for everlasting peace."

**B.B.C. Monitoring Service** recently produced the 2,000th issue of *Digest of World Broadcasts*. This *Digest* is Britain's largest daily publication, translating into English the broadcasts received in 32 different languages. A million words a day are heard from stations all over the world; by eliminating repeat broadcasts and selecting the required material this is reduced to 300,000 words. This is cut and edited down to some 100,000 words, comprised in the *Digest*, which is produced on seven days a week.

**Canadian R.T.P.B.**—Canada, like its neighbour the U.S., has appointed a Radio Technical Planning Board. Panels, or committees, have been appointed to study specific aspects of radio, such as FM, television, international SW, radiotherapy, industrial electronics and standard broadcasting, from whose reports recommendations will be made to the Dominion Government for international consideration.

**Phototelegraphy.**—During the three months ended in November more than 340 photographs were sent by radio from London to Buenos Aires. Cable and Wireless states that reception of 86 per cent. of the transmissions was reported "good."

**Leicester Radio Society** has been successfully restarted and at their next meeting, on March 6th, A. Folwell, the secretary, will give a demonstrated talk on cathode-ray tubes. A further meeting of the society is to be held on March 20th, when S. May will lecture on "The Spectrometer and its Applications." Both meetings commence at 7.30 at the United Baptist Chapel, Charles Street, Leicester.

**M.M. for Radio Operator.**—The Military Medal has been awarded to L.A./C. Ranger, R.A.F.V.R., for maintaining communications between the R.A.F. headquarters in the Epirus area of Greece and Cairo. Eighteen months ago he landed in Greece by parachute and was placed in charge of a radio set. On two occasions during the fighting he dismantled the set under fire and played a leading part in saving the equipment and preventing casualties.

15,000 tons of waste paper are urgently needed for use in the manufacture of wall board to repair houses damaged by enemy action.

**MEETINGS****Institution of Electrical Engineers**

*Radio Section.*—"Frequency Modulation," by K. R. Sturley, Ph.D., B.Sc., March 7th.

"Colour Television," discussion to be opened by L. C. Jesty, B.Sc., March 13th.

"Apprenticeship and Trainee Systems in the Radio Industry," discussion to be opened by J. Greig, M.Sc., Ph.D., March 20th.

All these meetings will be held at 5.30 at the I.E.E., Savoy Place, Victoria Embankment, London, W.C.2.

*Cambridge Radio Group.*—"Multipath Interference in Television Transmission," by D. I. Lawson, M.Sc., March 13th, at 6 o'clock at the Technical College, Collier Road, Cambridge.

"The Design and Manufacture of Radio Valves," by G. Liebmann,

Ph.D., March 27th, at 7 o'clock at the University Engineering Department, Trumpington Street, Cambridge.

*South Midland Radio Group.*—"An Elementary Description of Some Molecular Concepts of the Structure of Dielectrics," by E. B. Moullin, Sc.D., at 6 o'clock at the James Watt Memorial Institute, Birmingham, on February 26th.

*London Students' Section.*—"Mercury Arc and Mercury Vapour Rectifiers in Transmitters," by T. M. Ellison, March 5th, at 7 p.m. at the I.E.E.

**British Institution of Radio Engineers**

*London Section.*—"Dielectric Heating by the Radio Frequency Method," by L. Grinstead, at 6 o'clock at the Institution of Structural Engineers, 11, Upper Belgrave Street, London, S.W.1, on February 28th.

*Midlands Section.*—"Magnetic Dust Cores," by E. R. Friedlaender, at 6 o'clock at the University of Birmingham (Latin Theatre), Edmund Street, Birmingham, on February 28th.

*North-Eastern Section.*—"Proposals for Television and Broadcasting Transmission Systems," by W. A. Beatty, at 6 o'clock in Neville Hall, Newcastle-on-Tyne, on March 14th.

**Royal Society of Arts**

"The Making of a Gramophone Record," by H. W. Bowen, on March 21st, at the Royal Society of Arts, John Adam Street, Adelphi, London, W.C.2, at 1.45.

**Royal Institution**

"Some Aspects of Pre-War and Post-War Television," by H. I. Kirke, on March 2nd.

"Is Human Speech Good Enough," by Sir Richard Paget, on March 23rd.

Both meetings commence at 5 o'clock at the Royal Institution, 21, Albemarle Street, London, W.1.

**Institution of Electronics**

*North-West Branch.*—"Pulse Generation," by Dr. F. J. G. van den Bosch, on March 23rd, at 6.30 at the Reynolds Hall, College of Technology, Manchester.

**Institute of Physics**

*Electronics Group.*—"Electron Diffraction," by G. I. Finch, F.R.S., on March 6th, at 5.30, in the small Physics Theatre, Imperial College of Science and Technology, Prince Consort Road, London, S.W.7.

**Television Society**

Annual General Meeting, followed by a discussion on "Some Social Aspects of Television," opened by Capt. C. H. Cazaley, R.E.M.E., on March 27th, at 5.30 at the I.E.E., Savoy Place, Victoria Embankment, London, W.C.2.

**City and Guilds Radio Society**

"Harmonic Analysis at Very-High Frequencies," by D. M. Tombs, M.Sc., on March 2nd.

"The Transmission of Television Signals over Ordinary Non-loaded Telephone Pairs," by A. R. A. Rendall, Ph.D., on March 9th.

"Some Problems in Instrument Design," by F. E. J. Ockenden, on March 16th.

All these meetings will commence at 5.15 at the City and Guilds College, Exhibition Road, London, S.W.7.

Letters to the Editor

Technical Training Criticisms • Books: Good and Bad • What is "Static"?

"Radio Engineering Education"

IN the February issue of your paper appeared an article on "Radio Engineering Education," by Thomas Roddam, who makes an outrageous criticism of the polytechnics, which he regards as bad and sterile. He remarks that a large proportion of recruits to the industry are coming from the polytechnics and from Hankey courses in the Universities.

Mr. Roddam's knowledge of the educational facilities in this country is lamentable, as there happen to be polytechnics only in the London area, and I do not believe that he really meant to criticise only those few institutions in the London area which bear the name of "polytechnic." In fact, his ignorance is so great that he is unaware that the provincial university which apparently meets his requirements was in all probability previously an institution exactly comparable with a polytechnic. Furthermore, Mr. Roddam's statement that a large proportion of to-day's recruits to radio are coming from the polytechnics obviously betrays his abysmal ignorance even of the radio industry, as it is quite well known that the large proportion of the people entering the industry have had no training whatever.

T. J. DRAKELEY.  
Association of Principals of  
London Polytechnics.

I AM very pleased to find the problems of education being thrashed out in the Press and agree by and large with your contributor Thomas Roddam. I think he is a little impatient, however, with the full- and part-time staffs of polytechnics and technical colleges who, despite their lack of contact with phenomenally rapid wartime developments and lack of experimental and more particularly measuring apparatus, were able to train tinkers and tailors as wireless and radio mechanics.

A suitable textbook is notice-

ably lacking, and as radio is entering many new fields I feel that a comprehensive survey could best be made by inviting contributions from accepted authorities in Government or industrial research laboratories to an outline drawn up by themselves and representatives of the teaching profession. The whole should be edited as regards technical and mathematical standard by someone with teaching experience.

J. W. BAYLISS.  
North Cheam, Surrey.

WITH respect to the training of future radio engineers, I say at once that I entirely agree with the views of Thomas Roddam, but I cannot agree with your Editorial view that the so-called "academic" education of engineers should be mixed up with training in industry. From my own experience and that of teaching electrical communication to students from first-year National Certificate to higher degrees in electrical communication, I am quite convinced that the best years for acquiring sound fundamental knowledge are between the ages of 15 and 21, and that none of this time should be unnecessarily wasted in picking up odd bits of information in a works. After the age of 21 it becomes increasingly difficult to appreciate fundamental knowledge. In works there is a general tendency to disregard the finer criticism of fundamental issues when a general line of least resistance of getting on with the job at all costs prevails.

These two points of view cannot be reconciled and if, at a much later age, you wish to have people in industry of high critical faculties, they should be left in a continuity of learning as long as possible. Short vacation courses in works can make better use of holiday times, no doubt, but it must always be remembered that students of Universities go into many avenues apart from industry, and to insist that all such



THE "FLUXITE QUINS" AT WORK

"When we're down off this roof—I'll be glad, My fingers are frozen, bedad!"  
Yelled EE "Hey! Hold tight!  
We'll need that FLUXITE,  
We're soldering—not ski-ing, m'lad!"

See that FLUXITE is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 30 years in Government works and by leading engineers and manufacturers. Of all Iron-mongers—in tins, 8d., 1/4 & 2/8.

Ask to see the FLUXITE SMALL-SPACE SOLDERING SET—compact but substantial—complete with full instructions, 7/6.

TO CYCLISTS! Your wheels will NOT keep round and true unless the spokes are tied with fine wire at the crossings AND SOLDERED. This makes a much stronger wheel. It's simple—with FLUXITE—but IMPORTANT.

The FLUXITE GUN puts FLUXITE where you want it by a simple pressure. Price 1/6, or filled, 2/6



ALL MECHANICS WILL HAVE

**FLUXITE**

IT SIMPLIFIES ALL SOLDERING

Write for Book on the ART OF "SOFT" SOLDERING and for Leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1d. each.

**FLUXITE LTD.**

(Dept. W.W.), Bermondsey Street, S.E.1

**Letters to the Editor—**

students, many of them destined to become research workers, should spend valuable years in works is a misleading policy.

L. E. C. HUGHES.

London, N.W.8.

**"Pity the Poor Student"**

I AGREE with Sqn. Ldr. A. M. Hardie that your reviewer "T. R." is to be congratulated for his courageous stand regarding the bad technical books which are now being published.

There is no short cut to scientific knowledge, and least of all to mathematical knowledge. Instead of wasting time and money in publishing new books, would it not be possible to reprint some of the old mathematical and scientific books which are far better than the modern ones.

I have in mind the books of Professor Augustus de Morgan, the greatest teacher of mathematics which this country has produced. It was left to the Open Court Publishing Company, of Chicago, to reprint, in 1898, his books on "The Study and Difficulties of Mathematics" and "Elementary Illustrations of the Calculus," which should be in the hands of every teacher and student of mathematics.

I suggest that some enterprising firm reissue his two small books on Algebra and Trigonometry. There are no better and clearer books in existence, although they were written some 100 years ago. As Professor de Morgan pointed out, mathematics, when taught as an art, has no value. To-day mathematics as a science is not taught at all, and least of all in the modern text-books.

LIONEL CALISCH.

London, S.W.5.

**AGC Circuit**

IN superheterodynes demodulation is sometimes achieved by circuits which do not lend themselves easily to the production of an automatic gain control voltage.

With such gear it has been found convenient to take off part of the IF, say, after the first IF amplifier, apply it to the triode portion of a double-diode-triode for magnification and subsequent detection in the diode portion of the same valve.

No trouble has been experienced with an inductive anode load, as the heavy damping of the diode across it prevented the triode from falling into oscillation. At the same time the anode-grid capacity was regenerative enough to give the valve a high input impedance, thus introducing very little damping into the attached associated circuit.


The valve is run on a self-biased cathode of 2-3 volts, this being the delay for the AGC diode. Medium-mu and medium high-mu valves have been used with advantage. The general picture of a set fitted with the new gadget is given in the diagram.

As was to be expected the

prevent racketeering, and the entry (as after the last war) of new speculators who merely buy and sell surplus material as such, and contribute nothing to the industry generally.

There are still left in the Trade a number of the old-time radio component dealers, who sincerely tried to give real service, both in war and peace. I suggest that these people, so many of them as are left, formed the real backbone of the radio industry in the early days, and went to great lengths to assist the enthusiast in every way, to foster his enthusiasm, and to make the material available as freely and as cheaply as possible.

R. H.

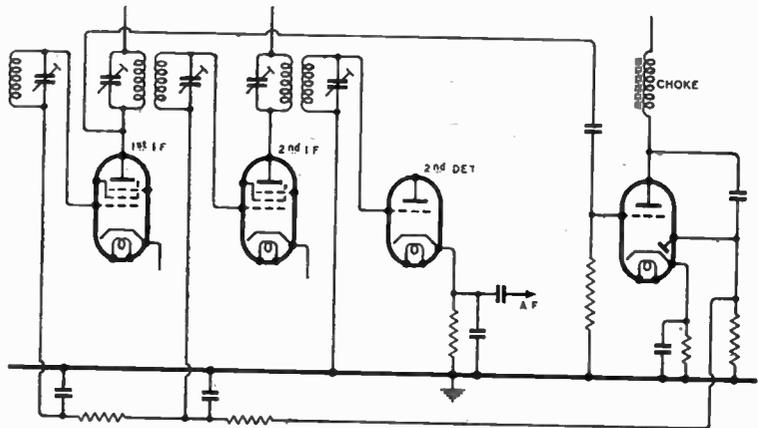

Circuit including AGC arrangement described by K. E. Marcus.

arrangement produced an "over control," as on strong signals the AGC voltage was far in excess of the AF voltage across the demodulator load, whilst on weak signals the AF output exceeded the control voltage. 40db fading gave no appreciable difference in sound intensity, apart from the well known "approaching" of the background noise.

K. E. MARCUS.

Uxbridge, Middx.

**War Surplus Disposal**

I HAVE read with interest the discussion in your columns about the disposal of war surplus equipment, and I should like to give as my view that it would be fairer in every way if the Government were to adhere to the original promise, expressed some months ago in the daily Press, to sell this equipment through the normal Trade channels, and thus

**Electric Lamp Failures**

BY a coincidence I had exactly the same experience yesterday as your contributor "K. G. B." (see p. 49 of the February *Wireless World*). The noise emitted was a fairly high-pitched hum, but the interference with a small receiver in the same room was sufficient to drown the local broadcast almost to extinction. The interference disappeared with the substitution of the lamp.

C. ATHERTON.

Manchester.

[This refers to the type of lamp failure where the glow from a broken filament is maintained by thermionic emission. In a footnote to "K. G. B.'s" contribution last month we expressed doubt as to whether serious interference with wireless reception could be caused by this kind of lamp fault. From the above letter and many others we have received it now

seems to be definitely established that such failures are in fact responsible for strong interference. —ED.]

**Justifying "Static"**

IN the November, 1944, number of *Wireless World* T. W. Bennington rightly deplors the use of the word "static" to describe radio noise produced by lightning flashes. But there is a proper and clearly defined use for "static" as distinct from "atmospherics." If we adopted a lightning conductor as a shunt-fed aerial, when local thunder-clouds were present there would be a soft corona discharge from the conductor, and it would be excited in its normal modes. A characteristic rushing or hissing sound would be received, and this noise would properly be called "static." Any aerial having a DC path to earth may behave in this way, although

the sharp point of a lightning conductor will increase the effect. An unearthed aerial, in the presence of high electrostatic fields, will charge up, and may reach a potential sufficient to "corona" to earth, if the condenser is sufficiently good to prevent leakage.

Another form of static may be produced in rubber-tired vehicles which can charge to sparking potentials as a result of the suction of the tyres on the road. This effect is well known in hospitals, and I believe that patients under anaesthetic have been known to explode when a spark has detonated the air-ether mixture in their lungs. The trailing chains behind petrol lorries are a familiar sight, and provide an earth leak for those charges.

I would urge that B.S.I. should canonise this use of "static," which in its common use is a redundant and confusing term.

THOMAS RODDAM.

**RANDOM RADIATIONS**

By "DIALLIST"

**Robust Radiolocation Gear**

TO me one of the greatest triumphs of our "secret weapon," radiolocation, is that these delicate and highly complicated instruments were so designed and made as to be able to stand up to the rough treatment of war. I frankly admit that when I first heard that it was intended to install them on A.A. gun-sights I thought that they would never withstand either the vagaries of the weather or the heavy vibration due to gunfire at close quarters. But they did, even from the first. It would be difficult to imagine conditions more trying to wireless gear of any kind than those which prevailed during the thaws following the cold spells of the early war years. With the melting of the snow the ground became a quagmire and the foggy air was so damp that one never seemed to have any possession that was really dry. You might have expected constant trouble with the radiolocation equipment, but we didn't have it; it just went on working. On many sites during the second half of 1940, when the Battle of Britain was toward, and the first half of the following year, the guns were constantly active, but so long as radiolocation apparatus received normal care and maintenance attention it seemed to be very little affected by

the vibration. That, I feel, is a real triumph and something more than a credit to those responsible for both design and construction.

**So Simple**

Another remarkable achievement was that the gear was made so simple to operate that it could be handled by intelligent men of the rank and file after a period of training. And not by men only, for by 1941 girls, most of whom had no previous knowledge or experience of electricity and electrical apparatus, were proving themselves to be highly competent radiolocation operators. My first impression of the inside of a radiolocation set was that it was about as complicated a box of tricks as one could want to play with. There are some pretty brain teasers amongst its ingenious circuits and some lovely mazes of wiring to puzzle out. But the actual operation is amazingly simple and complete novices; so long as they are of the right kind, take to it very quickly despite the (at first sight) formidable number of knobs and switches on the panels.

□ □ □

**In the Right Direction**

THE luncheon given recently by the Radio Industry Council to inaugurate the campaign which it is to undertake was a great success.



The new Vortexion 50 watt amplifier is the result of over seven years' development with valves of the 6L6 type. Every part of the circuit has been carefully developed, with the result that 50 watts is obtained after the output transformer at approximately 4% total distortion. Some idea of the efficiency of the output valves can be obtained from the fact that they draw only 60 ma. per pair no load, and 160 ma. full load anode current. Separate rectifiers are employed for anode and screen and a Westinghouse for bias.

The response curve is straight from 200 to 15,000 cycles in the standard model. The low frequency response has been purposely reduced to save damage to the speakers with which it may be used, due to excessive movement of the speech coil.

A tone control is fitted, and the large eight section output transformer is available to match, 15-60-125-250 ohms. These output lines can be matched using all sections of windings, and will deliver the full response to the loud speakers with extremely low overall harmonic distortion.

PRICE (with 807, etc., type valves) £18.10.0

Plus 25% War Increase

MANY HUNDREDS ALREADY IN USE

Supplied only against Government Contracts

**VORTEXION LTD.**  
 257, THE BROADWAY,  
 WIMBLEDON, S. W. 19.  
 Phone: LIBerty 2814

### Random Radiations—

Some 500 of us heard the chairman's account of what the industry has done so far during the war and his forecast of the part it will play when peace returns. The great point is that the industry has got together to let the public know something of its achievements and its intentions. The man-in-the-street may well have imagined that the industry has been asleep since September, 1939. His chief impression of its doings is that it hasn't supplied the new set that he wants and that it has been none too easy to get the old set repaired! He doesn't know, though he will soon when the Council gets into its stride, that the industry is more than two-and-a-half times as big today as it was when war came. Nor does he realise that the seemingly impossible has been accomplished over and over again in keeping pace with the ever-growing and almost insatiable demands of the armed Forces for radiolocation, wireless and electrical gear. Hundreds of acres of new factory space have been built; millions of pounds' worth of precision machinery has been installed, and the industry accomplished all this whilst having to release some of its best men to the Services and to fill its depleted ranks by training novices. The more apparatus the industry supplied to the Navy, the Army and the Air Force, the greater was the demand by them for trained men to operate and maintain it. As it was expanding rapidly all the time, the industry had to train some two-and-a-half novices for every skilled man it lost.

### The Future

This move to let people know what it has achieved and how well prepared it is to supply civilian needs after the war is an excellent one; I hope, too, that its original scope may be enlarged. I've always held that the public needed to be educated in the matter of wireless reception and wireless receivers, and now that the industry is to speak to us with one voice, here is a magnificent opportunity of doing something on these lines. As regards the future, we shall have immediately after the war the receivers that would have appeared in 1939/40. This is sound, for the designs are ready and they can be turned out quickly to meet the enormous demand that will occur. After that there should be interesting developments. I see no reason why the bigger and better set should not ultimately come into its own. Mass production should mean bigger output and smaller cost of valves and other components, and the industry has made immense strides during the

war in mass-production machinery and methods.

□ □ □

### An Interesting Tool

THE Bio Electric Company have sent me one of their Biobas electric soldering irons to try out, and I have made considerable use of it during the week before writing this note. It is not a midget iron suitable for fine work on instruments; it is in fact a light iron (the complete tool weighs about 14 ounces) such as one uses for general wireless jobs, with a bit of screw-driver shape just over a quarter of an inch in width. This iron has several interesting features, the most important of which is the novel and effective method of temperature control. The heater consists of two elements. The main element is made of an alloy which has something like a zero temperature/resistance coefficient; the special alloy used for the ballast element has a high and increasing temperature/resistance coefficient. The two are assembled into a kind of double sandwich between clamping plates. Thus the main element heats the other to approximately its own temperature, causing the total resistance to rise and fall in accordance with the heat conditions; that is, the electrical input is balanced against the heat output. In practice the control works well. I have left the iron idling for half an hour or more and found no noticeable rise beyond the working temperature. In use the temperature remains substantially constant whether the work one is doing calls for the heating of very small surfaces or comparatively large ones. The heater assembly can be withdrawn by removing one screw, and the heater elements changed if need be by removing and reinserting two other screws. Altogether a very satisfactory tool. It will not, I am told, be on the market until some time in March. Meantime I am trying to persuade its makers to produce a midget iron on the same lines.

□ □ □

### A Student's Experience

REFERRING to my notes in last month's *Wireless World* on the training of electrical engineers who wish to specialise in communications, a reader now serving with the R.A.F. sends me an account of his experiences of the course for the B.Eng. degree at one university. Having passed the intermediate, he settled down to work for Part I of the final examination, but found that in the course for this tele-communications were completely ignored. How, he asks, would a radio engineer benefit from a deep knowledge of the construction of

cranes, boilers, heat engines, chimneys, dams and roof trusses? It might be useful to him on rare occasions to know something of such things; but surely it is a work of supererogation to devote the time and energy needed to study them in detail. There was, he found, to be no real work in radio until the last year of the course. In disgust he turned in his student's exemption from military service and joined the Air Force. Really, I'm not surprised. This kind of thing must be most galling to a keen youngster. It is high time that the authorities of some universities at any rate realised the great and growing importance of radio—to say nothing of the vastness of the subject—and put their houses in order accordingly.

□ □ □

### A Singing Lamp

THE note by K. G. B. (February *Wireless World*) on the failure of an electric lamp was particularly interesting to me, for some time ago I came across a "singing" lamp that caused a perfect uproar of noise from the loudspeaker of a set in the same room. This lamp must have had a broken filament for some days. Here is what happened. I was spending the evening with some friends and at nine o'clock the set was switched on for the news. As its heaters warmed up horrible noises began to issue from the loudspeaker. The set, I was told, had been like that for a day or two; they had given up using it except for the news, which was just intelligible above the din. Then one member of the family said that she had tried it early that afternoon and found it absolutely as it should be. That gave me a clue: whilst the news was coming in I switched off the only light in use in the room, a pendant 100-watt bulb. Reception immediately became normal, the din starting again as soon as the lamp was switched on. There was no noticeable flickering of the light, but a distinct low singing noise could be heard when one's ear was near the lamp. A replacement was fitted and I asked to be allowed to take the faulty one home for examination.

### A Curious Break

When I came to have a look at it in daylight, I found a rather unusual state of affairs inside the bulb. It was an old lamp with a tungsten filament strung zig-zag between spoke-like supporting arms, each with a hook at its end. At first I couldn't find the break, but I spotted it at last with the help of a reading glass—luckily it was a clear bulb. The filament had given way at the very bottom of one of the

downward "zags" and the main part had either jammed itself in or become welded to the hook. The broken end was standing off only a tiny fraction of an inch from the hook. When the lamp was put into a holder and switched on the loose end of the filament could be seen vibrating. It was, I suppose, owing to the rapidity of the vibrations that there was no obvious flickering of the light. The broken end would be physically attracted to the hook as current increased in either direction and released at the minima. The most interesting and unusual point was that the lamp continued to function for so long and survived so many switchings on and off. Years ago, when that method of filament suspension was, if not the only method in use, at any rate the most usual, one could sometimes effect a repair when a filament broke between two hooks. You put the bulb on a table and turned it till the break was uppermost. A few sharp taps on the glass might, if you were lucky, make the broken ends overlap and when current was subsequently passed through the filament they would often stay put for some little time.

□ □ □

**Nae Bother at A'!**


WHY, I wonder, should the Saltire Society of Scotland be so anxious that Scots should have complete control of their own programmes? One of their suggestions is that the proceeds of all the Scots receiving licences should be handed over to a Caledonian Broadcasting Corporation, which would then assume entire responsibility. Well, the licence fees collected in Scotland amount to only about £400,000, and I shouldn't have thought that that would go very far. To the best of my recollection the peacetime Scottish Regional programme hadn't much of the Sassenach about it. But if they feel that they'd like to make the Scottish National really a Scottish National, why not say "It's nae bother, nae bother at a'" and hand it over? That would at any rate solve the problems of those Gaelic "hours" and news bulletins, which (if one dare breathe it!) were found rather a nuisance by southrons. There'd need be no need to tie the C.B.C. down to the £400,000; we could supply them gratis with any of our "piped" programmes that they liked to take.

**GOODS FOR EXPORT**

The fact that goods made of raw materials in short supply owing to war conditions are advertised in this journal should not be taken as an indication that they are necessarily available for export.

*It's the hidden details that count*

140  
Types  
in  
Production

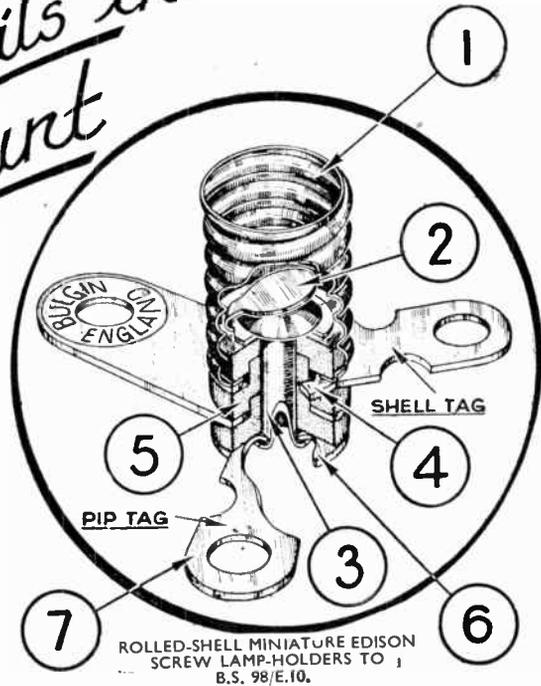

- 1 — Threaded shell with dimensions and details to B.S. 98—10 mm. "MES"; silver-plated finish.
- 2 — Central "pip"-contact of spring phosphor-bronze to ensure good contact; silver-plated.
- 3 — Central rivet of solid steel ensuring permanently tight and positioned assembly.
- 4 — Locking teeth on "shell"-contact solder-tag, ensuring contact and preventing unintended rotation.
- 5 — Stepped insulant-washers preventing short-circuit and permitting comparatively high-voltage working conditions.
- 6 — Toothed solder-tag locks to rivet-turnover, fixing position and ensuring contact to "pip"-contact.
- 7 — Dual-purpose soldering tags coated pure tin and accepting "threaded" or "wound" wiring; fixing bracket, normally "dead," may contact with shell and replace the "shell-tag."

**THE CHOICE OF CRITICS**



**A. F. BULGIN & CO. LTD., BYE PASS RD., BARKING, ESSEX**

RIPpleway 3474 (5 lines)


(The name "BULGIN" is registered Trade Mark)

# RECENT INVENTIONS

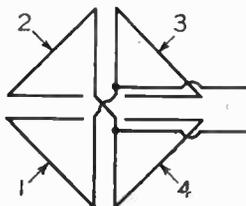
## RADIO BEACONS

**H**ORIZONTALLY polarised waves are generally used for marking out a short-wave navigational course from a beacon station, because they are less subject than vertically polarised waves to be re-radiated from the ground, or from the conductors normally found in the vicinity of an airdrome. This in turn makes it easier to give an unambiguous indication to the pilot.

The drawing shows an aerial system of this kind designed to provide four converging routes. Two pairs of antennæ A, B and C, D, elevated above ground, are arranged at the four corners of a square, the side of which is approximately half the working wavelength. Each unit consists, as shown separately, of two horizontal crossed dipoles 1, 3 and 2, 4, the conductors of each pair being energised in phase opposition. The overall length of a radiator is half a wavelength, but the outer ends are bent over, so that radia-



(a)

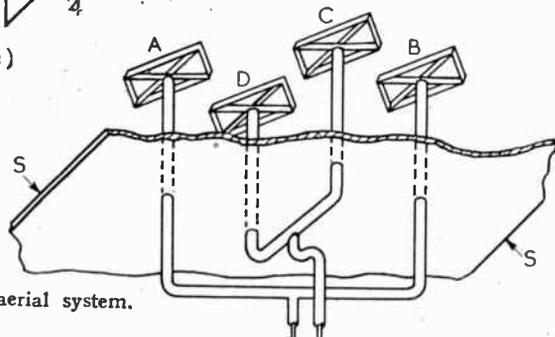

Beacon aerial system.

tion is effectively concentrated along the sides of each of the smaller squares, the usual "end-effect" of vertical polarisation being thus minimised.

One pair of units A, B is connected to the RF source in alternation with the other pair C, D through a switch (not shown) which is operated in the usual A-N sequence so as to apply interlocking signals to the two overlapping beams. A metal sheet S screens the aerials from the ground so as to prevent re-radiation from that quarter.

*Standard Telephones and Cables, Ltd. (assignees of A. Alfjord). Convention date (U.S.A.) October 19th, 1939. No. 563075.*

## APPROACH PATH BEAMS

**W**HEN waves of the order of three metres or less are used at an airfield for marking out an approach path, the effect of re-radiation from the steel and other metal work in the vicinity of the transmitter becomes pronounced and troublesome. The reflected waves are superposed on the

## A Selection of the More Interesting Radio Developments

direct energy of the overlapping beams and so produce undesired "field-patterns," which tend to blur the true straight-line path, and to create local "false" paths.

This so-called "scallop" effect is avoided, according to the invention, by deliberately wobbling the carrier-wave frequency of the beacon over a range of, say, one per cent. At any given point in space, the phases of the reflected waves will then vary differently from those of the direct beams, according to the individual space paths, but the instruments on the aircraft will respond only to the "average" pattern produced during each complete wobble. They will therefore correctly indicate the approach path marked out by the original beams.

*Standard Telephones and Cables, Ltd. (assignees of A. Alfjord). Convention date (U.S.A.) October 11th, 1939. No. 563076.*

sides of the oscillator. To prevent twisting or turning movements, two separate grips may be provided along one side of the crystal.

*Marconi's Wireless Telegraph Co., Ltd. (assignees of S. A. Bokovy). Convention date (U.S.A.) July 5th, 1941. No. 563139.*

## MICROPHONE "BACKGROUND" NOISE

**T**O ensure clarity, when broadcasting directly from a political meeting or other public gathering, the general background of noise should preferably be excluded from the line. One suggested way of securing this result is to use two separate microphones, connected in opposition, and spaced apart so that the more distant undesired noises are balanced out, whilst the voice of a nearby speaker is not.

The present invention is based on the assumption that the following features are essential to the successful operation of such a system: (a) The two microphones should be separated by a distance not exceeding a quarter of the wavelength of the highest frequency it is required to eliminate; approximately three-quarters of an inch is specified. (b) Both microphones should be non-directional. (c) Only sound apertures should be available, one for each microphone.

In one described arrangement, the two microphones are mounted on the inner faces of a baseplate which is bent into a wide-angled "vee," so that the voice of the speaker is mainly directed against only one of the pair.

*F. C. Beekly, Convention date (U.S.A.) December 26th, 1941. No. 563595.*

## MAGNETIC DUST CORES

**T**HE powdered-iron cores used for RF inductances are so brittle that they are liable to crack or break, either when being wound, or during the final heat treatment, when replacement is costly.

According to the invention, the cores are strengthened by including reinforcing strips of non-magnetic material in the course of manufacture. For instance, the core for a toroidal winding is moulded in two "split" halves, each circular in plan and semicircular in cross section. A ring-shaped strip of whalebone fibre, 20 to 40 mils thick, is cemented to the flat face of each half, and the two halves are then cemented together, strip to strip, to form the complete reinforced core. This is baked hard to dry out the cement, before being taped and varnished.


*Automatic Telephone and Electric Co., Ltd.; J. Bylewski; and A. Davidson. Application date, April 1st, 1943. No. 564621.*

## PIEZOELECTRIC CRYSTALS

**T**O minimise the effect of mechanical vibration on a crystal oscillator, when used, say, on an aircraft, the element is generally held under compression between nodal points, where the clamping produces the least possible damping. In practice, it is found that mechanical shocks tend to make the gripping points slip out of position on the smooth surface of the crystal, and so give rise to sudden jumps in the operating frequency. Any such movement is also liable to scratch the thin metal film forming the electrode.

By contrast, it is now proposed to hold the crystal under a constant tension or stretching force. A V-cut crystal, for instance, is gripped between the flat lower face and a peripheral lip or rim on the dish-shaped upper face, by a pair of suitably shaped jaws, each carried by a terminal spring. In the case of a flat crystal, the bent end of each holding-spring is hooked into a hole or recess formed on opposite

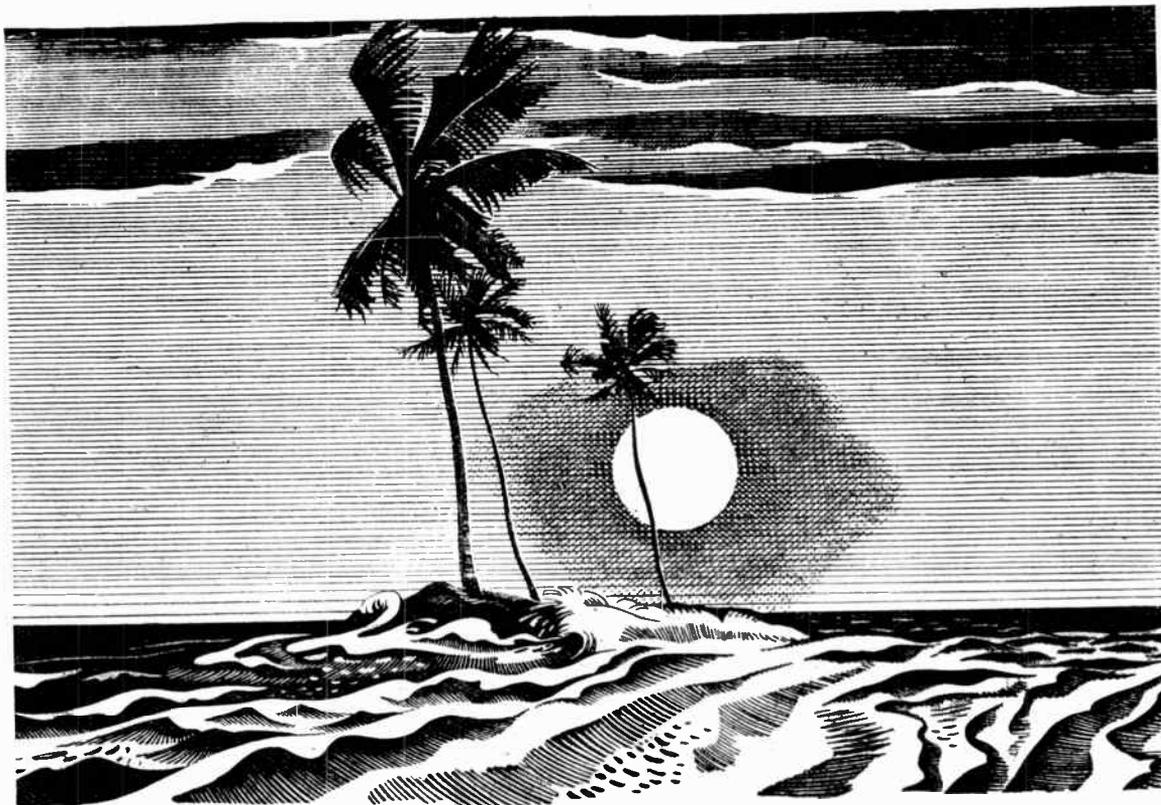The British abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1/- each.



## The Isle that Grew from the Sea

A little land above the surface of the sea ; white surf and leaning palms . . . but underneath, out of sight, the foundations go down deep and wide to the bed of the ocean.

So, too, with great industrial organisations like that of Philips. Their

achievements and the high reputation of Philips products are broad-based on persistent research, skilled technicians, highly-developed factories and long-accumulated knowledge and experience of the application of electricity to the needs of the modern world.

# PHILIPS



LAMPS ★ RADIO ★ X-RAY

COMMUNICATIONS EQUIPMENT AND ALLIED ELECTRICAL PRODUCTS

PHILIPS LAMPS LIMITED, CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2 (100)

Rate 6/- for 2 lines or less and 3/- for every additional line or part thereof, average lines 5-6 words. Box Numbers 2 words, plus 1/- Press Day April 1945 issue, first post Thursday March 8th. No responsibility accepted for errors.

Under Defence Regulations 1939, Statutory Rules and Orders 1940, Number 1689, a permit (T99G) must be obtained before sale or purchase of certain electrical and wireless apparatus particularly such valves and apparatus as are applicable to wireless transmission.

## NEW RECEIVERS AND AMPLIFIERS H.P. RADIO SERVICES, Ltd., offer:-

**CIVILIAN** ac wartime receiver, £12/3/4; battery model, complete with batteries, £12/6/8; 5w 3v ac/dc amplifier, with valves, neat chassis construction, amazingly efficient, £6/10; suitable Celestion loud speaker, matched, 33/-.

**PHILIPS** home battery charger for ac mains, output 12v, 1.3amp, £3/1/6.

**ROTHERMFL** crystal pickups, 812, £3/13/6, Senior 78/9; mains transformers (specify 4v or 6v heaters), 80ma, 27/6, 120ma 35/-; super quality 0.3amp line cord 2/6 yd.; 0.2amp voltage droppers, 4/9, 0.3amp 5/6; new grey steel drilled chassis, 10in x 8in x 2 1/4in, 2/6. **VOLUME** controls, all popular sizes, 3/6, with switch 4/6; Dubilier 2mf 650v block condensers, 4/- each; "Rola" 8in PM speaker, 2-3 ohms, 22/-; Celestion 8in PM speaker with transformer, 30/-; Celestion 8in mains energised with transformer, 2,000 ohms field, 36/-; Celestion CT102 6in with special multi-ratio transformer, 35/-.

**UNIVERSAL** output transformers, 6/6 each; Bell transformers, 5/11; stepdown transformers, 200w 230-110v, 35/-; 60w ditto, 29/-; Meico moving coil microphone, 5gns.; Meico folding floor stands, 42/6; Meico microphone transformers, 12/6 each; microphone trans., 70/1, 8/6; carbon microphones, 2/6, 7/6.

**VIBRATORS**—Mallory 6v 4 pin, 12/-; Bulgin vibrators, 6v 6 pin, self-rectifying, 20/-; bases 1/-; 12v vibrators, in small square case, non-rectifying, 10/-; plug or distributor suppressors, 2/3 each; dynamo condensers, 2/6 each; telegraphic car aerials, with bumper-bar clamp, 21/-.

**MULLARD** or Cossor electrostatic cathode-ray tubes, 3in, 3gns. each, bases 4/6 each; GTIC argon filled relay, 25/-; new Mullard universal measuring bridge, 5gns.; Mullard B100 cathode-ray tube unit with tube, 12gns.; highest grade 0-1 ma meters, 73/6; 3/4in diameter brand new Wheatstone Morse tape recorders (incorporate silent 12v motor), beautiful instruments, 5gns.

**BOOKS**—"Radio Valve Manual," 3/6; "Radio Circuits," 2/-; "Amplifier Manual," 2/-; "Short Wave Manual," 2/-; "Modern Radio Test Gear Construction," 1/6; "Rapid Radio Repairs," 4/6 "Radio Reference Handbook," 4/6; "Radio Manual," 1/-; "Manual Disc Recording," 2/-; "Radio Inside Out," 4/6. Postage extra under £4.

**H.P. RADIO SERVICES, Ltd.**, 55, County Rd., Walton, Liverpool 4, Tel. Aintree 1445.

**COMMUNICATION** receivers.—Remember "Dale" after the war.—Dale Electronics, Ltd., 152-6, Gt. Portland St., W.1, Mus. 1023.

**BRAND** new high fidelity 12-watt amplifier, 7 valves, treble and bass boost, etc.; energised Rola G.12, in 2ft sq. box baffle; £40.—Box 3360. [3514]

**QUALITY** amplifiers, 200-250v ac, 5w, 8 1/2gns; 12w, £14; output impedance to requirements, both types; s.a.e. for leaflet and copy "Design for Quality."—John Brierley, 1, St. Paul's Ave., Lytham St. Annes. [3195]

**AMPLIFIERS**—Complete equipment for P.A., industrial, dance and stage installations and portable apparatus from 15 to 150w; early deliveries; illustrations and spec. on request.—Broadcast and Acoustic Equipment Co., Ltd., Broadcast House, Tombland, Norwich 26970. [2963]

**HENRY'S** offer t.r.f. 4 valve ac/dc kit set, med watt, complete with all components and drilled chassis, 10x4x2 1/2, easy to build, circuit supplied, 5in speaker, no other extras; £8/10; cabinets for same, 22/6; 7 days' delivery.—Henry's, 5, Harrow Rd., Edgware Rd., W.2 (Pad. 2194). [3339]

**£24** World Quality amplifier with tone control stage, 8watts push-pull triode output, price includes super Quality triple cone, 12in permanent magnet speaker with large matched output transformer and all valves; as above but with 15watt tetrode output, £25/10; ideal for realistic reproduction for public address; limited number available.—Bakers Selhurst Radio, 75, Sussex Rd., S. Croydon. Tel. Croydon 4226 for demonstration. [2772]

**RECEIVERS, AMPLIFIERS—SECOND-HAND**  
**ARMSTRONG** 88-10, s-het straight r-gram chassis.—Offers 109, Brancaster La., Purley.

# Registration

with a difference!

YOU have registered for  
Food. YOU have  
registered for Service

—BY ORDER

NOW comes something more in  
keeping with British Tradition

# Voluntary Registration

## THE POST-WAR CATALOGUE

of

# PARTRIDGE TRANSFORMERS and CHOKES

will be sent to all "Registered Customers" as soon after the war as conditions permit.

During our five years' enforced silence we have evolved a number of new types which, of course, cannot be released or publicised during hostilities.

All these, plus our Standard models, will be fully described and illustrated in the Catalogue for which you are invited (not ordered, mark you!) to register to-day.

**FILL IN THE COUPON** BELOW giving your permanent address, and please print in BLOCK CAPITALS.

Telephone:  Abbey 2244

# PARTRIDGE TRANSFORMERS LTD

76-8, PETTY FRANCE, LONDON, S.W.1

### COUPON

To PARTRIDGE TRANSFORMERS LTD.,  
76-78, Petty France, London, S.W.1.

Please register my name and send me free of charge your POST-WAR CATALOGUE as soon as conditions permit, in accordance with your offer in "Wireless World," March, 1945.

Name .....

Address .....

**HARTLEY** Turner duode de luxe, 2,500 ohm field; offers.—Box 3350. [3473]  
**HAYNES** 2 h.f. tuner chassis, model R, oscilochron, 7 valves; offers.—Box 3369.  
**NATIONAL** H.R.O., 9 coils, power pack, speaker, as new.—Benson, Bushburn, Robertsbridge. [3530]

**NEW** Mono ac, 6-wt., oak cab., auto. rec., changer; elec. clock; Farrex 10-115 aw cony; £65.—Box 3351. [3475]

**AS** new, 16 watt amplifier, battery operated, microphone, £25; suitable mains unit, £5.—R. K. Wilson, Alnwick. [3518]

**TRIX** U70T ac/dc amplifier, speaker, telescopic mike, with cables, 2 inputs; £27.—Pearson, 132, Rugby Rd., Binley, Coventry

**12** W.A.T. Baker's amplifier and speaker, little used, £20; 1/4hp ac motor, 110v, £3/10.—Davidson, Cinema, Portway, Banffshire.

**HARTLEY-TURNER** complete, perfect, offers.—Nightingale, 31, Barnpton Lane, Dartington, [3494]

**PHILIPS** 6-volt de luxe car radio, Rola G.12, energised with transformer, both as new; offers; wanted, H.M.V. High Fidelity pick-up.—Box 3365. [3528]

**PHILCO** 16 11-valve 23mc to 520ks, in 5 ranges, 10 watt output, £25; Savage 30-watt high gain amplifier, £25.—Courtney Davis, Harpenden. [3533]

**HARTLEY-TURNER** 5-band feeder unit, variable selectivity, etc., £16; new Pamphonic 18in speaker, £15; Quality amplifier, p.p., DA30s, £16.—Hardwicke, 29, Warwick Av., Crosby, Lancs. [3498]

**CLEARANCE**—Slag-wool baffle for 10in speaker, 30/-; several 8in speakers, fields 1,000 up, from 15/-; M.W. TRF feeder units, 4/6, 3 volts, £3/17/6; one superhet 3-wave ditto, 6.3 volts, £6/10.—BM/ZDDF, Lond., W.C.1. (Wan. 3488 evgs.) [3527]

**A** REALLY good 18-valve Midwest radio for sale, price 50gns., excellent volume and tone, with 12in speaker, receives New York, Buenos Aires and Moscow, etc., louder and as clear as most sets do London.—G. Muir, 10, Penhurst Gdns., Edgware, Mdx., Edg. 0850.

**NEW LOUDSPEAKERS**  
10in mains energised speaker, 2,000 field, 2.5 voice, 45/-, boxed; Benjamin ac field kit, 55/-.—25, Ormonde Av., Hull. [3481]

**NEW** Broadcast P.M. loudspeakers, 3 models; 12in 12watt 15,500 lines, 1 1/4 dia, voice coil; 12in 25watt 18,000 lines, 1 1/2in dia, voice coil; 15in 40watt 18,000 lines, 2 1/4in dia, voice coil; machines and precision built instruments, Ticonal magnets, detachable diaphragms, die-cast chassis, uniform response, accuracy, tonal quality, appearance and finish; superior standards in fidelity, sensitivity, prompt deliveries; specifications and illus. upon request.—Broadcast & Acoustic Eq. Co., Ltd., Broadcast House, Tombland, Norwich. [8537]

**£5/15** only.—Brand new Baker superhet Quality 12in Auditorium permanent magnet speaker with triple cone, manufactured by Bakers Selhurst Radio, the pioneer manufacturers of moving coil speakers since 1925, wide frequency range, even response, ideal for quality reproduction, fitted with magnet having exceptionally high flux density in the air gap, suitable for public address equipment when quality reproduction is first consideration; send 2d. stamp for leaflet.

of above and constructional details of a new acoustic chamber designed to extend loud speaker frequency range; also constructional details of an infinite baffle cabinet; every music lover interested in realistic reproduction should write for leaflet.

**£8/15** only.—Brand new Baker super power cinema permanent magnet speaker with 18in triple cone of new design, giving wide frequency response free from objectionable resonances; speech is clear and natural and music is reproduced with exceptional realism; fine engineering job, extremely sensitive, ideal for public address equipment when power handling capacity plus realistic reproduction is required.—Bakers Selhurst Radio, 75, Sussex Rd., S. Croydon. Tel. 4226 for demonstration.

**LOUDSPEAKERS SECONDHAND**  
VOIGT twin diaphragm unit, P.A. type; £16.—Box 3363. [3523]

**VOIGT** twin dc, Magnavox 66, 2,000 ohms, P.P.O.P. trans; offers.—113, Hazel Rd., Longview, Liverpool. [3463]

**HARTLEY-TURNER** standard p.m.; £5/10.  
**H**—Hare, Westholt, Hen-w, Beds. [3511]

**B.T.H.** R.K. Senior ac model, separate 15:1 output transformer; £5.—Lewis, 57, Basing Hill, London, N.W.11. [3542]

**VOIGT** h.c. horn, offers; R.G.D. cabinet, s.s.; £5; Pye 10 valve 4-band console, £35.—Clews, 73, Linden Crescent, St. Albans. [3512]

**MAGNAVOX** moving coil speaker, in case, £48; Marconi eliminator, 230 volts, £3.—Scammells, Fashion St., E.1. Bis. 3521. [3479]

**MAGNAVOX** P.M. Auditorium, 12in, £24/10; F.I. p.m. horn units, £4/10; Trivox £15; p.m. horn unit, £4.—Courtney Davis, Harpenden. [3534]

B.T.H. RK. 12in cinema speaker, 15-ohm v6 6V field; what offers? Box 3354. [3493]

**DYNAMOS, MOTORS, ETC.**

JANETTE rot. con., 230 dc-230 ac 500w; £17/10. Best offer.—Box 3362. [3522]

HARRIS, Strouds, Bradford, Berks, offers clearance items at bargain prices; all goods in stock subject to being unsold. ROTARY converters.—60w M.L., 100v dc input, 600v dc output, £3; 70w Crypto, 220v dc, 15v dc, £3; 150w Neco, 440v dc, 12v dc, £2/10; 300w Electron, 110v dc, 110v ac, £7; 500w Phyme, 110v dc, 70v ac, £5; 750w Crypto, 230v dc, 150v ac, £7; 800w Siemens, 220v dc, 150v ac, £6/10; 900w Lang, 250v dc, 150v ac, £8.

A.C. MOTORS (all 50 cycles 1 phase).—1/6 hp Metro-Vick, 100v 1,720 rpm, £1/10; 1/10 hp B.K.B., 110v 2,000 rpm, £1/10; 1/8 hp Holzer Cabot, 100v, £3/10; 1/4hp Fuller, 200v 1,400 rpm, £2/10; 1/2hp G.E.C., 110v 1,425 rpm, £2; 1/6hp Brown Boveri, 100v 1,400 rpm, £1/10; 1/4hp Siemens, 210v 1,440 rpm, £5; 1/2hp Neco, 220v 1,400 rpm, £4; 1hp Brook, 200v 1,400 rpm, £7/10.

D.C. MOTORS.—1/4hp Elec. Co., 200v, £2; 1/10hp Burroughs, 220v 1,750 rpm, £2; 1/6hp Century, 200v 1,750 rpm, £3; 1/8hp Century, 210v 1,720 rpm, £3/10; 1/4hp Verity, 100v 2,400 rpm, £2/10; 1/4hp Siemens, 40v 2,000 rpm, £2; 1/6hp Delco, 240v 1,760 rpm, £2/10; 1/4hp Singer, 230v with clutch, £3/10; 2hp Newton, 240v 1,640 rpm, £6/10.

BATTERY chargers.—Crypto, 230v ac input, 15v 5a dc output, rotary, £7; Valley, 200v ac, 25v 6a dc, rotary, £7; Neco, 205v ac, 16v 24a dc, rotary, £12/10; B.K.B., 230v ac, 15v 45a dc, rotary, £5/10; Phillips 100v ac, 12v 1 1/2a dc, valve, £2; Tobe, 110v ac, 6v 5a dc, metal, £3; Bone-dri, 110v ac, 7 1/2v 5a dc, metal, £3; Tungal, 110v ac, 15v 3a dc, valve, £4; Tungal, 110v ac, 75v 6a dc, valve, £9/10.

THE above is only a selection of machines in stock; enquiries solicited.—Harris, Strouds, Bradford, Berks. [3536]

NEW ac motors, 1/4hp, high starting torque, 200-250v, £4/15; 1/2hp, £2/5; 1/2hp £7/5; 1hp, £9/7/6; all other sizes available; also machinery.—John W. V. Steel, Bingley, Yorks.

ALL types of rotary converters, electric generator sets, etc., in stock, new and second hand; supplied against priority orders only. WARD, 37, White Post Lane, Hackney Wick, E.9. Tel, Amherst 1933.

**CABINETS**

SPECIAL offer to clear.—Loudspeaker cabinets, polished oak, 12/6 and 15/6, polished walnut, 17/6 each, delivered in any quantity; any type of radio cabinet made to order; send us your enquiries.—Waldenberg Bros., Ltd., New York Rd., Leeds. [3030]

**NEW MAINS EQUIPMENT**

LAMINATIONS for mains transformers available from stock; send 3d. for sample & price.—V. E. S., Radio House, Ruislip, Mdx.

VORTEXION mains transformers, phokes, etc., are supplied to G.P.O., B.B.C., L.P.T.B.; why not you? Imitated but unequalled; orders can only be accepted against Government contracts.

VORTEXION, Ltd., 257, The Broadway, Wimbledon, London, S.W.19. Tlb. 281.

**TEST EQUIPMENT**

AVOMETER, 36-range Universal, with case; £12.—155, Trehaner St., S.W.18. [3506]

LATEST Raymeter, 83A, new, 74 ranges, 4,000 opt., £16.—McEwen, 211, Hampermill Lane, Oxhey, Herts. [3545]

EVERSHED & VIGNOLES 500v Megger, large mod., 0-100 meg in lea. case, new cond.; £17/10.—Hall, 172, Park Rd., Bkspool.

TESTOSCOPES, indispensable to radio service engineers; makes 20 lists; interesting booklet on request; from all wholesalers or direct; send for leaflet "R.I."—Runbaken, Manchester, 1. [3702]

OSCILLOSCOPES, signal generators, multi range test meter, etc., test gear of every description, British or American, repaired, serviced, recalibrated.—A. Huckelbee, "Hazlejohn," Crofton Lane, Orpington, Kent. [3031]

SIGNAL tracers, ideal for tracking down distortion, etc., £25; 0.1ma meters, round type, first grade, £2/18/10; test prods., 1/9 per pair, available from stock; orders also accepted for Multi-range meters, Avon, Taylors, etc., and for trimming tools; further details by request.—V. E. S., Radio House, Ruislip, Mdx.

**MORSE EQUIPMENT**

ORIGINAL de luxe model, Vinbroplex key, perfect; £4 10.—BM/RLDO, W.C.1. [3509]

MORSE practice equipment for class room or individual tuition; keys, audio oscillators for both batt. or main operation.—Webb's Radio, 14, Soho St., W.1. Ger. 2089. [2291]

GRAMOPHONE AND SOUND EQUIPMENT PICK-UP, latest Marconi hypersensitive, a new; offers.—Box 3361. [3515]

MARCONI pick-up; offers wanted, H.M.V. hypersensitive pick-up and transformer or Voigt moving coil pick-up.—Box 3349. [3470]

# PREMIER RADIO

ALL POST ORDERS TO:  
JUBILEE WORKS, 167, LOWER CLAPTON ROAD, LONDON, E.8. (Amherst 4723.)

CALLERS TO:  
JUBILEE WORKS or  
162, FLEET STREET, E.C.4. (Central 2888.)

Send for details of other accessories available. All enquiries must be accompanied by a 2d. stamp.

1-VALVE BATTERY S.W. RECEIVER, with 2-volt valve, 4 coils, 12-170 m. bandspread tuning, 55/-, including tax.  
STEEL CHASSIS, 10x8x2 1/4, 7/-, 16x8x8, 8/6; 20x8, 10/6.

SHORT-WAVE COILS, fit octal sockets, 4-pin aerial coils, 9-15, 12-26, 22-47, 41-94, or 76-170 m., 2/6 each; 150-350 or 250-550 m. 3/-; 490-1000 or 1000-2000 m. 4/-, 6-pin H.F. Trans., 9-15, 12-26, 22-47, 41-94 or 76-170 m., 2/6. S.W. chokes, 10-100 m., 1/3; 5-200 m., 2/6.

SHORT-WAVE CONDENSERS, all brass, easily ranged, 15 mmfd., 2/11, 25 mmfd. 3/3, 40 mmfd., 3/3, 100 mmfd. 3/11, 100 mmfd. 4/8, 250 mmfd., 5/8, 2-gang, 100 mmfd., 15/-; shaft couplers, 7d. Desirable dials, 1/6.

MIDGET "P" TYPE COILS, 12-35, 16-47, 34-100, 91-261, 250-750, 700-2000, 2000-557, available as H.F. Trans., aerial, or osc. coils, 2/3 each. Suitable Yaxley type wave-change switches, every type available; locators, 2/- each; wafers, 1/6 each. Suitable small 2-gang, 200 p.f. condensers, 1/5 each; suitable metal-cored iron-cored 465 K.C. I.F. Trans., 45/- pair; midget type, B.K.B. type. Suitable 60 mmfd. trimmers, 1/-; osc. psdler, 750 mmfd., 1/9.

SUNDRIES, 2 mm. Syntoflex, 2 1/2d. yd.; resin-cored solder, 6d. per coil of 4.6 per lb.; selected 2-pin plugs and socket, 9d.; ditto, 8-pin, 2/-; Octal sockets, 10/4; 4-pin valve screens, 1/2. Knobs, 6d. Pointer knobs, 1/1. Crocodile clips, 4d. "Gain" and "tone" indicator plates, 7 1/2d. Fuses, any size, 5d. Fuse holders, 6d. 6-volt vibrators, 4-pin, 12/6. Crystal pickups, £3 18s. 9d., including tax.

BATTERY CHARGERS for 2v. batt. at 4s. 25/-; for 2, 4 or 5v. batt. at 1s. 45/-; for 6v. batt. at 1s. 30/-; for 12v. batt. at 1s. 49/6; for 6v. batt. at 1s. 4s. £3 10s.

MAINS TRANSFORMERS, 300+300 v., 60 m/a, three 4 v. 2-3 a. windings, 25/-; 350+350 100 m/a, 5 v. 2-3 a., 6.3 v. 2-3 a., 29/-; 350+350 100 m/a, three 4 v. 2-3 a. windings, 29/-; 350+350 150 m/a, two 4 v. 2-3 a. windings, 29/-; 350+350 150 m/a, 5 v. 2-3 a., 6.3 v. 2-3 a., 39/-; 500+500 250 m/a, 5 v. 3 a., 6.3 v. 2-3 a., 6.3 v. 4 a., 65/-. Many other types available; auto-trans. 220/110 or vice-versa, 60 watt 21/-, 125 watt 27/6, 250 watt 37/6.

AMERICAN VALVES, many types, in stock, controlled prices, incl. tax: 6X4, 6X5, 6P6, 5Y3, 5Z4, 251A, 7B, 48V, 6AR, 457Z, 10C5, 12K7K.

SUPER QUALITY AMPLIFIERS, 9 watts output, high and low gain inputs with mixer, treble and bass controls, twin DB 30-11,000 cycles, negative feedback, 2, 4, 8 and 15 ohms output, £4 14s.

MOVING COIL SPEAKERS, 8 inch P.M. with P.M., no trans., 25/-; 8 inch P.M. with 3 or 15 ohm voice coil, no trans., 30/-; Plessey 8 inch energised 7,500 ohms, no trans., 25/-; B.T.H. 10 inch energised, 1,600 ohms, no trans., 40/-; Midget, standard or P.P. trans. for any above, 10/6. Super quality gain Matchmaker output transformers, match any type single or P.P. to any voice coil, 7-watt, 22/6; 15-watt, 30/-; 30-watt, 49/6; 50-watt, 59/6.

MICROPHONES, Transverse current, 45-7,500 cycles, 23/-; moving coil, 56 DB, 25 ohms, 25 5s.; microphone capsules, 2/6; microphone trans., 10/6; collapsible mike stand, 52/3; crystal mike, 50-8,000 cycles, mhd. 60 DB, 39/6.

RESISTANCES, 500x100x100x100x100, 2 amp., 5/6; 40,000 ohms tapped every 5,000 ohms, 10 watts, 5/-; heavy duty potentiometers, 50,000 ohms, 60 watts, 15/-; 4 watt res., 6d. each; 1 watt, 9d. each.

CHOKES 8L, 300 ohms, 100, 100 m/a, 400 ohms, 100 m/a, 300 m/a, 300, 100 m/a, 400 ohms, 19/6; 3011, 185 ohms, 150 m/a, 25/-; 25H, 250 m/a, 120 ohms, 39/6; 15H, 500 m/a, 62 ohms, 65/-.

SMOOTHING CONDENSERS, 8 mf., oil-filled, 500 v.w., size 4 1/2 x 3 1/2, 10/6; 8 mf., 30 v., size 3/2 x 1, 1,000 v.w., 2/-; 1,000 v.w. 4 1/2; all values tubular condensers, 9d.; 2 mf., 350 v.w., 3/9; 2 mf., 450 v.w., 4/6; 4 mf., 450 v.w., 7/6; .5 mf., 350 v.w., 2/-; 1-1/4 mf., 300 v.w., 3/-.

METERS, First grade 0-2 m/a, with 300 v. and 600 v. multipliers, 31-inch, 5s. 5s.; 3-volt and 30 volt multipliers, 30 and 300 m/a shunts for same, 2/6 each; first grade 4 1/2-inch 0-25 m/a meters, removal of internal shunt reduces to 5 m/a, 55/-; one milliamper meter, 2 square, £3; ditto, 500 micromap., 24; any value multiplier or shunt for same, 2/6 each; metal rectifiers to convert above to A.C. instruments, 10/-; Tenway switches, 2/6; 1st grade M.C. 2 1/2 sq. meters 10, 15, 20, 25 or 30 m/a., 35/- each.

BURNEDEPT needle armature pick-up and scratch filter, 50/-; Ferranti AF3 10/-, AF4 7/6, AF10 5/-, AF5C 20/-, all perfect.—Box 3355. [3495]

E.M.I. electric gram motor and Baker 10in energised triple cone speaker with rect. and smoothing, £19/10, ex. Avon Bridge.—Worton, Willington, Derby. [3477]

COILS for Hartley and Brierley circuits, transformers and chokes for all W.W. circuits.—R. Clark, 30, Langland Cres., South Stanmore, Tel. Wordsworth 5321. [3551]

RECORDING engineer offers consulting service for disc, film, tape, etc.; advice, diagrams, general information all aspects sound recording; stamp with enquiries.—BM/DISC, London, W.C.1. [3498]

VOIGT m.c. pick-up and corrector; W.W. m.c. pick-up and transformer; Voigt 21 horn; Sound Sales 4-valve contrast expander, offers.—Jolly Gardener, Maiden's Green, Bracknell, Berks. Winkfield, Row 234. [3540]

PLAYING desk, mahogany, accommodating 500 records, incorporating 2 h.f. tuner (Haynes), diaphase amplifier (PX4s), metered, twin Garrard motors, Wilson Rothmel pick-ups, Voigt with power pack, mahogany h.c. horn; £85; demonstration.—Parker, 17, Allerton Park, Leeds, 7. Tel. 43502. [3541]

VALVES ALL B.V.A. valves available, also number of discontinued types; list prices; pro forma or c.o.d.—David Robinson, Ltd., 100, High St., Bedford. [3421]

COULPHONE RADIO, New Longton, near Preston, for a better valve service; all Tungsram and B.V.A. valves at present manufacturing in stock; list prices. [2821]

MARCONI valves surplus to our immediate requirements, including tax:—MH41, 11/7; X41 14/-; P63 6/9; D42 11/7; KT33C 14/8; KTW63 12/10; KT56 12/10.

MARCONI valves surplus to our immediate requirements, including tax:—TH41 14/-; L2DD 9/2; PHND04020 15/3; PEN45DD 15/3; TP26 12/10 VP41 12/10, VP1322 12/10, VP210 11/-; AC/VP1 12/10, AC/VP2 12/10, AC/ME 10/5, AC/TH1 14/-, AC/HLDD 11/7, SP215 9/1-, SP1320 11/7, SP41 12/10; HL1320 1/2, HLDD1320 11/7, HL42DD 11/7, HL23 12/10, HL22 5/10, UU5 11/-; U07 11/-; TP23 12/10.—Larg's Radio Service, Whitehall St., Dundee. [3558]

OUR adaptors will help in replacing unobtainable valves; send 7d. for interesting booklet on valve replacements; trade enquiries invited.—V.E.S., Radio House, Ruislip. [3558]

VALVES.—See November issue, Pen41DD out.—Pen45DD in., 15/3 each; postage and packing 9d.; c.o.d., but cash with order preferred.—London Sound Labs., Ltd., 40, South Molton Lane, Bond St., London, W.1.

TUNGSRAM valves, surplus to our requirements, all free of tax: APP4, 10/6; APP4B, 10/6; CB215, 9/6; DD4, 5/6; DD13, 5/6; DD4, 9/6; DDT15, 9/6; DDDPA, 12/6; HL44, 7/6; HL13, 7/6; HP118, 10/6; HR210, 4/9; LD210, 4/9; LP220, 6/-; MH118, 11/6; PP2, 9/-; PP4, 10/6; PP418, 10/6; P215, 6/-; SP2B, 9/-; SP4S, 10/6; SP4S, 10/6; TH41, 11/6; TH4B, 11/6; TX4, 11/6; VME4, 10/6; V02, 10/6; VP4B, 10/6; VP4S, 10/6; 5Y3G, 9/-; 6B8G, 11/6; 6K7G, 10/6; 6V6G, 10/6; 6X5G, 9/-; 35, 10/6.—Low's (Dundee), Ltd., 21, Crichton St., Dundee.

**COMPONENTS—SECOND-HAND, SURPLUS**

MALLOY 6-volt 4-pin vibrators for car radio, etc., 15/- each.—F. Turner, 446, Stockport Rd., Denton, Manchester. [3387]

P.M.s.—8 and 6 1/2in. 19/6 ea.; trf., 6/3; volt dropers, 4/-; line cord, 1/2 ft.; Midget trf coils, 3/3; Piezo P.U.s, 70/-, v.c.s, 3/-; w.s.w., 4/10; 4-page list, 2d.; cod or cwo.—16, St. Helen's Ave., Lincoln. [3546]

BUY your components direct and save pounds. Build our super Victory Four ac/dc receiver, it's 100% efficient; circuit and everything supplied, knobs and dial ready for cabinet, £27/19/6; cabinets, 30/- and 42/-; detailed circuit separately, 1/6; bright steel chassis, drilled ready, 4/6; chassis with valve holders, speaker, 2-gang condenser and dial bracketed and fitted on, 59/6; chassis made up to your own specification; estimates.—Bucleuch, Radio Manufacturers, 1 and 2, Melville Terr., Edinburgh. [3513]

COSSOR 4 1/2in C.R. tube (26D) holder, tube densers, 2 thyratrons, 2 h.v. rectifiers, few odd valves; s.a.e. enquiries.—Box 3359, 3510

ASSORTMENT of new and used radio components, etc., for experimenters and constructors, £1 per parcel; satisfaction guaranteed.—E. H. Robins Trading Co., Ltd., 27, Wellfield Rd., Cardiff. [3539]

SERVICE kits. See November issue. C.o.d., but cash with order preferred.—London Sound Labs., Ltd., 40, South Molton Lane, Bond St., London, W.1. Look out for combined valve tester and circuit analyser. [3523]



# RI

## Transformers

**FAMOUS THROUGHOUT  
THE WORLD**

*There is a type for every radio purpose, and it is the right type. Satisfaction assured if it bears our name.*

**RADIO INSTRUMENTS LTD.**  
Purley Way, Croydon.  
Telephone: Thornton Heath 3211

## LASKY'S RADIO

370, Harrow Rd., Paddington, W.9  
(Op. Padd. Hospital.) Phone: Cunningham 1979

### SERVICE KITS.

Kit No. 1. 24 assorted condensers consisting of 8 mfd. 500 v., 4 mfd. 600 v., 16 mfd. 450 v., 2 mfd., etc., etc., £2.

Kit No. 2. Similar to above but Total 48 cond. in larger quantities of popular types. Price £3 15s.

### SPEAKERS

Roia Sin. P.M., less Transformer, 21/6.  
" 6in. " " " 22/6.  
" 8in. " " " 23/6.  
" 6 1/2 mains energised with Trans., 32/6.

Goodmans 3 1/2in. P.M. Speaker, less transformer, 30/-.  
Celestion 6 1/2in. mains energised and transformer, 30/-.  
Celestion 10in. P.M. and transformer, 45/-.

Larger types in stock. Prices on application.

Volume Control, with switch, long spindle, all values, 5/6 each; less switch, 3/9.

Midget Volume Controls with switch, long spindle, 1/2 meg., 6/6 each.

### MAINS TRANSFORMERS.

350-0-350 4 v. C.T., 120 ma., 32/6.  
350-0-350 6.3 and 5 v., 120 ma. C.T., 35/-.

### CONDENSERS.

2 mfd. paper block 600 v. at 2/6 each.  
4 mfd. " " " 500 v. at 5/6 "

Other types in stock.

RESISTORS. Kit of 48 assorted, 20/-.

VALVES. We have a large stock of mains and battery valves, English and U.S.A. types, at B.O.T. prices.

### TUNING CONDENSERS.

.0005 Midget two-gang, at 13/3.  
.0005 Midget two-gang with trimmers, 15/6.  
.0005 Midget two-gang with ceramic trimmers, 17/6.

.0005 three-gang, less trimmers, 11/6.

See our Ads. last month's issue for rest of goods in stock. Send Id. for our current lists. Send us your requirements C.O.D., but cash with order preferred.

G. A. RYALL, 36, Huron Rd., S.W.17.—Mail order only; no c.o.d. under £1.

TWO-WAY screened flexible, good quality, 1/3 yard, 3/6; 2/9; twin screened, high insulation and cotton outer cover, 1/9 yd, 4-way 2/3 yd. TEN-WAY cable, good conductors, 1/3 yd, 3 yds 2/9.

OCTAL 8-pin plugs with base, complete with insul. metal cap, 1/3 each, 3 for 2/9. Ditto with solder tags to take heavy gauge wire, 1/4 ea, 3 for 3/3.

MORGANITE long spindle 10,000 vol. con., less switch, 3/9. DIAL plates, oblong, 5 1/2 x 2 1/2 approx., Varley, 4 for 1/6.

BURNDEPT 4-band dial, 8 x 5 1/2, s.w. on lower half of scale, 1/6 each.

MICROPHONE capsules by Standard Tele-phones, 3/9 ea; Centralab vc, less switch, long spindles, 5,000ohms, 1/2 meg, 3/9 ea. INPUT strips, 2in x 3/4in, 2-way, 2/6 dozen; with terminal screws, 3/3 dozen; anchor or mounting strips, 2/3 dozen, 5-way.

SPECIAL offer, T.C.C. double mica cond. 0.0001 x 0.0001 five (ten condensers) for 1/3; Hunts 0.01 mica cond., 1/- ea; hf chokes on ebonite bobbins, 5,000ohms, 1/3 ea.

ERIE colour coded resistances, 2-watt type, 680, 8800, 140,000, 150,000, 220,000, 470,000, 820,000, 2 1/3; Erie 3w, 680, 1/3 ea. YAXLEY type low loss switches, single pole dt, 2 bank, 2/9, single bank, 2/3.

TWIN rubber flexible cable, new, for mains leads, etc. (one cover), 1/3 yd, 3 yds 2/9; push-back connecting wire, stranded, 2 colours, cotton-covered, 12yds 2/3.

YAXLEY type switches, 3 bank, 2 pole, 4 way, with middle screen, long spindle, 4 shorting bars, 6/9 each. [3397]

CHARLES BRITAIN RADIO (K. H. Ede) offers good quality radio apares.

SERVICE kits.—No. 1: One 8mfd 450v tubular and 1 doz asstd. conds., 11/6. No. 2: Two 16mfd can conds., one 60mA choke, one mains dropper and 12 asstd. ceramics, 30/6.

No. 3: Two 8mfd, 450v tubulars, two 4mfd 250v tub., two 2mfd Mansbridge and 24 asstd. ceramics and tubular conds., £1 12/6.

MAINS transformers (ex R.D.G.), 4v. 4amp, 4v lamp, 350-0-350, beautiful job, 30/6 ea; chokes (ex H.M.V.), 120MA 500 ohms, 12/- ea; multi-ratio sprk. trans., C.T., 6/6 ea; toggle switches, with "on-off" plate, 3/-; radio side cutters, 4/6 pr; heavy duty cable couplers, 3/6 pr.

KNOBS, best quality with brass inserts, 1/4 spindle, 1 1/2 dia, 8/6 doz; 1 1/4 dia, 7/6 doz; pointer knobs, 8/6 doz.

TWO-GANG, condensors, 0.0005 midget type, with trims, 13/6 ea; four-gang condensers, 3/6 ea (to clear); trimmers, 40-50mmf, 4/6 doz; glass dials, Marconi or H.M.V. all-wave, 7 1/2 x 4 1/4, 1/6 ea; vertical type 2 1/2, 8/-; paper dials for midgets, 8/- doz; ivorine dials, M.W. (Home, Forces, etc.), 2/- ea; potentiometers, long spindle, less switch, Dubilier, 5,000, 10,000, 25,000, 100,000, 1/4, 1/2, 1 & 2 meg, 3/6 ea; 1/4, 1/2, 1 & 2 meg, with switch, 5/6 ea.

TUBULAR condensers, N.1 (prices per doz), 0.1, 600v wkg, 10/-; 500v, 8/6; 400v, 7/-; 0.01 to 0.05, 6/6; 1,000v test, 0.001 to 0.005, 5/-; mica, 0.0001 to 0.0005, 5/-; resistances, 50 ohms to 1 meg, 1/4w, 5/6 doz; 1watt, 7/- doz; Morganite volume controls, 50,000 ohms, short spindle, 2/3 ea.

COSSOR knobs, less grub screws, 3/6 doz; sleeving, 2/6 doz yds; valve holders, British 5, 7, 9 and octal, American 4, 5, 6, 7 and octal, 7/6 doz; tinned copper wire, all gauges, 2/6 per 1/2lb reel; push-back wire, stranded, white and green, 2/6 doz yds.

THIS month's special offer! Mansbridge condensers, 2mfd 500v wkg, 2/- ea; terms, cash or c.o.d. over £1.—Charles Britain Radio (temp. address), Eureka, Surrey Gdns., Effingham, Surrey. [3553]

BRAND new components only, at list prices for discriminating amateurs and professional constructors.

SUPPLIERS to British and Allied Services and Government Departments.

A.V.O. and Weston test equipment and meters, Cosor and G.E.C. cathode ray tubes, T.C.C. and B. and I. condensers, Erie resistors, wire-wound precision resistors, Colvern w.w. potentiometers, Keston mains transformers, chokes and output transformers, London relays, Rothermel pick-ups and potentiometers, instrument and wavechange switches, ceramics, J.B. single, 2 and 3-gang vari condensers, Celestion and Vitavox speakers.

SERVICE includes circuits, practical help in construction, crystal calibration of receivers and oscillators; unlimited resources for technical information; specialists in short-wave work for amateur.

TELE-RADIO (1943), LTD., 177a, Edgware Rd. (Corner of Edgware Rd. and Marylebone Rd.), London, W.2. (Business hours 9 to 5.30 every day except Thurs, 9-1). Tel. Pad. 6116.

SUPERIOR ac eliminator, 3 var. h.t. outputs, 2, 4, 6-volt 1/2amp charger, incorp; 55/-; Harland, 4, South Av, Brighton. [3499]

# ARMSTRONG

ARMSTRONG has always had the name for Quality.

When this war has been brought to a successful conclusion our new range of ARMSTRONG CHASSIS will prove that our reputation was built on a firm foundation.

**ARMSTRONG WIRELESS & TELEVISION CO. LTD.**  
WALTERS ROAD, HOLLOWAY, LONDON, N.7

'Phone: NORth 3213

## REWINDS

Armatures, Fields, Transformers, Pick-ups, Fractional H.P. Motors, Speakers Refitted New Cones & Speech Coils.

All Guaranteed and promptly executed.

Valves, E.V.A. and American, good stocks. Send stamped addressed envelope for list of Radio Spares, and C.O.D. Service.

**A.D.S. Co.** 261-3-5, Lichfield Road, ASTON, BIRMINGHAM, 6



We have been moving—our new address is

No. 15, Silverdale, Sydenham, S.E.26

Voigt Patents Ltd.

# WELWYN

HIGH STABILITY  
CARBON  
RESISTORS




TROPICAL GRADE  
TYPE APPROVED  
CLOSE TOLERANCES  
LOW TEMPERATURE  
COEFFICIENT

ENQUIRIES ARE INVITED FROM THE TRADE—CATALOGUE SHORTLY AVAILABLE

**WELWYN ELECTRICAL LABORATORIES LIMITED**  
WELWYN GARDEN CITY · HERTS

The **“PYROBIT”** Tester

Pat. applied for

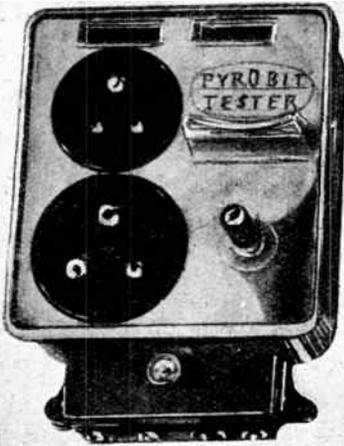

is indispensable for:  
Wireless Engineers, Repair Shops,  
Factories, etc., for Testing;  
Continuity, Earth connection, Leak-  
ages, on all kinds of tools and  
apparatus.

**ASK FOR LEAFLET**  
Completely foolproof

**ACRU ELECTRIC TOOL MFG. CO. LTD.**  
123, Hyde Road, Ardwick, M/c, 12

**MORE** extracts from  
letters sent in by **CANDLER** students

1. "I have studied Lesson 1 according to your instructions, and in spite of my lack of spare time and very short practice periods, I feel myself that I am progressing well."—Ref. 984. A. F.
2. "I am very satisfied with the first two lessons and have improved considerably, despite the fact that these were only elementary lessons."—Ref. A. F.M.
3. "I have just completed lessons 1 to 3. . . I can tell there is a marked difference by just learning the first three." . . . "My morse has improved considerably."—Ref. 1935. P. B.
4. "I have just finished lesson 4. . . I am getting on fine with my sending and receiving speeds. The other week I had my A.T.C. Morse Exam., and I passed 100 per cent."—Ref. 1661. J. R. B.

These students are taking the **JUNIOR Code Course**.  
NEXT MONTH we will give you extracts from letters sent in by **CANDLER** students who are taking the **ADVANCED Code Course**.

**WRITE NOW FOR THE FREE "BOOK OF FACTS."**  
**JUNIOR Scientific Code Course** for beginners. Teaches all the necessary code fundamentals scientifically.

**ADVANCED High-speed Telegraphing** for operators who want to increase their w.p.m. speed and improve their technique.

**TELEGRAPH Touch Type-writing** for speedy recording of messages and for commercial uses.  
Code Courses on Cash or Monthly Payment Terms.

**THE CANDLER SYSTEM CO.**  
(Room 55W), 121 Kingsway, London, W.C.2  
Candler System Co., Denver, Colorado, U.S.A. (345)

**SUPREME RADIO**, 746, Romford Rd., Manor Park, London, E.12. Tel. III. 1260.  
**EVERYTHING** for the radio engineer.  
**MIDGET** coils, aerial and h.t., t.r.f., with fittings and circuit, 8/6 pr.; also m.l. wave, 10/6 pr.; midget 2-gang s.m. 0.0005mid, split vanes, 12/6 ea; midget diams, all wave, 4in x 5in, coloured r.g.b., 1/9 ea; midget wave change sws., m.l., 10d. ea; knob, black or brown, 1/4in spindle, 9/- doz; good quality 100ma 300 h.m.s. chokes (smoothing), 10/6 ea; slow motion drives (only), 1/- ea; speaker trans., power and pen, 40 mlls., 7/6 ea; Celestion 8in speaker with trans., 29/- ea; line cords, 0.2 2-way, ranging from 250 ohms to 550 ohms, 4/6 ea; line cord, 3-way, 60 ohms per ft., per yard, 5/6; line cord, 2-way ditto, per yard 4/6; mains droppers, 0.2 amp, 1,000 h.m.s., 2 sliders, with feet, 4/6 ea; mains droppers, 0.3 amp., 800 h.m.s., 2 sliders, with feet 5/3 ea; Triple trimmers, 40 plds., 1/6 set; volume controls with sw., all sizes, 5/3 ea; volume controls, less sw., all sizes, 4/- ea; bias condensers, 50mid, 12v, 2/3 ea; metal speaker cabinets, 8in fitting, rubber feet, colours old gold, blue, green, cream and grey, with silk, 17/6 ea; mains transformers, 2 amp, 4v 5amp, 350+350, 19/6 ea; ditto, 5v 2amp, 6v 4amp, 19/6 ea; 2,000 ohms and 10,000 wire wound, less sw., v.c.s. 5/6 ea; many other lines in stock; stamped addressed envelope for all enquiries to Dept. M; cash with order, no c.o.d. 6d. extra for postage. [3485]

**VALVE holders**.—Celestion Amphenol octals, 8/- doz; 4, 7, 9-pin B.V.A. and 4, 5, 6, 7-pin U.S.A. Mazda octals, 6/- doz; 5-pin B.V.A., 8/- doz; side contacts, 15/- doz.  
**LOUDSPEAKERS**, less transformers: Rola's p.m., 5in 21/6, 6 1/2in 21/6, 8in 24/-; R. & A. p.m., 8in 25/6, 10in 31/6; R. & A. m.e., 2,000 ohms, 8in, 24/9.  
**LOUDSPEAKER** pol. oak cabinets; 15/- each. **VOLUME** controls, wire-wound, 10 ohms, 36/- doz, 3/4 each; carbon, with switch, 3/- each; carbon, without switch, 2/6 each.  
**ROTHERMEL** Bullet crystal mike; £3/15.  
**HENLEY** soldering irons, tapered bit, 13/4; pencil, 15/-; 5,000 valves stocked, English and U.S.A. types, all at B.O.T. controlled prices; send 1d for lists.  
**TERMS**, c.w.o. or c.o.d.; carriage paid on orders £1 or over.—H. Ransom, 34, Bond St. Brighton 5603. [3504]

**B.A.** thread screws, useful sizes, 2/6 gross; ditto, nuts, 2/6 gross; assorted screws and nuts, 2/6 gross; ditto, brass washers, 1/6 gross; wire washers, 1/6 gross; assorted solder tags, 2/- gross; assorted small eyelets and rivets, 1/3 gross; rubber-covered stranded copper wire, 1d. yard; heavier quality, 1 1/2d. yd; very heavy quality, 2 1/2d. yd, ideal for aerials, earths, etc.; tinned copper connecting wire, 20ft coil, 6d.; ditto, rubber-covered, 10ft, 6d.; cotton-covered tinned copper wire, single, 25g, 12yds 9d., 50yds 3/-, many uses; C twin bell wire, 1/9 doz, yds; ditto, heavier quality, 2/3 doz, yds; ditto, flat rubber-covered, 3d. yard; twin flat braided electric cable, 6d. yard; Wood's metal stick, 2 1/2in by 1/4in, 1/-; cotton-covered copper instrument wire, 1/4lb reels, 18, 20, 22, 24 gauges, 1/6; 26, 28 gauges, 1/9; 30, 32g, 2/-; 34g, 2/3; 24, 26, 28g, silk-covered, 2oz reels, 1/6; 30, 32, 34, 36g ditto 1/9; 42g, 2/-; 16g double silk-covered, 1lb, 5/-; sensitive permanent detectors, tellurium-zincite combination, complete on base, guarantee efficient, 2/6; reliable crystal, with silver cats-whisker, 6d.; reconditioned headphones, complete, 4,000 ohms, 12/6; all postage extra.—Post Radio Supplies, 33, Bourne Gardens, London, E.4.

**LINE** cord, 2-way, 3/6 per yard; 3-way, 4/6 per yard (approx. 60 ohms per foot); speakers, Celestion (latest) speaker, 2 1/2in, pm, 27/-; 8in, pm w/transformer, 27/6; 6 1/2in, pm (multi-ratio transformer), £1/8/6; 10in pm (with trans.), 57/6, (less trans.), 52/6 (for P.A. work); Rola 5in, pm, 22/6; 6in, pm, 21/- (less transformer); Goodman, 5in, pm (less trans.), 30/-; 2-gang condensers, 0.0005, less trimmers 14/-, with trimmers 15/6; midget coils, 6/6 per pair; valve holders (British and American types); volume controls (all values), less switch 3/6 each, with switch 4/6 each; mains transformers, 4v and 6v, 27/6 ea; mains transformer of radio valves in England, list prices plus purchase tax, B.V.A. and American; Rothermel (crystal) pick-ups, metal S8 £3/14, Senior de luxe £3/18/9; condensers, all types in stock, 4's, 8's, 16's, 32's, mfd, 500v working, 0.1, 0.01, 0.25, 0.002, 0.5, etc., etc.; special offer, silver mica condensers, all values, 4/6 per doz.; assorted parcel, 6 doz. lots, £1/10, 12 doz. lots £2; accumulators, glass, 2v, 45 dmp, 14/6; celluloid (portable), 2v, 17/6; resistances, 1/2 and 1 watt, all values, 1/- each, 10/6 per doz.; strictly cash with order, plus postage; enquiries invited.—Matt Radio Service (Kingston 4881), 152, Richmond Rd., Kingston-on-Thames, Surrey. [3488]

**AUSTERITY**  
**RADIO LIMITED**

For  
**CONSTRUCTORS' KITS**  
see last month's issue

**MAINS TRANSFORMERS**

Primary, 10-0-200-220-240; screened primary, H.T. 375-0-375 at 175 ma.; LTI, 5 v. 2 a.; LT3, 6.3 v. 4 a.; LT3, 6.3 v. 4 a. Price 52/6 each, post 1/1.  
350-0-350; 150 ma.; L.T.s. 6.3 v. 5 a.; 4 v. 4 a.; Rec. 5 v. 2 a.; 4 v. 2 1/2 a.; can be used with international or English valves. Colour coded. Mains Input tapped 200/220/240 A.C. 50/-, post 1/1. 400-0-400; 120 ma.; L.T.s. 4 v. 2 1/2 a.; 4 v. 4 a.; 4 v. 2 a.; 4 v. 2 a.; Long Colour Coded Leads, with high insulation. (200/220/240) Mains Input Tappings, 45/-, post 1/1.  
350-0-350; 80 ma.; 4 v. 4 a.; 4 v. 2 a.; A/O Mains Input 230, 30/-, post 8d.  
300-0-300; 80 ma.; 4 v. 4 a.; 4 v. 2 a.; A/O Mains Input 230, 30/-, post 8d.  
350-0-350, Chassis Mounting, Shrouded, 4 v. 4 a.; 4 v. 2 a., Input 200/220/240, 35/-, post 9d.  
300-0-300, 75 ma., Chassis Mounting, Shrouded, 4 v. 4 a.; 4 v. 2 a.; Input 200/230/250, 37/6.  
Mains Transformers, wound to specification.  
**L.F. TRANSFORMERS**, Midget, 3:1, 4:1, 5:1 ratios, 6/- each.  
**L.F. CHOKES**, 15 Hy., 80 ma., 1,000 ohms, tapped at 360 and 640. Price 12/6 each. 30 Hy., 80 ma., 1,000 ohms, Price 17/6. Small 10 Hy., 50 ma.; 380 ohms, 8/6.  
**PUSH-PULL** Input Transformers, heavy duty. Split secondary windings ratio 4:1. Price 16/6. Small for Parallel Feed Standard, 6/-.  
**OUTPUT TRANSFORMERS**, Standard Pentode, midget, 3 ohms, 7/6. Pentode small, 8/6. Multi-ratio, standard, 12/6.

**4-VALVE, 4-WATT**  
**GRAMOPHONE**  
**AMPLIFIER CHASSIS**

Assembled on black Crackle-finished chassis fitted with separate Tone Control, Volume Control with on/off switch, sockets for microphone, gramophone and extension speaker. Hum free, good quality reproduction. A.C. only. Input 200/250 v. Size overall, 8 x 6 1/2 x 7 1/2in. Ready to play. Price, **10 Gns.** including valves and speaker.  
Theoretical and practical Bine Prints of the above available separately, 2/6 pair.

**CONDENSERS**, 2-gang, small, 2 trimmers, fixing brackets, .0005 ceramic-insulation, boxed, 14/6. 3-gang Small, .0005 Ceramic insulation, fixing brackets, boxed, 13/6.

**SHORT WAVE TUNING CONDENSERS**, .0001, .00014, .00015, 3/6 each; .00018, 4/-; .0002, 4/6 each.

**REACTION CONDENSERS**, .0003, .0005, .00015; Differential .0003, .0005, 3/-.

**Trimmers**, T.O.C. Straight Line Air Spaced, 10 to 35 pf. max., 1/-; Single Ceramic, postage stamp type, 30 pf., 9d.; 30/80, 100/120, 150/250, 180/200, 1/- each. Twin Trimmer, Ceramic, .0005, 2/6.

**Silver Mica Condensers**, wire ended, 40 pf., 88 pf., .00015, etc., 9d. each.

**Resistors**, standard values, 1 watt, 6d.; 1 watt, 1/- each.

**Main Dropping Resistors**, with variable tappings, 2 a. 1,000 ohms, 8/-; 3 a. 750 ohms, 7/- each. Wire Wound Resistors, 500, 1,000, 2,000 ohms, 10 watt, 2/6 each.

**Microcore Solder**, 6d. box.

**Volume Controls**, 10,000, 50,000, 100,000, 1 meg., 1 meg., 3/6, less switch.  
**Toggle Switches**, Miniature, on-off, single pole, 2/6. D.P., D.T., 3/3.

**Coils**, Short Wave, 16 to 50 metres, on Faxolin Formers, colour coded, A. & H.F. with reaction, boxed matched pairs, 4/- with circuit. Aerial and Oscillator Coils, Long, Medium and Short (16-50 m.) on one former, 12/6 pair.

**Medium Wave**, Midget, 8/1 per pair.

**Line Cord**, 3-core, .3 amp. 60 ohms per foot, 5/- per yard.

**Flexible Couplers**, 1/2 spindle, 1/- each.

**307, HIGH HOLBORN,**  
LONDON W.C.1. Phone HOLBORN 4631

## SEXTON'S for SERVICE & SATISFACTION

**THE DORSET BATTERY THREE** for £6.6.0. This excellent battery radio can be constructed at home without any previous knowledge of radio. Complete instructions, including full-size wiring diagrams, chassis drilling template, every step and wire described explicitly. 3/6 post paid.

**THE WIZARD FOUR** valve, AC/DC mains. This mains radio can also be built at home at a maximum cost of only £9.9.0. Instructions contain full-size wiring and assembly diagrams, drilling template, etc., components can be obtained from any radio dealer. Complete instructions 5/- post paid.

**LOUDSPEAKERS**, "Rola" 5in. with trans., 29/6; 8in. size with multi-ratio trans., 32/6. "Celestion" with trans., 8in. size, 29/6. Goodman's 3in., two types available, 2-3 ohms or 12-15 ohms speech coil, 30/- each. "Celestion" mains energised 10in. size, 2,000 ohms speech coil, 42/6 each; with trans., 50/- each.

**Three-Gang .0005 Tuning Condensers**, large type with slow motion drive, mounted on metal frame, suitable for any radio, 12/6 each.

**War-Time Civilian Radio Receivers** for A.C. mains only. Four-valve superhet circuit. A soundly constructed radio with plenty of volume, complete in cabinet, 42.3.4.

**American Radio Valves**. We stock most types. Write for lists.  
**Auto-Transformers**. 200-watt type. 100 volt input, 240 output and vice versa, 22/6 each.

Terms: Cash with order only. Send 1d. stamp for latest list.

**J. E. SEXTON & CO. LTD.**  
164, Gray's Inn Road, London, W.C.1.  
Tel.: Terminus 1304 & 4842.

## YOU can become a first-class RADIO ENGINEER

We are specialists in Home-Study Tuition in Radio, Television and Mathematics. Post coupon now for free booklet and learn how you can qualify for well-paid employment or profitable spare-time work.

**T. & C. RADIO COLLEGE**  
2 The Mall, Ealing, W.5

(Post in unsealed envelope, 1d. stamp.)

Please send me free details of your Home-Study Mathematics and Radio Courses.

NAME .....

ADDRESS .....

W.V.37

**VOIGT HO** horn and base chamber, twin cone unit with ac field rectifier, offers; Magnavox 66 200-250v dc field, £5; modern walnut radiogram cabinet, £3; 12in cathode ray tube with stand and deflector coils, £3/10; buyers must arrange own carriage.—Miall, 46, Station Rd., Orpington, Kent. [3474]

**LOOK! Look! Look!** 4- and 6-volt combined mains transformers; 3-way line cord, 0.3-amp; 120-watt auto transformers; speaker transformers; volume controls (with and without switch); p.m. and m.e. speakers (with and without transformer); spade terminals; wander plugs; Bakelite electrical accessories; etc., etc.; trade only; send 1d. stamp for latest list. Ralph Lewis and Co., Ltd., 150, Charing Cross Rd., London, W.C.2. Tem. 0232. [3468]

**HENRY'S** offer.—T.C.C. 2mfd, 1,000v wkg., 7/6; T.C.C. block, 4x4x2x2x1x5 mfd, 450v wkg., 17/6; Celestion 6 1/2in mains energised, 700 ohms, with trans., 32/6; Midget t.r.f. coils, med. waves, 6/6 pr., with ac/dc circuit; also med. wave coils, with trim, 8/6 pr.; Bulgin twin fuse-holders, with safety cover, 2/9; mid 2-gang cond., with trim, 14/-; 3-gang, 12/6; 0.2 line cord 2-way, 500-ohms length, 7/6; 3-way, 10/-; 1 jack and 2 plugs with 6ft lead, 6/-, complete; Westinghouse h.t. 10.200v 100 mA, 21/-; W.6 Westector, 5/-; 5 mA ins. roc., 15/-; Celestion Amphenoil valve-holders, octal, 5 and 4 pin Eng. and Am., 1/- each, 10/6 doz.; 465 i.f. transformer small cans, 15/- a pair; s.a.e. for lists.—Henry's, 5, Harrow Rd., Edgware Rd., Paddington, W.2. [3435]

**A VO** stockist.—Good stocks of avometers for immediate release against contract numbers with priority rating. Unless holding a Government contract don't waste time writing D.C. Minors £3/10, Uni Minors £8/10, model 40 £17/10, model 7 £19/10. For particulars of multipliers, shunts, and transformers for above send 1d. for illustrated list. Wolf electric drill stockist, now free from restriction; to take up to 1/4in drill £8/8, 3/4in £10/10, 1/2in £15/10; state voltage. Send 1d. for illustrated list. Valve stockist, list prices; Brimar, Cossor, Darco, Ever Ready, Ferranti, Hivac, Lissen, Marconi, Ostram, Mazda, Mul-lard, Philips, Triotron, Tungram and American. If uncertain of the type required send old valve or sketch showing position of valve in chassis and model number of set. All valves tested before dispatch; we specialise in matched pairs PX4s, 6V6s, etc. Tungram contacts for Philips tubular converters, sets of 8 3/6. Resistance wires; 1oz 27g 3.2Ω-ohms p. yard max. cur. 9amp, 2/6; 1oz 31g 6.4Ω p.y., max. cur. 52 amp, 3/-; 1oz 33g 8.6Ω p.y., max. cur. 0.42amp, 3/4; 1/2oz 37g 18.5Ω p.y., max. cur. 0.26amp, 2/-; 1/2oz 39g 31.7Ω p.y., max. cur. 0.16amp, 2/2; 1/2oz 41g 44.3Ω p.y., max. cur. 0.14amp, 2/6; 1/2oz 43g 66.2Ω p.y., max. cur. 0.11amp, 3/6. In addition to above we carry complete radio, electrical stocks, and our motto for the last 25 years is, If you can't get from us, give it up. All goods are cash with order, post free over 5/-.—Park Radio, 676, Romford Rd., Manor Park, London, E.12. Tel. III. 2066. [3555]

**COULPHONE RADIO**, New Longton, nr. Preston.—New goods only, all Tungram and B.V.A. valves at present manufactured; mains transformers, interleaved impregnated windings; screened primaries, 350.0-350v 100mA, 4v 6A, 4v 2 1/2A, or 6.3v 3A, 5v 2A, 28/6; bobbins only, windings as above, 15/6; 425.0-425v 200mA, 4v 8A, 4v 4A, 4v 4A, 52/6; smoothing chokes, 251ly 200 mA, 21/6; speaker field coils, 2,000 ohms, 9/6; speakers p.m., less trans, 5in 21/6, 8in 24/-, 10in 35/-; with trans, 8in 30/-, 10in 45/-; 8in energised, 2,000 ohm, with trans, 35/-; output transf, power-pen, 40mA, 8/6; push-pull power-pen, 80mA, 21/-; push-pull extra H.D., 100mA, 37/6; Rola push-pull, 15/6; mains dropper resistors, 800 ohms 0.3A, 2 varitaps, 5/6; push-back wire, 50ft 3/-, 100ft 5/6; tinned copper wire, 1/2lb, 2/3; 2mm sleeving, 3d.; resin-core solder, lb, 4/-; 4mfd, 1,000v dc working paper condensers, 12/6; tuning condensers with trimmers, 0.0005, 2 gang 12/6, 3 gang 13/6; M. and L. wave coils, t.r.f., 12/6 pair; Parafeed i.f. trans, 4:1, 6/6; quality p.p. i.f. transf, split secondaries, 2:1, 22/6; h.f. chokes, 1/9; carbon resistors, 50 1/2ms to 5 megohms, 1/2w 6d, 1w 9d; switch cleaner, 3/6 bottle; vol. controls, less sw, 3/9; with sw, 5/-; Pyrobit pencil bit electric soldering irons, 21/-; grid clips, 10d. doz.; valve-holders, Eng. and Amer., 1d. per pin; smoothing iron elements, 450w, 2/3; fire spirals, 750w 2/-, 1,000w 2/6; shaft couplers, 6d.; tin knobs, 9d.; single-screened cable, 10d. yd; all sizes tubular and mica condense, limited quantity, 3 1/2in dial, 0-1mA m.c. milliammeters, B.S. 1st grade, 70/-; send s.a.e. for the best service list available; no c.o.d.; all orders over 5/- post free, post 6d. extra under 5/-.

Here's to Good Listening



# AMBASSADOR RADIO

WILL SET THE STANDARD  
OF POST-WAR LISTENING  
MAY WE ADD YOUR NAME  
TO OUR MAILING LIST?

R-N-FITTON LTD BRIGHOUSE YORKS.

## WARD ROTARY CONVERTERS

Petrol Electric Generating Plants, H.T. Generators, D.C. Motors, Frequency Changers, etc., up to 25 K.V.A.

**CHAS. F. WARD**  
37, WHITE POST LANE, HACKNEY WICK, E.9  
Phone: Amherst 1393


## TESTOSCOPE



Indispensable to Radio Service Engineers. Makes 20 tests. Interesting Booklet on request. From all Wholesalers or direct. Send for leaflet R.4.

**RUNBAKEN -- MANCHESTER -- I**

## GECALLOY RADIO CORES

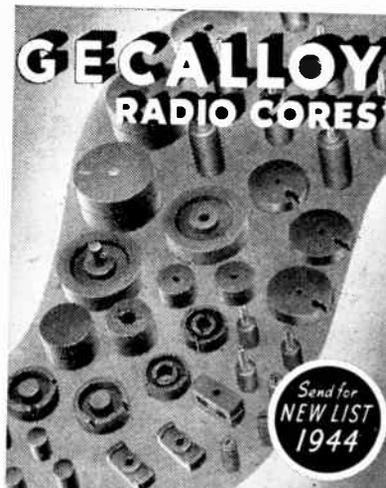

Send for NEW LIST 1944

**SALFORD ELECTRICAL INSTRUMENTS LTD.**  
PEEL WORKS, SALFORD, J.  
Telephone: BRADLEY 688 (4 lines) Turgate and Canal. Salford, MANCHESTER  
PROPRIETORS: THE GENERAL ELECTRIC CO. LTD. OF ENGLAND

# WAVEBAND RADIO

AMERICAN SERVICE MANUALS

Vol. 1. Spanton/Emerson. Vol. 2. Crossley/Belmont. Vol. 3. Crossley/Belmont, part 2. Vol. 4. RCA Victor and GE Admiral. Vol. 5. Emerson, part 2. ALL at 12/6 each, or the set of five for 60/-, post paid.

"RADIO INSIDE OUT." Complete Serviceman's guide, 4/9. Wireless Amplifier Manual, fully illustrated, 2/3. 66-page Radio Valve Manual, 3/9.

"LUSTRAPHONE" Moving Coil Microphone. In modern N.P. case, beautifully finished. Impedance 20-25 ohms. Dimensions: 2 1/2 in. x 4 in. with socket tapped 1/4 in. thread. 85/- (7 days approval allowed).

WALSALL Moving Coil Milliamperimeters, 2 1/2 in. diam., bakelite case, 55/-.

INDUSTRIAL Solder Irons, 18/6. CAR VIBRATORS, 12 volt, 15/-.

CARBON RODS, 12 in., for Sunray Lamps, 1/4 in. diam., 1/-.

DROPPERS. .3 amp., 800 ohms, with feet, 5/9.

SWITCHES. D.P.D.T. Rotary Switches, 4/-.

TWIN SCREENED WIRE. 6 yards for 7/6.

VOLUME CONTROLS. Every value in stock, with switch, 5/9.

STANDARD SPEAKER FIELD COILS, 2,000 or 1,500 ohms, 8/6.

TRANSFORMERS. 25 watt P.P. O.P. transformers, 27/6.

CHOKES. Heavy duty chokes, 30 hys. 120 m.a. 200 ohms, 14/6.

REPLACEMENT BOBBINS, for either 6 v. or 4 v. mains transformers, 18/6.

TWIN H.F. Suppressor chokes, 4/6. METAL BUZZERS, 2/6.

EXCLUSIVELY MAIL ORDER


## WAVEBAND RADIO LTD.

63, Jermyn St., Piccadilly, London, S.W. 1



## EQUIPMENT

### THE "BROADWAY" A15 AMPLIFIER

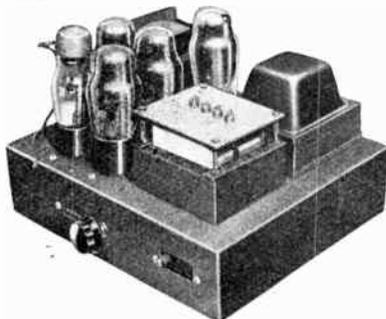

Designed and produced for Dance Halls, Canteens, Clubs, Etc. For Reproduction of Gramophone Records and announcements.

CIRCUIT. Fifteen watts obtained with two 6F6 valves in Push Pull. First anode is a 6J7C feeding into 6J5 as phase changer. RC coupled to the two 6F6's.

A large, specially made Output Transformer is tapped at 3, 5 and 8 ohms. The chassis, 10 x 8 x 2 1/2, finished black crystalline, has the valve sockets, input strip and mains adjuster parts already riveted in position, fixings are provided for the transformers. Smoothing is by Paper Mansbridge Condensers. Simply bolt the trans. to the chassis and wire up. Supplied complete with valves and all accessories.

Price £12.10.0

Other equipments include a 45-watt amplifier and an A.C. Mains TRF receiver in unique cabinet. For full details write (enclosing stamp) for Leaflet A12.

Full size Blue Prints of these Kits are available 2/3 each.

**RADIO INSTRUMENT CO., Radio Products,**  
249, BROADWAY, BEXLEY HEATH, KENT.

THE Simplex Four, theoretical circuit diagram of 4-valve m. wave, ac/dc t.r.f. Midget, with all component values, 1/6; complete kit of parts, valves, etc., for this most successful Midget receiver, £9; Midget polished cabinet, 30/-; Midget aerial and h.f.m. wave, t.r.f., high gain coils, 9/- pair; short wave, aerial and oscillator coils, i.f. at 465 kc/s, 5/6 pair; ditto m. wave coils, 9/- pair; Midget 2-gang variable 0.0005mf condensers, 15/-; 3-gang, 14/-; Midget chassis de luxe, sprayed grey, 10 1/2 by 6 by 2 in, drilled 4 valves, 9/6; "Simplex" Midget chassis, drilled 4 valves, and all component holes, speaker cut-out, electro zinc finish, 11 by 4 1/2 by 2 in. 7/6; Midget dials, m. wave, 4 x 3 1/2 in., ivorine, 2/-; Midget chokes, 7/6; heavy duty, 80ma, 12/6; 120ma, 15/-; Midget speaker transpen, 27/6; R. & A. Bin. M.F. field, 1,200 ohms, with trans., 35/-; condensers, 25mfd, 12vw, 2/-; 250mfd, 25vw, 4/6; 0.1mf, 8/-; doz; Midget rotary switches, on/off, 3/-; d.p.s.t., 3/6; d.p.d.t., 4/-; line cord, 3-way, 60 ohms foot, 0.3 amp, 6/6 yard; ditto 2-way, 5/- yard; mains droppers, 0.2 amp, 1,000 ohms, 4/6; 0.3 amp, 800 ohms, 5/6; comprehensive list, monthly, 2/4d.; s.a.e. enquiries; postage all orders.—O. Greenlich, 34, Bancroft Rd., Cambridge Heath Rd., London, E.1. Ste. 1334. [3549]

CHARGER kits, instrument rectifiers, mains transformers, gramophone pick-ups, mikes. Metal rectifier 2v half amp, with transformer, makes ideal trickle charger for 2v wireless cell, 13/6, postage 7d.; instrument rectifiers for meters, bridge type, bakelite, very good make, 1ma and 5ma, 18/6, post 3d.; 10ma to 50ma, 15/6. Metal rectifier 6v 2.5amp, with transformer and ballast bulb for 2v 6v charger, weight over 5lb, 46/6, post 10d.; ditto, 2amp, 42/6; ditto, 1.5amp, 35/-, post 10d.; Junior 6v charger kit approx. 0.8amp charge, 29/6, post 10d.; all with instruction sheet and circuit. New charger kit, superior model, weight over 12lb, ideal for car battery boosting, 6v-12v at 3amps continuous, also charges at 1.8amp or 1.2amp, price £4/17, post free, packing returned. Metal rectifier for 2v to 12v charger, 37/6, post 9d.; ditto, 1.5amp, 47/6; also the popular model 12v 2.5a rectifier, with transformer and ballast bulb, 59/6, postage 10d. Mains transformers, 21v, tapped at 10v and 14v 2amps, 26/-, postage 9d.; also 21v tapped at 16v 4amps, 55/-, post 1/1. Rothermel Senior bakelite crystal pick-ups, 78/9; Rothermel D.104 de luxe microphones, £4/14/6; also the "Bullet" microphones by Rothermel, £3/5; moving coil microphones in stock, leaflet and price list on application with 1d. stamp, a new standard of value set by this really fine production.—Champion 43, Upland Way, N.21, Lab 4457.

SOUTHERN RADIO'S wireless bargains.—S. Special offer of latest radio publications: "Radio Valve Manual," equivalent and alternative American and British types, with all necessary data, 3/6; "Radio Circuits," fully illustrated, receivers, test equipment, etc., 2/-; "Services Signalling Manual," Morse, International code, etc., 1/-; "Amplifiers," fully descriptive circuits, 2/-; "Radio Manual," formulas, tables, colour code, etc., 1/-; Telsen large drives, complete boxed (type W184), 2/6; reaction conds., 0.0001, 0.00015 1/9; 2mfd conds., P.O. upright paper type used but fully guaranteed, high working voltage, age, 2/6; Ace P.O. mikes, complete with trans., ready for use with any receiver, 7/6; Multicon mica conds., 28 capacities in one, from 0.0001 upwards, 4/-; crystal detectors, complete, 2/6; Dr. Cecil crystals, 6d., with catwhisker, 9d.; push-back wire, insulated, 25yds for 5/-; insulated sleeving, assorted colours, yd. lengths, 3/6 doz; single screened wire, doz yds, 10/-; twin screened wire, 17/- doz yds; metal case conds., 0.1+0.1+0.1, high working voltage, 2/6; power rheostats, Cutler-Harmer, 30 ohms, 4/6; push-button switches, 3-way 4/-, 8-way 6/- (all complete with knobs); escutcheons for 8-way p.b. switches, 1/6; p.b. knobs, 6d.; pointer knobs (black or brown), special instrument type for 1/4 in spindles, 1/-; Erie resistances, brand new, wire ends, 1/4, 1/2, 1 and 2w, mostly low values, but a very useful selection, 100 for 30/-; copper earth rods, 18in, 2/6; heavy duty I.F. chokes, 30hys, 100ma, 250 ohms 14/-, 500 ohms 16/-, 1,000 ohms 17/6; we have for disposal a large quantity of brand new assd. screws, sample 1lb weight, 5/-; soldering tags, including spade ends, 6/- gr; coil formers, ceramic and paxolin, 7/6 per doz; special bargain offer of 50 assd. conds., 20 tubulars, 20 mica conds., 8 silver mica conds. and 2 electrolytic conds., all brand new, 47/6 the parcel of 60; all types of Probit soldering iron available from stock, chassis mounting valve holders, English and American types, all sizes, 1/- ea.; hundreds more bargains.—Southern Radio Supply Co., 46, Lisle St., London, W.O. Gerrard 6653. 18023

# ELECTRADIX

We carry large stocks of Radio—Electrical—Mechanical and Scientific Apparatus. You are invited to visit our showrooms.

MOVING COIL SOUND UNITS. P.M. 45 ohm, 1/4 in. coil, 1 1/4 in. overall, complete for little speakers, mikes, headphones, etc., coil energised by famous ALNI Magnet. In bakelite case, with 3in. front flange. As new, 12/6.

SMALL MOTOR GENERATORS by E.D.C. and others. Pocket size for use with Receivers to take the place of H.T. battery, will drive off small 6- or 12-volt accumulator, output 230 v. 30 ma., beautifully made for Government radios. Brand new, 75/-.

HAND MIKES for announcers, broadcasters and recorders, hand type by Tannoy, multi-cell carbon type, weatherproof, suitable for hall or outdoor use, with neat switch in handle, 21/-.

TRANSFORMERS. 3 kW Crypto, 230 v. to 115 v., shrouded, £12. 3 kW Metvick, 50 cy. 400 v. to 600 v., £9 10s. 1 kW Powquip 50 cy. 250 v. to 50 v. 20 amps., £9. 500 watt Foster 50 cy. 440 v. to 110 v. 5 amps., £4/15/-. 150 watt Foster 400 cy. 230 v. to 15 v. 10 amps., £2/15/-. 5 watts H.T. test Transformers, 110/220 v. to 1,000 v. 5 m.a., 10/-.

TRANSFORMER PARTS. We have a limited number of shrouded Transformer carcasses for rewinding, 3 kW. size, with laminations, first-class make, 75/-.

METERS. Moving coil milliammeters, flush panel type, 3in. dia., 0-1 m.a. 100 ohms resistance, bakelite case, new, 60/-. Voltmeters, precision A.C./D.C. moving iron type, flush panel, 3 1/2 in. dia., 0-60 volts dead beat, 45/-. Polarised M.I. voltmeters for D.C. readings only, 0-9 volts, flush panel type, 2 1/2 in. dia., 21/-. Many other bargains available. Send us your enquiries.

MOTORS A.C. Motors 230 volts, new, 1,425 r.p.m., enclosed type with starting switch incorporated, 1/2 h.p. and 1/4 h.p. for prompt delivery.

MOTORS D.C. Fine modern motors, 1/5th h.p., 200/250 volts, enclosed, drip proof, silent bearings, double end shaft weight 35 lbs. Compound, 1,440 r.p.m., 70/-.

MOTOR PUMPS. We can give immediate delivery of the famous Stuart Turner 12-volt D.C. motor pumps; 120 gallons per hour, 84/-. Same type, but for A.C. mains, 136/-. Pumps only: R type twin-piston rotary for 1/2 h.p. motor drive, £3/5/-.

PETROL FILTERS. Enots brass petrol filter with union, 7/6.

BUTTON MICROPHONES are SOUND TRANSMITTER UNITS. A marvel of acoustic engineering design, as used by G.P.O. For amplification and detection of sound for all purposes.

### EVERY BUTTON GUARANTEED.

The lin. dia. brass body forms the granule chamber and the diaphragm is thin mica. Needs only a pocket battery 4 1/2 volts and a high ratio transformer. With special transformer and instructions, 7/6. Button only, 2/6.



RHEOSTATS "AETNA" panel switch rheos. to 1 ohm and off, 6 volts 3 amps., with bulb in knob, 2/6 each, postage 6d. Slider rheos. for all currents; heavy grid 40. 10-stud control, 240 volts to 45 volts, 33in. x 16in. x 14in., £5/10/-; smaller for 110 volts to 45 volts, £3/10/-. Pickin Lab. rheos., circular 8in. glass front, 50 ohms 2 amps., 35/-.

CONTROL BY LIGHT and Invisible Rays. Raycraft sets with selenium bridge, 10,000 ohms tele-type Relay, fittings and booklet, 42/-.


G.P.O. ELECTRIC COUNTERS to 10,000, 5/6 each.

Please include postage for mail orders.
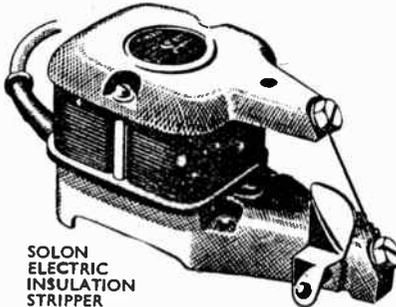
## ELECTRADIX RADIOS

214, Queenstown Road, Battersea, London, S.W. 8  
Telephone MAcaulay 2159

**SOLON**  
INDUSTRIAL  
ELECTRIC APPLIANCES



SOLON  
ELECTRIC  
INSULATION  
STRIPPER

The SOLON Electric Insulation Stripper provides a quick method of severing the insulation neatly without damaging the conductor, by means of an electrically heated wire. Full details are given in Folder Y.9, which also describes the range of SOLON Electric Soldering Irons and the SOLON Electric Solder Pot.

**W. T. HENLEY'S TELEGRAPH WORKS  
COMPANY, LIMITED,  
WESTCOTT • DORKING • SURREY**



**FOR THE  
RADIO SERVICE  
MAN, DEALER  
AND OWNER**

The man who enrolls for an I.C.S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

Special terms for members of H.M. Forces and discharged members of H.M. Armed Forces.

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

Dept. 38, International Buildings,  
Kingsway, London, W.C.2

Please explain fully about your instruction in the subject marked X.

Complete Radio Engineering  
Radio Service Engineering  
Elementary Radio Television

And the following Radio examinations:

British Institution of Radio Engineers  
P.M.G. Certificate for Wireless Operators  
City and Guilds Telecommunications  
Wireless Operator & Wireless Mechanic, R.A.F.

Name.....Age.....  
Address.....

**SERVICEMEN.**—The following products are well designed and of high quality; volume controls, carbon type, all values, with or less switch, wire-wound resistors, 1 to 60 watts; dropper resistors, 0.2 and 0.3amp; line cords and razor resistors; terms and quotations on req.—Dagole, Ltd., 35, High St., Ruislip, Mdx.

**L INECORD.** 0.3amp, 3-way, 3/6 per yd.; un-drilled chassis, 8x7x2 1/4, 3/- ea., doz lots at 2/3 ea.; volume controls, 0.25, 0.5, 1.0 meg, short spindles, no switch, 2/6 ea.; American oct. valve-holders, 7/6 doz; 2mm sleeving, 2/9 doz yds; resin cored solder, 4/6 lb; 18G tnd. cpr. wire, 4/- lb; Midget medium wave coils, 5/- pair; Midget 60ma chokes, 6/6 ea.; Multitap, 5/-; 0.3amp, 5/6 ea.; both with fixing feet; mains transformer replacement bobbins, 4v, or 6.3v heaters, 17/6; electric soldering irons, 12/6; black set knobs, bushed, 7/6 doz; "Meico" moving coil microphones, massive all-chrome quality job, £5/5; solder tags, 2/- gross; etc.; large stocks valves, all service requirements, list 1d.; orders above 10/- post free (mail order only).—A. Huckelsbee, "Hazlejohn," Crofton Lane, Orpington.

**WANTED, EXCHANGE, ETC.**  
WANTED, Mullard TV6 tuning indicator valve.—Box 3567. [3532]

WANTED, Rich. Bundy E105 choke.—Rudd, 132, Trafford Rd., Norwich. [3532]

WTD., 3 Ostar Gantz valves, 1G5, 2V3.—Davidson, 22, Douglas St., Bannockburn.

**B.T.H.** Pezolectric pick-up wanted.—Say Heriot-Watt College, Edinburgh, 1. [3548]

WTD., Universal Avominor, good cond.—Avery, 43, Broom Rd., Teddington, Mdx.

**VARIOUS** split valve adaptors wanted.—Ramsay, Eastholme, Bigby Rd., Brigg.

**ACOUSTIC** chamber or infinite baffle cabinet for 18in speaker.—Osborne, 30, Forester Rd., Bath. [3491]

WANTED, Voigt domestic corner horn, with or without unit.—G., 7, Villiers Rd., Southall, Middx. [3544]

**NATIONAL H.R.O.** Senior, with complete set coils, power pack and speaker, and H.R.O. 1-10.—Below.

**GARRARD** 201a motor and turntable, Walco sapphire needle and Telefunken T1001.—79, Allesley Old Rd., Coventry. [3520]

**H.M.V.** or Garrard auto-change ac gram. motor, with p.u., in good condition, wanted.—Box 3370. [3547]

**REQUIRED,** Howe box baffle for 12in auditorium speaker.—Reply to J. L. Ware, 18, Gunter Grove, S.W.10. [3476]

WTD., bandpass coils for 2 hf diode tuner, or complete tuner or Wireless World Straight Six.—Box 3352. [3482]

WANTED, electric gramophone described W.W., May 11th, 1939.—Rathke, 40, West St., Dorking, Surrey. [3492]

WANTED, recording unit, with motor; Parmeko preferred.—Trinder, 36, Hurst Rd., Longford, Coventry. Tel. 88811. [3501]

**WE** offer cash for good modern communication and all-wave receivers. — A.C.B. Radio, 44, Widmore Rd., Bromley. [1541]

WTD., All-Wave mains signal generator, Avo preferred; cash or exchange new valves, electrolytics, etc.—Box 3366. [3529]

WANTED, "Wireless World" for 1941, '42, '43 and '44.—Saunders, 71, Southbourne Gdns., Eastcote, Middlesex. [3543]

WTD., "W.W.," Sep, 1943; Dec. 2 & 9, '37; Sep. 22, '38; Feb., Mar., Apr., May, '40.—Pugh, 14, Varley Rd., Liverpool, 19.

**TRADER** Service Sheets wanted; various back numbers required to complete stock.—Radio Service Depot, Wellgate, Rotherham.

WANTED, automatic record changer, universal preferable, if not, ac 230v.—Chapman, Waterloo House, High St., Ascot, Berks.

WANTED, Service oscillator, capacitor, etc., measuring bridge, signal analyser, available for 230v ac, 50 cycle mains, and output meter; also service sheets.—Particulars to BM/ABY, London, W.C.1. [3497]

WANTED, National P.W. drive, coil unit range A and latest manual for Senior H.R.O.; also Simpson's electric turntable.—Box 3364. [3526]

**EXCHANGE** to value for autochanger with Hypersens; or m/coil pick-up; H.M.V. ac player; new high-voltage electrolytics; crystal pick-up; Remington close-shaver; ferrocast coils and 4-gang; m/coil meters; cash, etc.—Solent Hotel, Ventnor, I.O.W. [3486]

**WE** buy for cash, new, used, radio, electrical equipment all types; especially wanted, radios, radiograms, test equipment, motors, chargers, recording gear, etc.—If you want to sell at the maximum price, call, write or phone to University Radio, Ltd., 22, Lisle St., Leicester Square, W.C.2, Ger. 4447.

**REPAIRS AND SERVICE**  
Mains transformers re-wound and constructed to any specification; prompt delivery.—Brown, 3, Bade Burn Rd., Jarrow. [3480]



**OR INSTRUMENT MOUNTINGS**  
a few types of which are illustrated, have been specially developed to take care of different frequencies and to control vibration. Types and sizes available to carry varying loads (Rubber to metal bonded).

**HARRISFLEX BEARINGS LIMITED**  
TIDDINGTON ROAD · STRATFORD-ON-AVON

**Aladdin**  
**RADIO CORES**  
for all purposes  
**GREENFORD, MIDDx. WAXLOW 2300**

**AMERICAN MIDGETS HANDBOOK**

Describing with many circuit diagrams the peculiarities of small American (Midget) Radios. Especially written for service men, most likely faults and their remedies with hints on wartime substitutes for unobtainable parts are all given. The valve data section gives bases and working characteristics of the 80 or so valves used in midgets.

Price 2/6

from booksellers or by post, 2/8.

V.E.S. (W.)

Radio House, Melthorne Drive, Ruislip, Mdx.

**THESE ARE IN STOCK**

**TIME BASES. SCANNING GENERATORS.**

By O. S. Puckle, M.I.E.E. 16/-. Postage 5d.

**FOUNDATIONS OF WIRELESS.**

By M. G. Scroggie, B.Sc., A.M.I.E.E. 7/6. Postage 4d.

**HIGH FREQUENCY. THERMIONIC TUBES.**

By A. F. Harvey, B.Sc. (Eng.) Wales, D.Phil. Oxon., A.M.I.E.E. 18/-. Postage 5d.

**RADIO RECEIVERS AND TRANSMITTERS.**

By S. W. Amos and F. W. Kellaway. 21/-. Postage 5d.

**RADIO LABORATORY HANDBOOK.**

By M. G. Scroggie, B.Sc., A.M.I.E.E. 12/6. Postage 4d.

**WIRELESS SERVICING MANUAL.**

By W. T. Cocking, A.M.I.E.E., of the "Wireless World." 7/6. Postage 4d.

**VALVE REPLACEMENT MANUAL FOR RADIO SERVICE ENGINEERS.**

By A. C. Farnell and Arthur Woffenden. 6/-. Postage 2d.

We have one of the Finest Stocks of Technical Books in the Country.

**THE MODERN BOOK CO.**  
19-23, Prad Street, London, W.2.

# CALLING ALL AMATEUR RADIO CONSTRUCTORS!



**COMPONENTS.**

Well-known makers' products and 100% guaranteed by us.

**CHASSIS.**—Ready for assembly, drilled and sprayed, or zinc-plated, 5/6.

**VALVE HOLDERS.**—All bases in stock, 1/-.

**DIALS.**—Medium and long-wave stations printed, 1/-.

**TWO-GANG CONDENSERS.**—Special midjet condenser with or without (long spindle) trimmers, 15/6.

**THREE-GANG CONDENSERS.**—Standard type, 12/6.

**MAINS TRANSFORMERS.**—EME 200/230 volts 300-0-300, 4 v. 4 amps., 4 v. 2 amps., 37/6.

**ACCUMULATORS.**—Multi-plate, 2 v. 16 amps., 17/6.

**SPEAKER TRANSFORMERS.**—Universal output (Pentode and Power), 6/9. Universal Midjet model, 6/9.

**VOLUME CONTROLS.**—Most values in stock, with switch, 6/9, less switch, 4/9.

**POTENTIOMETER.**—Wire wound, variable, 0-10 ohms, complete with knob, 3/9.

**TRIMMER SCREWDRIVERS.**—Non-capacity ebony, 1/9 each.

**RESISTORS.**—1 watt, card of 36 assorted values, 27/6; 1/2 watt, 26/-; 5 and 10 watts, 12 values assorted, 21/-.

**DROPPERS.**—Ready to fit, 1/2 doz. assorted: Cosmor, Ferranti, Decca, Mascotto, Ferguson, Ekco, instead of £2.3s. 37/6.

**VARIABLE MAINS DROPPER RESISTORS.**—2 or 3 amps., 6/9. Resistor in cages to permit fixing outside set, 3 amps., 740 ohms, 11/9.

**TRF COILS.**—Set of medium wave coils (Aerial and HT), complete with diagram, 9/6; ditto, ditto, popular type, 8/-.

**LINE CORD.**—2 core 2. 3/11 per yd.; 3 core 3. 4/9 per yd. (60 ohms per foot).

**MIKE CABLE.**—Twin rubber sheathed, screened, 1/9 per yd.

**SPEAKERS.**—8in. Rois, less transformer, 23/-.

**VIBRATORS.**—Brand new American, "MALLORY," 6 v. 4-pln, fully guaranteed, 13/6.

**MODERN AIDS.**

"**TESTOSCOPE.**" the vest pocket instrument for tracing faults. Enables 20 tests AC/DC, complete with leads, 27/6.

"**ELCO**" Electrical Light Weight Soldering Iron (state voltage), 13/6.

"**FLIK-O-DISK**," a novel calculator of Ohm's Law problems, 6/6.

"**PYROBIT**" new tester, for testing continuity earth connections, leads, etc., 59/6.

**MOVING COIL METERS.** 30 amps., charge, discharge, bakelite case, 19/6.

**CAR AERIALS.** telescopic, nickel-plated, 35/-.

Orders under 10/- C.W.O., otherwise G.O.D. Stamp with enquiries please. B.O.T. retail prices.

## J. BULL & SONS

(Dept. W.W.)

246, HIGH ST., HARLESDEN, N.W.10  
(See our February Classified Advertisement)

## THE AURI-PHONE

A miniature Ear-  
phone with a high-  
fidelity reproduction  
of Speech and  
Music equal to best  
headphones known.  
1 1/16 inch diam.;  
holds in Ear with-  
out headband or  
wire loop. Two  
interchangeable  
nipples, large and  
small; two models. 10 ohms and 1000 ohms.  
Operate from prim. or sec. terminals of Speaker  
transformer. Ideal for pocket radio, Valve or  
Crystal set. 5ft. flex cord. Price, black or  
flesh-colour enamel, 38/- each. Note: We do  
not make Deaf Aids.



**CEFA INSTRUMENTS, 38a, York Street,  
TWICKENHAM, Middx. POPesgrove 6597.**

**ACCURATE** radio rewinds, mains trans-  
formers, fields, op. transformers, etc.—  
Southern Trade Services, 297-299, High St.,  
Croydon. [2882]

**LOUDSPEAKER** repairs, British, American,  
any make; moderate prices.—Sincclair  
Speakers, 12, Pembroke St., London, N.1.  
Terminus 4355. [3308]

**ALL** types of radio receivers serviced;  
A. Murphy and Pilot specialist; valves in  
stock; sound repairs for 13 years.—T. E.  
Fevyer, F.I.P.R.E., 50, Vine St., Uxbridge.

**RADIOS,** speakers, electrical appliances re-  
paired, good stocks of valves, radio com-  
ponents and electrical goods.—Radio Service  
Depot, Donnington Wood, Wellington, Shrops.

**RADIO** repairs quickly executed to all  
makes, English or American; lowest pos-  
sible prices.—The Music Box, 89, London Rd.,  
London, S.E.1. (Tel. Waterloo 460 and 6766.)

"**SERVICE with a Smile.**"—Repairers of all  
types of British and American receivers;  
coil rewinds; American valves, spres, line  
cords.—F.R.I. Ltd., 22, Howland St., W.1.  
Museum 5675. [1575]

**MAINS** transformers service, repairs, re-  
winds, or construction to specification of  
any type, competitive prices and prompt ser-  
vice.—Sturdy Electric Co., Ltd., Dipton, New-  
castle-upon-Tyne. [3084]

**24-HOUR** service, 6 months' guarantee,  
any transformer rewind; mains 15/6,  
outputs, 4/-; i.f. transformer, 3/-; all types  
of new equipment supplied to specification.—  
Majestic Winding Co., 180, Windham Rd.,  
Bournemouth. [2764]

**REWRINDS** mains transformers, field coils and  
chokes, high grade workmanship even to  
ten days' delivery; new transformers manu-  
factured against Government contracts.—Metro-  
politan Radio Service, 1021, Finchley Rd.,  
Golders Green, London, N.W.11. [2603]

**TO** radio dealers and service engineers only.  
—Loudspeakers repaired quickly, or  
materials supplied; also big stocks of all  
components; send your trade card or billhead  
and 1d. stamp for our current lists.—A.W.F.  
Radio Products, Borough Mills, Sharpe St.,  
Bradford, Yorks. [3410]

**TRANSFORMER** rewinds and replacement  
coils, machine layer wound on bakelite  
formers, interleaved, impregnated and clearly  
marked, rewinds 1s. per unit, standard types  
to 70 watts; replacement coils, 15/6; larger  
types and additional secondaries pro rata; dis-  
count to trade; delivery by return post most  
types in common use; state model and iron  
size when ordering coils; cash with order or  
c.o.d.; fully guaranteed.—Radio Services, Field  
St. Works, Blackpool. R.T.R.A. Service mem-  
bers. Tel. 1774. [3328]

**DEGALLIER'S, Ltd.**—"Service with a  
guarantee." If you cannot get your  
receiver serviced, let American specialists do  
the job; first-class workmanship only; special-  
ising in Air-King, Belmont, Challenger, Det-  
rola, deWald, Emerson, Ferguson Garod,  
Hallifactor, Hammerlund, McMurdo, Mid-  
west Majestic, Pilot, Philco, Sparton, etc.,  
also any British set. Remember, for 15 years  
we have handled as distributors American re-  
ceivers; this is self-explanatory; s.a.e. with  
all enquiries.—Degallier's, Ltd., 9, Westbourne  
Court, London, W.2. [3398]

**MISCELLANEOUS**

**RUBBER** stamps.—V. E. S., Radio House,  
Ruislip. [3209]

**TIME** recorders.—Write for particulars.—  
Gledhill-Brook Time Recorders, Ltd., 84,  
Empire Works, Huddersfield. [2419]

**CHASSIS** trans. shrouds, clips and many other  
fittings quickly made on A.A. benders;  
accurate and inexpensive.—Details from A.A.  
Tools, 197w, Whiteacre Rd., Asht'n-u-Lyne.

**MANUFACTURERS!!!**—Radio wholesaler  
wishes to increase regular stock lines by  
the addition of new types of radio products.—  
Will manufacturers please send full particu-  
lars to Box 3209. [3025]

**CAPACITY** available for all types of electrical  
and radio assembly, all types of coil  
and transformer winding with vacuum im-  
pregnation to approved Ministry Super Tropi-  
cal Standards.—S. Green, 44-45, Tamworth Rd.,  
Croydon. Tel. Croydon 8025. [3517]

**ELECTRIC** guitar units.—Convert your  
guitar to an electric model by making  
one of my high-efficiency electro-magnetic  
units; complete constructional details, with  
blue prints, of three tested and guaranteed  
designs, 5/-.—L. Ormond Sparks (W), 9, Phoe-  
beth Rd., Brockley, London, S.E.4. [3551]

**TUTORIAL**

**RADIO** Engineering.—Television and Wire-  
less Telegraphy, comprehensive postal  
courses of instruction.—Apply British School  
of Telegraphy, Ltd., 179, Clapham Rd., Lon-  
don, S.W.9 (Estd. 1906). Also instruction at  
school in wireless for H.M. Merchant Navy  
and R.A.F. [9249]

## LONDON CENTRAL RADIO STORES

### NEW GOODS SURPLUS TO GOVERNMENT NEEDS

#### WIREWOUND POTENTIOMETERS



4,000 ohms. Open type on  
porcelain formers, 9/16 spindle,  
2 1/2 x 1 in. As illustrated. 12/6.

25,000 ohms. Tropical type  
enclosed in bakelite moulding  
1/4 in. spindle, 1 1/2 x 1 in. 5/6.

#### SPEAKERS


Goodmans 3 1/2 in. P.M. 3.2 ohms speech coil, less  
transformer. 30/- R. & A. 8 in. mains energised  
with Pentode output transformer, 1,200 ohm field,  
42/6. Celestion 10 in. P.M. with transformer. 47/6.

#### VITREOUS ENAMELLED RESISTORS

5-watt. 1.5, 500, 1,500, 5,700 ohms, 3/6 ea. 1-watt  
4,000, 8,000 ohms, 1/- ea. 2 ohms 10-watt approx.  
6/6, 23 ohms 0.4 amp., 5/6.
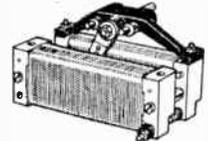
#### SLIDING RESISTANCES

1,100 ohms 0.4 amp.  
wirewound on twin  
porcelain formers. A  
first class engineering  
job. 37/6.



#### MAINS TRANSFORMERS

Made by Philips. A.C. input 100/250 v. Screened  
primary. 300-0-300 v. 80 m.a., approx., 6.3 v., 12.5 v.  
Highly impregnated. Colour coded leads to facilitate  
wiring. 18/6.

#### TWIN CARBON POTENTIOMETERS

0.5 megohm. 8/6.


#### D.C. Moving Coil MILLIAMMETERS

0-25 m.a., 2 in. clear reading dial. Flush mounting.  
Made by Ernest Turner Electl. Insts., Ltd. £3 5s.

#### MOVING COIL MILLIAMMETER

0-6 m.a., 2 in. clear reading dial, in 2 1/2 in. flush mounting  
bakelite case. Extra scales for conversion to voltmeter  
and ohmmeter. Internal resistance 250 ohms. £3.

#### TWO-RANGE D.C. VOLTMETERS

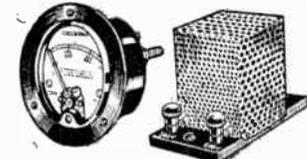

Moving coil 0-300, 0-600 v. Complete with shunt.  
2 in. clear reading dial. Flush mounting. Made by  
Ernest Turner Electl. Insts., Ltd. £5 5s.

**MIDGET POT. METRES.** Wirewound, 8 ohms. 4/6.

**ELECTROLYTIC CONDENSERS.** 60 mfd., 250 v. peak  
wkg. Metal cased. Insulated terminals. 4 1/2 x 2 1/2 x  
1 1/2 in. 15/6. 4 mfd., 800 v. D.C.W. Metal cased.  
5 1/2 x 3 1/2 in. 15/6.

**CONDENSERS.** Metal cased. 0.1 mfd., 1,000 v  
D.O.W. Insulated terminals. 2 1/2 x 2 1/2 in. 5/6.

**TUBULAR CONDENSERS.** 0.1 mfd., 350 v. D.C.W.  
Bakelite with metal ends. Tag terminals. 2/-.

**23, LISLE STREET,  
LONDON—GERrard 2969—W.C.2**

**L**EARN Morse code the Candler way.—See advertisement on page 27. [1292]  
**R**ADIO training.—P.M.G. exams and I.E.P. Diploma; prospectus free.—Technical College, Hull. [0611]  
**A** POSTAL training in electrical engineering—power or radio; individual correspondence tuition by highly qualified engineers with wide teaching and technical experience. Elementary or advanced courses. Preparation for recognised examinations. Pre-service training specially arranged.—G. B., 18, Springfield Mount, Kingsbury, N.W.9. [1731]  
**T**HE Tuition Board of the Institute of Practical Radio Engineers have available home study courses covering elementary, theoretical, mathematical, practical and laboratory tuition in radio and television engineering; the text is suitable coaching matter for I.P.R.E. Service-entry and progressive exams; tuition fees—at pre-war rates—are moderate.—The Syllabus of Instructional Text may be obtained post free from the Secretary, Bush House, Walton Avenue, Henley-on-Thames, Oxon. [1462]

**SITUATIONS VACANT**  
**R**ADIO.—Fully expd. technical salesman wanted; amateur ham not objected to; permanency. Full pars., sal. reqd., etc., to Berry's (Short Wave), Ltd., 25, High Holborn, London, W.C.1. [3550]

**P**OST-WAR plans.—Radio manufacturer will reserve valuable agency in certain areas for ex-Servicemen and give every assistance to re-establishing business quickly. In first instance write, giving full details of your pre-war business, etc., in confidence, to Box Z, c/o Victor Stewart and Co., Chartered Accountants, 82, Victoria St., London, S.W.1. [3550]

**R**ADIO service manager required; permanent position with good prospects for advancement; high-class trade, Belts district.—Write full details of technical experience, Box 3548. [3550]

**O**UTSIDE technical representative required. should have established personal contacts with radio designers; experience in design or manufacturing department of radio manufacturers desirable; salary about £600 p.a.; age 30-45 years.—Box 3323. [3536]

**P**OST-WAR development.—Body of radio technicians are desirous of making contact with persons interested in the formation of a concern dealing with specialised electronic devices; enquiries of a technical and financial nature are invited.—Box 3556. [3502]

**SITUATIONS WANTED**  
**P**ICTURE transmission.—Experienced operator seeks permanent post.—Box 3346. [3536]

**A**DVERTISER, with wide sales, production and engineering experience in electronics and public address, requires executive position.—Box 3368. [3537]

**R**ECORDING engineer, over 12 years' exp. of manufacturing, maintenance and research, seeks progressive post; available when N.S. release granted.—Box 3353. [3507]

**I**DEAS for sale.—Electrical engineer, Cambridge graduate, served apprenticeship, age 31, wishes to connect with small firm requiring technical direction; prepared to work in spare time on post-war projects, own or otherwise, until released from Government research laboratory.—Box 3387. [3503]

**PATENT NOTICES**  
**R**ADIO-electric patents.—Well-known London radio component manufacturers are open to consider patents or designs for post-war period.—Write Progress, c/o Alfred Bates & Son, Ltd., 130 Fleet St., London, E.C.4.



**W. BRYAN SAVAGE LTD.**

Expert assistance in the solution of problems relating to

● TRANSFORMERS, CHOKES

● AMPLIFIERS

● POWER UNITS

and Specialised Equipment embodying

ELECTRONIC CONTROL

WESTMORELAND RD., N.W.9  
 COLINDALE 731

**HILL & CHURCHILL**

BOOKSELLERS

SWANAGE DORSET

ENGLISH & AMERICAN

BOOKS IN STOCK ON

RADIO AND

TELECOMMUNICATION

CATALOGUE ON APPLICATION

**COVENTRY RADIO**

Component Specialists since 1925

- COIL FORMERS. Paxolin. 3" x 1 1/2" dia. ... 3d.
- CONDENSERS. .0003, .0005 mfd. bakelite dielectric ... 3/6
- TRIMMERS. 3-30 P.F. Postage stamp type 6d.
- L.F. CHOKES. 15/20 H., 500 ohm, 80 m.a. 8/9
- SWITCHES. Toggle S.P. On—Off ... 2/6
- SWITCHES. Rotary. 1 pole., 10-way ... 5/-

The above are a few items taken from our LATEST LIST. Price 1d.

PROMPT SERVICE, COMPLETE SATISFACTION

THE COVENTRY CO.

191, DUNSTABLE ROAD, LUTON.

OPEN ON SATURDAYS UNTIL 6.30 P.M.

**BERRY'S (SHORT WAVE) LTD.**

In addition to the usual radio parts, we carry a most complete range of

**RADIO AND ELECTRONIC EQUIPMENT**

including C.R. Tubes 2I", £3 6s. 0d.; 4I", £6 1s. 0d. Meters, 0.5 ma. 57/6; 0/1. 75/6. Meico 5w Amplifier—£16 10s. 0d. Rothenmel Crystal Mikehead, £4 15s. Pickups, 73/6, 78/9. Ceramic S.W. Variables: .0001, 4/6; .00018, 4/9; 15 mmf., 3/6; 25 mmf., 3/9; 40 mmf., 4/6; 75 mmf. midgeet, 6/-. Precision 4" S.M. Dial, 9/1, with driving head and vernier. 35/- S.M. Drive, 8/1, with station named dial escutcheon and glass, 8/6. "P" Coils, 2/3, 2/6. I.P.'s, 7/6. Metal Cabinets with hinged lid, panel and chassis, 39/6, 63/-. Jacks and Plugs, 2/6 each. S.W. H.P. Chokes, 2/6. All-wave 2.5 ma, 3/6. Toggle and Rotary switches, Ceramic Valve-base, Stand-offs, Feed Throughs, Formers, Radio Manolis. Send 1d. stamp for full list "W" to:—

25, HIGH HOLBORN, LONDON, W.C.1  
 (Tel.: Holborn 6231.)

THE proprietors of British patents Nos. 516110, 516111, 516167, 516168, entitled Improvements in Electron Discharge Tubes, and No. 516169, entitled Improvements in Bases or Caps for Electron Discharge Tubes, offer same for licence or otherwise to ensure their practical working in Gt. Britain.—Inquiries to Singer, Ehrlert, Stern and Carlberg, Chrysler Bldg., New York City 17, N.Y., U.S.A.

THE proprietor of British patents Nos. 527353 and 527484, entitled "Improvements in Photoelectric Cells, and Methods and Means for Making, Sensitising and Stabilising the Same" and "Improvements in Photoelectric Cells, and Method for Making, Sensitising and Stabilising the Same," respectively, offers same for licence or otherwise to ensure practical working in Great Britain.—Inquiries to Singer, Ehrlert, Stern and Carlberg, Steger Building, Chicago, 4, Illinois, U.S.A. [3484]

**TECHNICAL TRAINING**  
 GREAT possibilities exist for technically qualified engineers, key men in wartime and afterwards. Through the home-study courses of The T.I.G.B. take a recognised engineering qualification, such as A.M.I.Mech.E., A.M.I.E.E., A.F.R.Ae.S., A.M.I.Chem.E., C. and G., etc., in which examinations the T.I.G.B. students have passed 25 FIRST PLACES and hundreds of passes. Write to day for "The Engineer's Guide to Success"—free—containing the world's widest choice of engineering courses covering all branches, including aeronautical, mechanical, electrical, wireless, chemical, etc.  
 THE TECHNOLOGICAL INSTITUTE OF GREAT BRITAIN, 82, Temple Bar House, London, E.C.4. [3391]

**BOOKS, INSTRUCTIONS, ETC.**  
**A** TECHNICIAN wants any of the following publications. Kindly state price. Address BM/TLBP, W.C.1.

ANY bound or unbound volume of the Bell System Technical Journal (American), but particularly any of the following issues: Oct., 1931 (Vol. 10); Jan., 1928 (Vol. 7); Jan., 1935 (Vol. 14); April, 1936 (Vol. 15); April 1934 (Vol. 13). Also ANY copies of the Proceedings of the Institute of Radio Engineers (American), but particularly the following issues: May, 1933 (Vol. 21); June, 1934 (Vol. 22); Jan., 1934 (Vol. 22); Dec., 1936 (Vol. 24); May, 1934 (Vol. 22); May, 1935 (Vol. 21); June, 1935 (Vol. 23); July, 1931 (Vol. 19). [3472]

**W**IRELESS WORLD back numbers, Dec. 30th, 1937, to July 6th, 1939, few missing; what offers?—Box 3355. [3483]

**R**ADIO books.—Extensive range always in stock, including many that are out of print; call or write for free list.

**T**HE MODERN BOOK COMPANY, 19-23, Praed St., London, W.2. Padd. 4185.

**W**EBB'S radio map of the world locates any station heard, size 40x30in, 4/6, post 6d.; on linen, 10/6, post free.—Webb's Radio, 14, Soho St., W.1. Gerrard 2089.

*just because they give no trouble—don't forget*

**DALY ELECTROLYTICS**  
**DEALERS—Don't pay more than 2/9 for DALY 8 M.F. 500 P.V.**  
**DALY (CONDENSERS) LTD**

Condenser Specialists for over 20 years  
 West Lodge Works, The Green, Ealing, W5  
 Telephone Ealing 4841

**AFTER THE WAR!**

The advance in Radio Technique after the war will offer unlimited opportunities of high pay and secure posts for those Radio Engineers who have had the foresight to become technically qualified. How you can do this quickly and easily in your spare time is fully explained in our unique handbook.

Full details are given of A.M.I.E.E., A.M.Brit.I.R.E., City & Guilds Exams., and particulars of up-to-date courses in Wireless Engineering, Radio Servicing, Short Waves, Television, Mathematics, etc., etc.


**We Guarantee "NO PASS—NO FEE"**

Prepare for to-morrow's opportunities and post-war competition by sending for your copy of this very informative 112-page guide NOW—FRFE.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 388)**  
 17, Stratford Place, London, W.1

Printed in England for the Publishers, LIFFE AND SONS LTD., Dorset House, Stamford Street, London, S.E.1, by THE CORNWALL PRESS LTD., Paris Garden, Stamford Street, London, S.E.1. "Wireless World" can be obtained abroad from the following—AUSTRALIA AND NEW ZEALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: Imperial News Co.; Gordon & Gotch, Ltd. SOUTH AFRICA: Central News Agency, Ltd.; William Dawson & Sons (S.A.), Ltd. UNITED STATES: The International News Co.

# TO MEET THE ELECTRONIC AGE

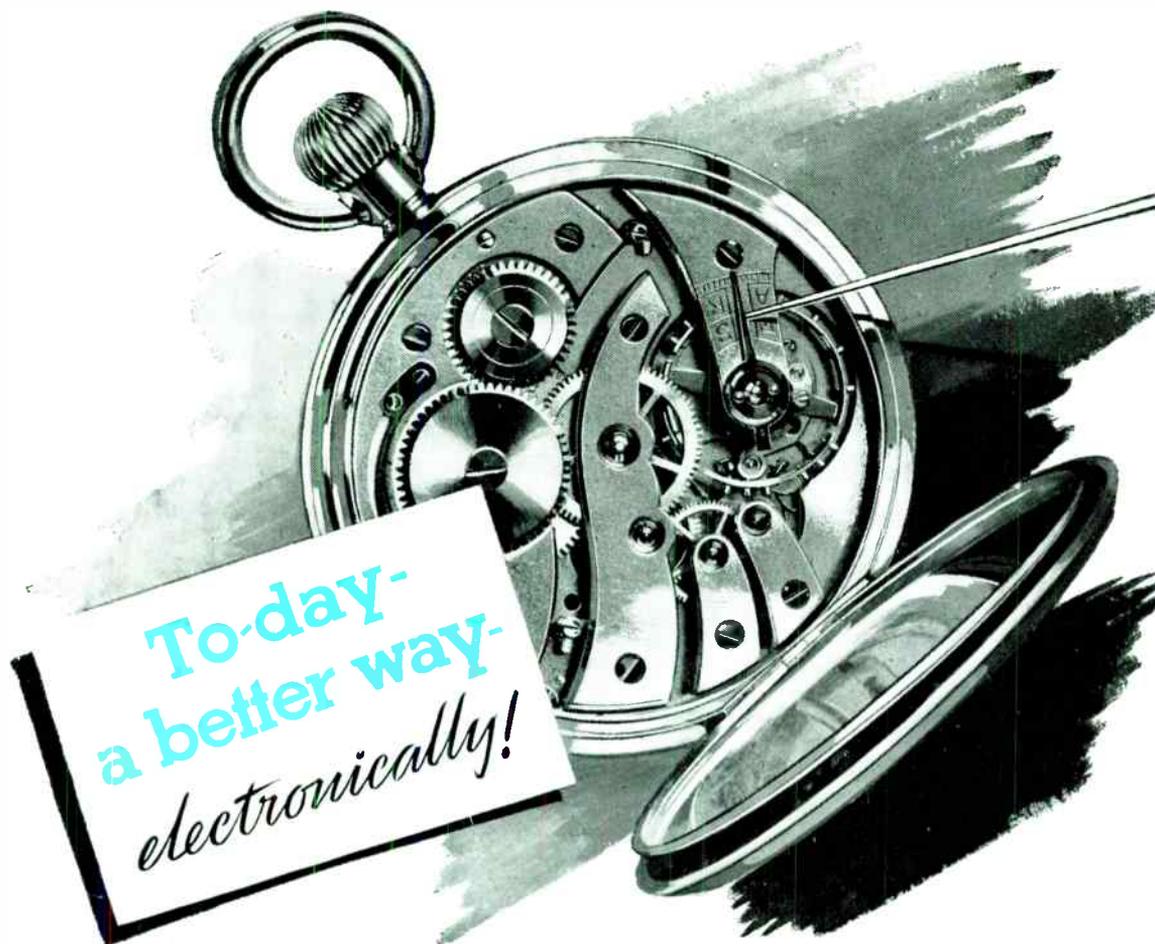

REGULATING a watch—or clock—is a tedious and hit-and-miss process. It's expensive, too, for the manufacturer. Imagine row upon row of watch movements being given their final testing—probably spread over several days—to ensure the highest standard of time-keeping accuracy.

That was the method until Electronics lent a magical hand to speed up the operation. Nowadays the job is simplicity itself. A watch movement (of the type to be regulated) is timed to split-second accuracy and its beat recorded on the oscilloscope.

This oscillograph, used as a master curve, permits each newly assembled watch movement to be regulated with very great accuracy almost as quickly as the shelling of the proverbial peas!

In a thousand different forms Electronics is helping Industry to speed up production—to reduce costs—to improve quality. As makers of capacitors—an essential component of every electronic circuit—we are vitally interested in this new Science. If you are already planning some new electronic development we offer you our co-operation and the benefit of our experience.



A. H. HUNT LTD • LONDON • S.W.18 • ESTABLISHED 1901

# Exide

## BATTERIES

## FOR RADIO

are playing their part in the great national effort. They are as indispensable to the purposes of war as to those of peace

THE CHLORIDE ELECTRICAL STORAGE COMPANY LIMITED  
Grosvenor Gardens House, Grosvenor Gardens,  
London, S.W.1